
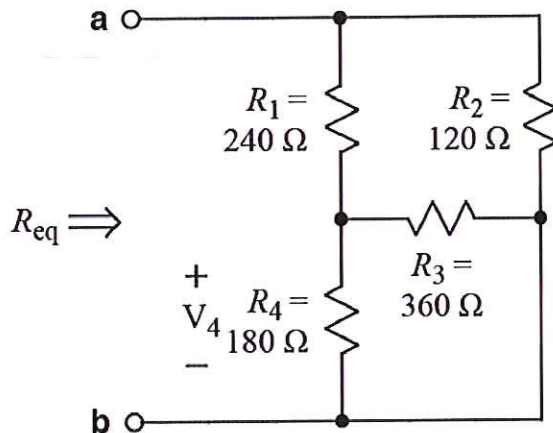


2. (20 points)

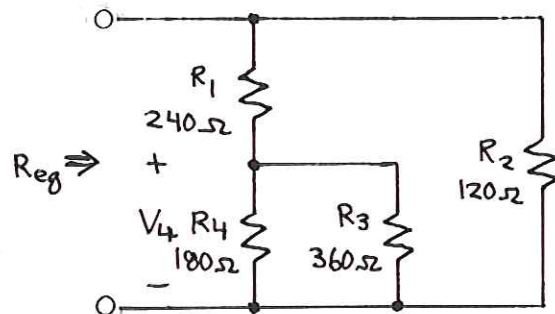

- a) Find the value of the equivalent resistance, R_{eq} .
 b) If 12 Volts is applied across a and b with + on top, find V_4 .

sol'n: a) We may redraw the circuit as follows:



$$R_{eq} = (R_1 + R_3 \parallel R_4) \parallel R_2$$

$$R_3 \parallel R_4 = 180\ \Omega \parallel 360\ \Omega = 180\ \Omega \cdot 1 \parallel 2$$

$$= 180\ \Omega \cdot \frac{2}{3} = 120\ \Omega$$

$$R_{eq} = (240\ \Omega + 120\ \Omega) \parallel 120\ \Omega = 360\ \Omega \parallel 120\ \Omega$$

$$= 120\ \Omega \cdot 3 \parallel 1 = 120\ \Omega \cdot \frac{3}{4} = 90\ \Omega$$

$$R_{eq} = 90\ \Omega$$

b) The voltage across R_4 is the same as the voltage across $R_3 \parallel R_4$. We know the voltage across $R_1 + R_3 \parallel R_4$, allowing us to use a voltage divider (with R_2 not involved).

$$V_4 = 12V \cdot \frac{R_3 \parallel R_4}{R_1 + R_3 \parallel R_4}$$

or

$$V_4 = 12V \cdot \frac{120\Omega}{240\Omega + 120\Omega}$$

or

$$V_4 = 12V \cdot \frac{1}{3} = 4V$$