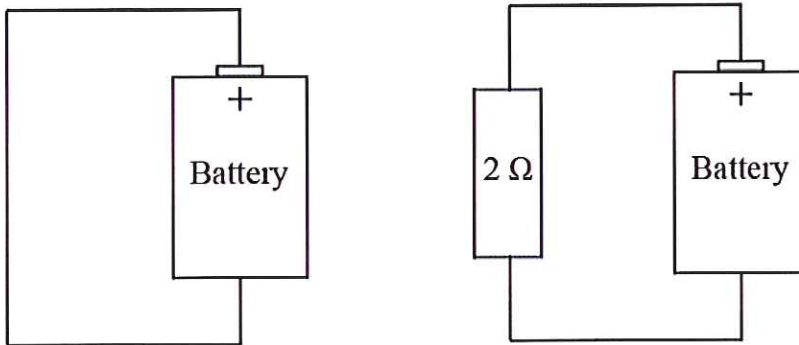


3. (25 points)




When the above battery is shorted out by a wire, it delivers 20 A of current.

When a $2\ \Omega$ resistor is connected across the battery, the voltage across the resistor is 8 V.

- Find a Thevenin equivalent model of the battery.
- How much power is dissipated by the resistance in the battery when the battery is shorted out?

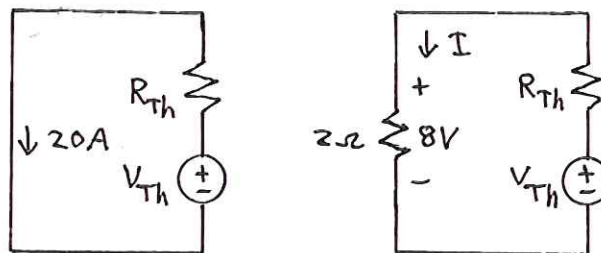sol'n: a) We have the following circuits.



From the first circuit, we have

$$20\text{A} = \frac{V_{\text{Th}}}{R_{\text{Th}}}$$

From the second circuit, we have

$$I = \frac{8\text{V}}{2\ \Omega} = 4\text{A} = \frac{V_{\text{Th}}}{R_{\text{Th}} + 2\ \Omega}$$

So

$$20\text{A}R_{\text{Th}} = V_{\text{Th}} = 4\text{A}(R_{\text{Th}} + 2\ \Omega)$$

$$20A(R_{Th}) = 4A(R_{Th}) + 4A(2\Omega)$$

or

$$20A(R_{Th}) = 4A(R_{Th}) + 8V$$

or


$$16A(R_{Th}) = 8V$$

or

$$R_{Th} = \frac{8V}{16A} = \frac{1}{2}\Omega$$

$$\text{And } V_{Th} = 20A R_{Th} = 20A \cdot \frac{1}{2}\Omega = 10V$$

Battery
Model:

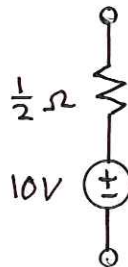

- b) When shorted out, the current is $20A$ (from problem statement). The power in the $\frac{1}{2}\Omega$ is I^2R where $R = \frac{1}{2}\Omega$.

$$p = I^2R = (20A)^2 \cdot \frac{1}{2}\Omega = 200W$$