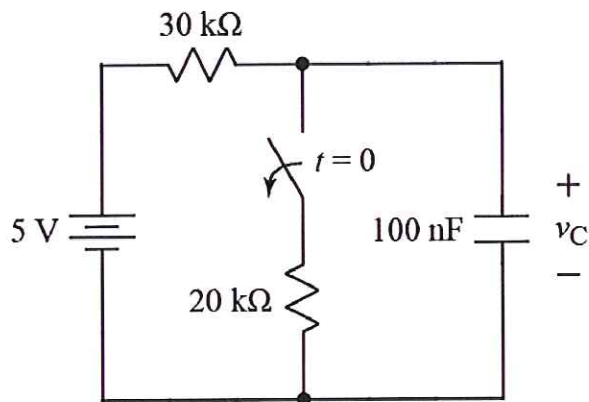



Ex:



The switch is closed for a long time before opening at $t = 0$.

- Find the energy stored by the capacitor at $t = 0$.
- Find an expression for $v_C(t > 0)$.
- If the switch is closed again at $t = 4\tau$ and left in that position forever, find the value of $v_C(t \rightarrow \infty)$.

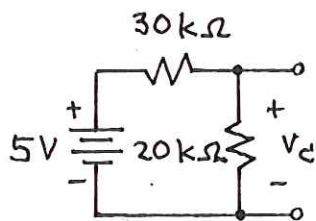sol'n a) We consider $t = 0^-$. $C =$ open circuit
 C is in parallel with $20\text{k}\Omega$ resistor.



We have a V -divider.

$$v_C(t = 0^-) = 5V \cdot \frac{20\text{k}\Omega}{20\text{k}\Omega + 30\text{k}\Omega} = 5V \left(\frac{2}{5} \right) = 2V$$

$$\text{Energy is } w_C = \frac{1}{2} C v_C^2(0^-) = \frac{1}{2} (100\text{nF})(2V)^2 = 200\text{nJ}.$$


b) We use the general form of solution.

$$v_c(t > 0) = v_c(t \rightarrow \infty) + [v_c(t=0^+) - v_c(t \rightarrow \infty)] e^{-t/\tau}$$

where $\tau = R_{Th} C$

From (a) we know $v_c(t=0^+)$ since $v_c(0^+) = v_c(0^-)$.

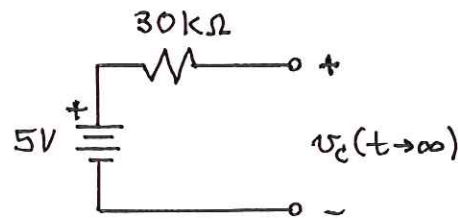
For $v_c(t \rightarrow \infty)$, the switch is open and C acts like an open circuit.



Since no current flows in the $30k\Omega$ R, the voltage drop across it is 0V. The $v_c(t \rightarrow \infty)$ value will be 5V.

$$v_c(t \rightarrow \infty) = 5V$$

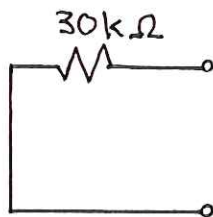To find R_{Th} , we turn off the 5V source and look into the circuit from the terminals where C is attached.



$$\leftarrow R_{Th} = 30k\Omega$$

$$\tau = 30k\Omega \cdot 100nF$$

$$\tau = 3ms$$

$$\text{So } v_c(t > 0) = 5V + [2V - 5V] e^{-t/3ms}$$

c) If the switch is closed and the circuit stays in that configuration forever, we have the same situation as at $t=0^-$.

$$\text{So } v_c(t \rightarrow \infty) = 2V.$$