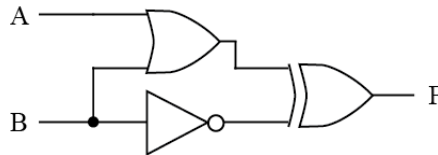




Ex: For the circuit below, write a Boolean expression for F in terms of A and B in the simplest possible way.



SOL'N: From the diagram, we write a Boolean expression for F.

$$F = (A + B) \oplus \bar{B}$$

Expanding the X-OR, we have

$$F = \overline{(A + B)\bar{B}} + (A + B)B.$$

Using De Morgan's theorem, we can rewrite the first NOR as an AND.

$$F = \overline{\bar{A}\bar{B}} + AB + BB$$

Eliminating redundant terms, we have an OR function and one inversion.

$$F = \overline{\bar{A}\bar{B}} + AB + B = \overline{\bar{A}\bar{B}} + B = \bar{A} + B$$

Using De Morgan's theorem, we could use a NAND gate, but we would have one additional gate input. Thus, the OR gate is a better solution.

$$F = \overline{\bar{A}\bar{B}}$$