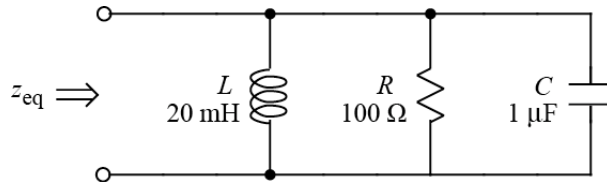




Ex:




Find the numerical value of the equivalent impedance,  $z_{eq}$ , for the above circuit. Frequency  $\omega = 10 \text{ kr/s}$ . Express your answer in polar form.

SOL'N: We convert to the frequency domain by computing impedance values.

$$j\omega L = j(10\text{k})(20\text{m})\Omega = j200\Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j(10\text{k})(1\mu)}\Omega = -\frac{j}{10\text{m}} = -j100\Omega$$

Our frequency domain circuit:

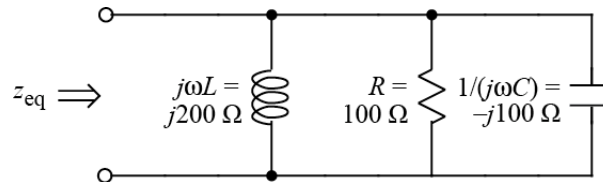

We treat impedance just as we would resistance. We have  $R$  in parallel with  $C$  and  $L$ .

$$z_{eq} = 100\Omega \parallel -j100\Omega \parallel j200\Omega = 100\Omega \cdot (1 \parallel -j \parallel j2)$$

We combine the two imaginary impedances first.

$$-j \parallel j2 = \frac{1}{\frac{1}{-j} + \frac{1}{j2}} \cdot \frac{j}{j} = \frac{j}{-1 + \frac{1}{2}} = -j2$$

So we have the following impedance:

$$z_{eq} = 100\Omega \cdot (1 \parallel -j2) = 100\Omega \cdot \frac{1}{\frac{1}{1} + \frac{1}{-j2}} = 100\Omega \cdot \frac{1}{1 + \frac{j}{2}}$$

This expression is simple enough for us to use rationalization:

$$z_{\text{eq}} = 100\Omega \cdot \frac{1}{1 + \frac{j}{2}} \cdot \frac{1 - \frac{j}{2}}{1 - \frac{j}{2}} = 100\Omega \cdot \frac{1 - \frac{j}{2}}{1^2 + \left(\frac{1}{2}\right)^2} = 100\Omega \cdot \frac{1 - \frac{j}{2}}{\frac{5}{4}}$$

or

$$z_{\text{eq}} = 100\Omega \cdot \frac{4}{5} \cdot \left(1 - \frac{j}{2}\right) = 80\Omega \cdot \left(1 - \frac{j}{2}\right) = 80\Omega - j40\Omega$$

In polar form:

$$z_{\text{eq}} = 80\Omega \cdot \left(1 - \frac{j}{2}\right) = 80\Omega \cdot \sqrt{1^2 + \left(\frac{1}{2}\right)^2} e^{j \tan^{-1}\left(\frac{-1/2}{1}\right)}$$

or

$$z_{\text{eq}} = 80\Omega \cdot \frac{\sqrt{5}}{2} e^{-j26.6^\circ} \doteq 40\sqrt{5} e^{-j26.6^\circ} \Omega = 89.4 e^{-j26.6^\circ} \Omega$$