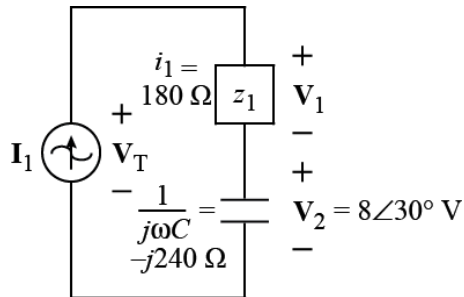


Ex:



- Find I_1 in rectangular form.
- Find V_T
- Find the numerical value of the phase angle between V_T and I_1 ?

SOL'N: a) The current is the same everywhere around the loop. Use Ohm's law for z_2 :

$$I_1 = \frac{V_2}{-j240\Omega} = \frac{8 \angle 30^\circ}{240 \angle -90^\circ} \text{ A} = \frac{1}{30} \angle 120^\circ \text{ A}$$

or

$$I_1 = 33.3 \angle 120^\circ \text{ mA} = -16.65 + j28.84 \text{ mA}$$

- b) Use a voltage sum with Ohm's law for z_1 :

$$V_T = V_1 + V_2 = I_1 z_1 + 8 \angle 30^\circ \text{ V}$$

or

$$V_T = \frac{1}{30} \angle 120^\circ \cdot 180\Omega + 8 \angle 30^\circ \text{ V}$$

or

$$V_T = 8 \cos(30^\circ) + j8 \sin(30^\circ) + 6 \cos(120^\circ) + j6 \sin(120^\circ) \text{ V}$$

or

$$V_T = 8 \frac{\sqrt{3}}{2} + j8 \frac{1}{2} - 6 \frac{1}{2} + j6 \frac{\sqrt{3}}{2} \text{ V}$$

or

$$V_T = -3 + 4\sqrt{3} + j4 + j3\sqrt{3} \text{ V} = 10 \angle 66.87^\circ \text{ V}$$

- c) Take the absolute value of the difference of the angles.

$$|\angle V_T - \angle I_1| = |66.87^\circ - 120^\circ| = 53.13^\circ$$