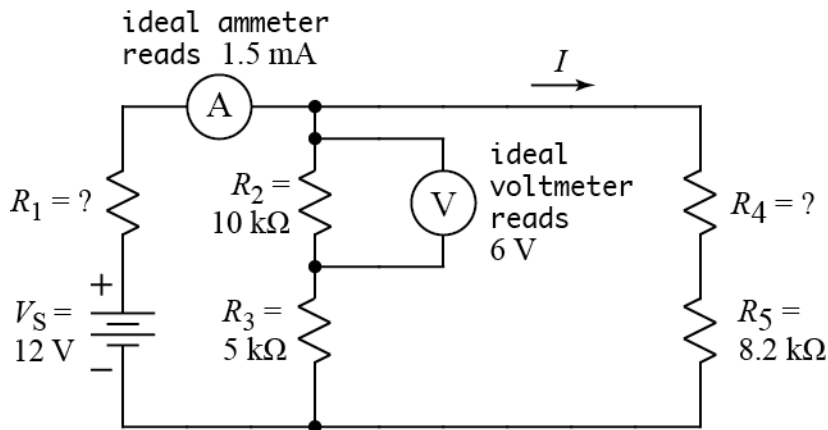


Ex:



Find the values of the following quantities in the above circuit.

- I
- R_4
- P_{R1} (the power dissipated by R_1)

SOL'N: a) We use Ohm's law to calculate the current through R_2 .

$$I = \frac{6\text{ V}}{10\text{ k}\Omega} = 0.6\text{ mA}$$

To find I , we use a current summation at the top center node.

$$1.5\text{ mA} = 0.6\text{ mA} + I$$

or

$$I = 1.5\text{ mA} - 0.6\text{ mA} = 0.9\text{ mA}$$

- The total voltage across R_2 and R_3 is related to the voltage across R_2 by a voltage divider formula.

$$6\text{ V} = V_{R2,3} \cdot \frac{10\text{ k}\Omega}{15\text{ k}\Omega}$$

or

$$V_{R2,3} = 6\text{ V} \cdot \frac{15\text{ k}\Omega}{10\text{ k}\Omega} = 9\text{ V}$$

This voltage appears across R_4 and R_5 . Using I and $V_{R2,3}$ and Ohm's law yields an equation for R_4 .

$$I = \frac{V_{R_{2,3}}}{R_4 + R_5} = \frac{9V}{R_4 + 8.2k\Omega} = 0.9\text{mA}$$

or

$$R_4 + 8.2k\Omega = 10k\Omega$$

or

$$R_4 = 1.8k\Omega$$

c) From a V-loop on the left side, we find the voltage across R_1 .

$$12\text{V} - V_{R_1} = 9\text{V}$$

or

$$V_{R_1} = 3\text{V}$$

We know the current is 1.5 mA, so we can compute the power in R_1 .

$$p_{R_1} = 1.5\text{mA} \cdot 3\text{V} = 4.5\text{mW}$$