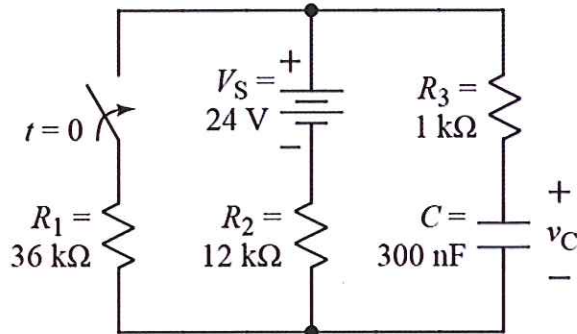



Ex:



The switch has been open for a long time and is closed at  $t = 0$ .


Write the full expression for  $v_C(t)$  for  $t > 0$ , including all the numerical constants that you find.

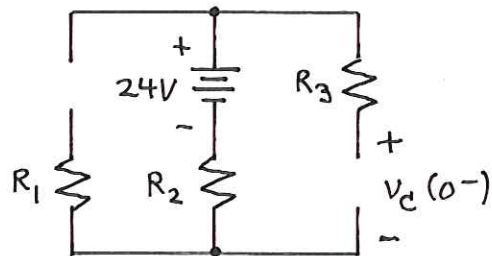sol'n: a) At  $t = 0^-$  the switch is open and  $C =$  open.



No current flows, so  $R$ 's all have 0V drops.  
From  $V$ -loop around center and right side,  
 $v_C(0^-) = 24V$ .

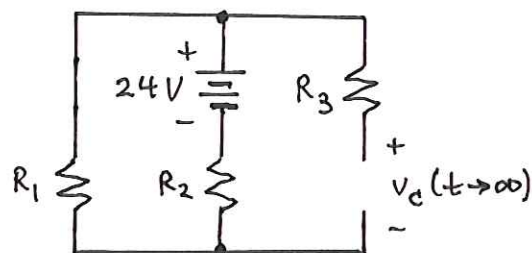For  $t \rightarrow \infty$  the switch is closed and  $C =$  open.



There is no current in  $R_3$  and no  $V$ -drop across  $R_3$ . So  $v_c$  is the same as the  $V$  across the center branch and the same as the  $V$  across  $R_1$ . We use the  $V$ -divider formula to find the  $V$ -drop across  $R_1$ .

$$v_c(t \rightarrow \infty) = 24V \cdot \frac{R_1}{R_1 + R_2} = (24V) \frac{36k\Omega}{36k\Omega + 12k\Omega}$$

$$v_c(t \rightarrow \infty) = 18V$$

For the time constant,  $\tau = R_{Th}C$ , we look in from the terminals for  $C$  with the  $24V$  source turned off (= wire). We see  $R_3$  in series with  $R_1$  parallel  $R_2$ .

$$R_{Th} = R_3 + R_1 \parallel R_2 = 1k\Omega + 36k\Omega \parallel 12k\Omega$$

$$\text{We have } 36k\Omega \parallel 12k\Omega = 12k\Omega \cdot 3 \parallel 1 = 12k\Omega \left(\frac{3}{4}\right) = 9k\Omega.$$

$$R_{Th} = 1k\Omega + 9k\Omega = 10k\Omega$$

We use the general formula for  $RC$  solutions:

$$v_c(t) = v_c(t \rightarrow \infty) + [v_c(0^+) - v_c(t \rightarrow \infty)] e^{-t/\tau}, t > 0$$

$$\text{where } v_c(0^+) = v_c(0^-)$$

$$v_c(t) = 18V + [24V - 18V] e^{-t/10k\Omega \cdot 300nF}, t > 0$$

or

$$v_c(t > 0) = 18V + 6V e^{-t/3ms}$$