
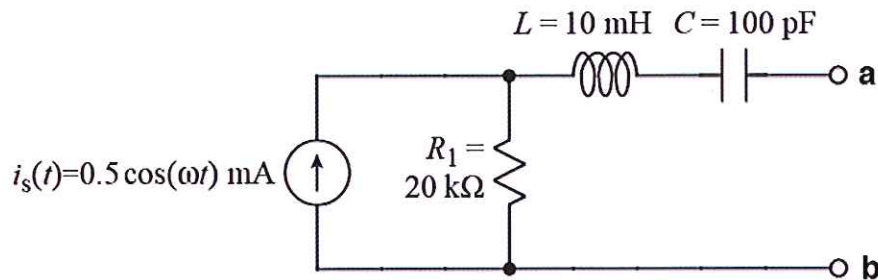


Ex:

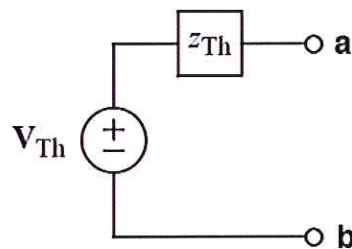

Find the Thevenin equivalent of the above circuit in the frequency domain. That is, find the values of phasor  $V_{Th}$  and impedance  $z_{Th}$  in the equivalent circuit below.

Note:  $\omega = 500 \text{ kr/s}$




sol'n: We use the frequency-domain picture of the circuit.

$$I_s = \frac{1}{2} \angle 0^\circ \text{ mA} \quad (\text{phasor for } i_s(t))$$

$$z_L = j\omega L = j 500 \text{ kr/s} \cdot 10 \text{ mH} = j5 \text{ k}\Omega$$
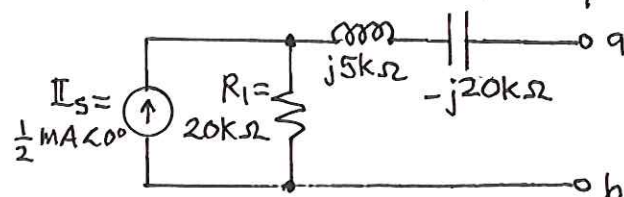
$$z_C = \frac{-j}{\omega C} = \frac{-j}{500 \text{ kr/s} \cdot 100 \text{ pF}} = \frac{-j \Omega}{50 \mu} = -j20 \text{ k}\Omega$$



$V_{TH} = V_{a,b}$  for above circuit.

No current flows in  $L$  and  $C$ , so no  $V$ -drop across  $L$  and  $C$ , and  $I_s$  flows thru  $R_1$ .

$$V_{a,b} = V \text{ across } R_1 = I_s R_1 = \frac{1}{2} \text{ mA} \angle 0^\circ \cdot 20 \text{ k}\Omega$$

or

$$V_{TH} = 10 \angle 0^\circ \text{ V}$$

To find  $Z_{TH}$ , we look in from  $a, b$  with  $I_s$  off, which is an open.

$$Z_{TH} = R_1 + Z_L + Z_C = 20 \text{ k}\Omega + j5 \text{ k}\Omega - j20 \text{ k}\Omega$$

$$Z_{TH} = 20 \text{ k}\Omega - j15 \text{ k}\Omega$$

