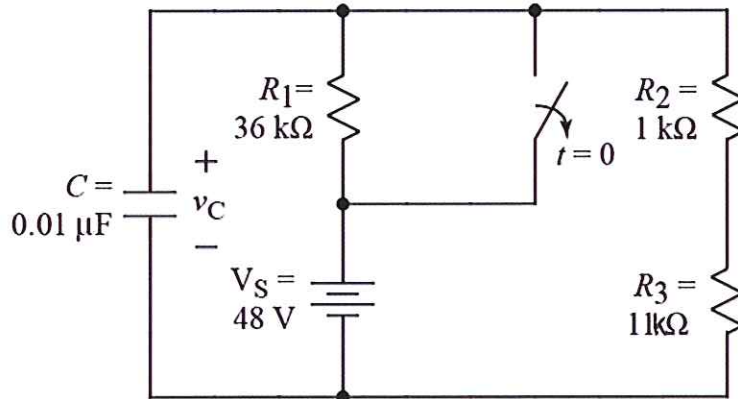



Ex:



The switch has been closed for a long time and is opened at $t = 0$.

Write the full expression for $v_C(t)$ for $t > 0$, including all the numerical constants that you find.

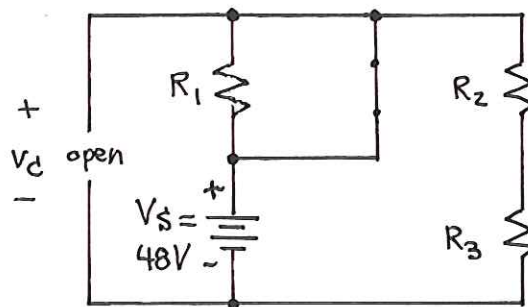
sol'n: For $t = 0^-$, the switch is closed and $C = \text{open}$.



If we follow wires from the 48V source, we find they are leading directly to the C. So $v_C(0^-) = V_S = 48\text{V}$, and $v_C(0^+) = v_C(0^-)$.

For $t \rightarrow \infty$, the switch is open and $C = \text{open}$.

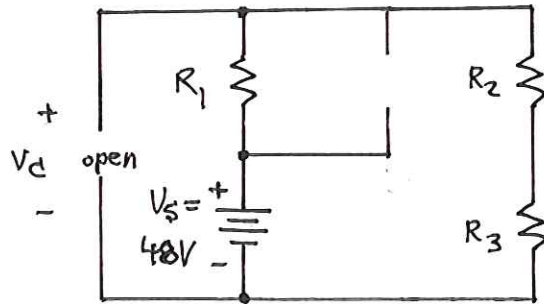We have a V -divider formed by V_S , R_1 , R_2 , and R_3 . $v_C = V$ across $R_2 + R_3$.



$$V_c(t \rightarrow \infty) = V_s \frac{R_2 + R_3}{R_1 + R_2 + R_3} = 48V \frac{1k\Omega + 11k\Omega}{36k\Omega + 1k\Omega + 11k\Omega}$$

or

$$V_c(t \rightarrow \infty) = 48V \frac{12k\Omega}{48k\Omega} = 12V$$

To find R_{Th} for time constant $\tau = R_{Th}C$, we look in from the terminals where C is connected and turn off V_s (= wire).

$$R_{Th} = R_1 \parallel (R_2 + R_3) = 36k\Omega \parallel (1k\Omega + 11k\Omega)$$

or

$$R_{Th} = 36k\Omega \parallel 12k\Omega = 12k\Omega \cdot 3 \parallel 1 = 12k\Omega \cdot \left(\frac{3}{4}\right)$$

or

$$R_{Th} = 9k\Omega \quad \text{and} \quad \tau = R_{Th}C = 9k\Omega \cdot 0.01\mu F$$

$$\tau = 90\mu s$$

We use the general form of solution for RC circuits:

$$V_c(t) = V_c(t \rightarrow \infty) + [V_c(0^+) - V_c(t \rightarrow \infty)]e^{-t/\tau}, \quad t > 0$$

or

$$V_c(t > 0) = 12V + [48V - 12V]e^{-t/90\mu s}$$

or

$$V_c(t > 0) = 12V + 36Ve^{-t/90\mu s}$$