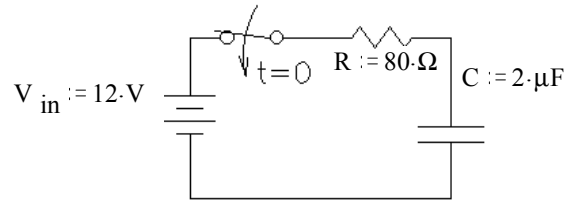


ECE 1250 homework # 8

1. A 10-microfarad capacitor has been charged to a potential of 150 volts. A resistor of 25Ω is then connected across the capacitor through a switch. When the switch has been closed for 10 time constants the total energy dissipated by the resistor is most nearly:

- (A) 1.0×10^{-7} joules (B) 1.1×10^{-1} joules (C) 9.0×10^1 joules (D) 9.0×10^3 joules


2. a) The switch is closed at time $t = 0$ and $v_C(0) = 0V$, find $v_C(t)$.



b) What is the value of the voltage across C at $t := 40\mu s$


3. The switch below has been in the upper position for a long time and is switched down at time $t = 0$.

At what time is $v_C = 4V$?

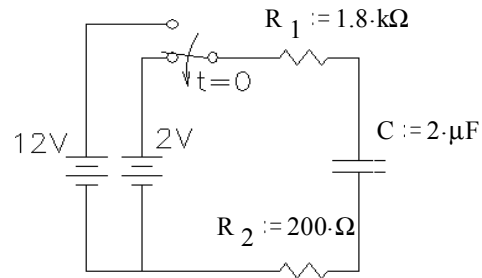


4. a) What is the time constant of this circuit?
Hint: Use a Thevenin equivalent circuit.

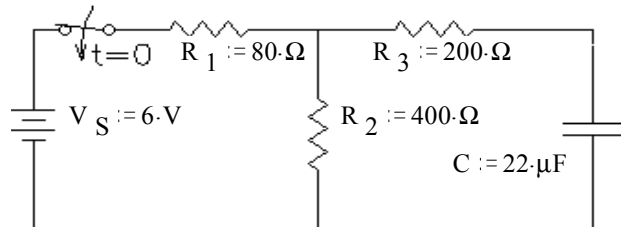b) What will be the final value of v_C ?
(After the switch has been closed for a long time)



5. The switch has been closed (making contact) for a long time and is opened (as shown) at time $t = 0$.

- a) Find the complete expression for $v_C(t)$.
- b) Find v_C at time $t = 2\tau$.
- c) At time $t = 2\tau$ the switch is closed again. Find the complete expression for $v_C(t')$ where t' starts at $t = 2\tau$.

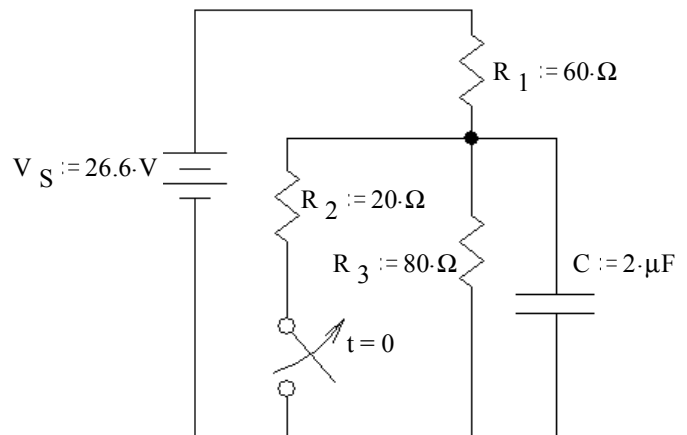

Answers 1. B 2.a) $12 \cdot V - 12 \cdot V \cdot e^{-\frac{t}{0.16 \cdot ms}}$ b) 2.65·V 3. 6.44·ms 4. a) 5.87·ms b) 5·V

5. a) $15.2 \cdot V - 9.6 \cdot V \cdot e^{-\frac{t}{68.6 \cdot \mu s}}$ b) 13.9·V c) $5.6 \cdot V + 8.3 \cdot V \cdot e^{-\frac{t}{25.3 \cdot \mu s}}$