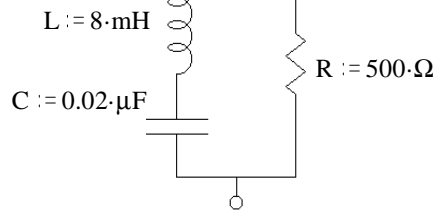


ECE 1250 homework # P2



a

1. Find Z_{eq} in simple polar form.

$f := 8000 \cdot \text{Hz}$



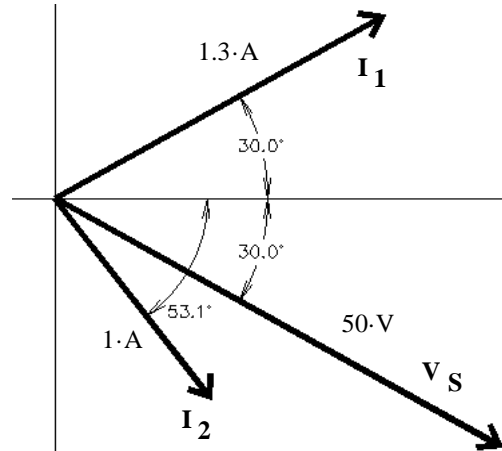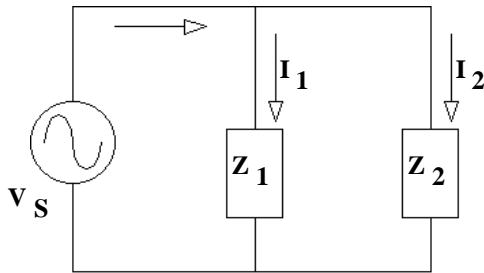2. The phasor diagram at right shows the source voltage and two branch currents of a parallel circuit. Find the impedance of each of the two branches.




3. a) Find the AC current source, I_{in} in polar form.


b) Find V_T .

c) Choose one:

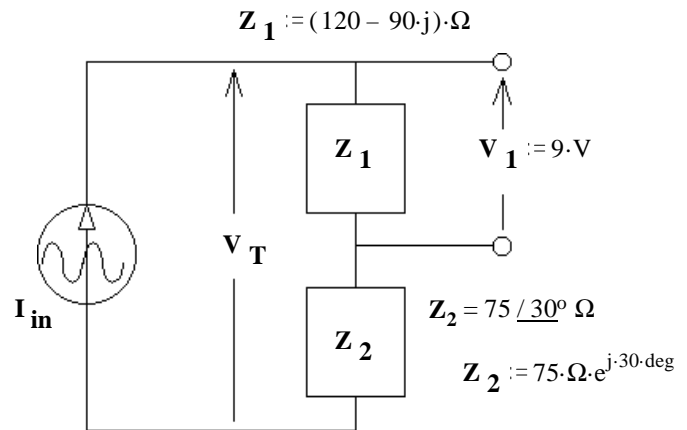- i) The source current leads the source voltage.
- ii) The source current lags the source voltage.



4. a) Find Z_1 .

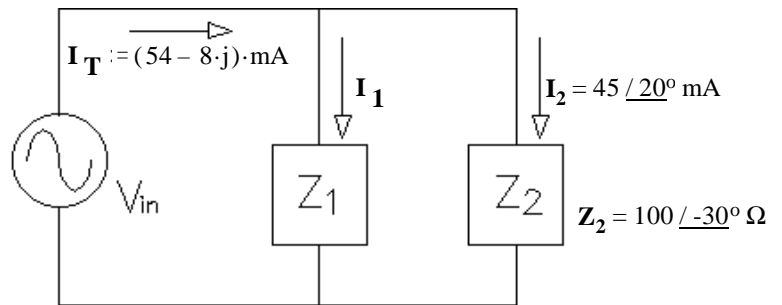

b) To make Z_1 in the simplest way, what part(s) would you need? Just determine the needed part(s) from the list below and state why you made that choice, don't find the values.


- | | | | | |
|-------------------|-------------------|----------|--------------|----------------|
| resistor | capacitor | inductor | power supply | current source |
| Thevenin resistor | Ideal transformer | | voltmeter | ammeter |
| | | | | scope |

c) Choose one: i) I_2 leads the source voltage (V_{in}) ii) I_2 lags the source voltage (V_{in})

d) Choose one: i) I_1 leads I_2 ii) I_1 lags I_2

ECE 1250 homework # P2 p.2

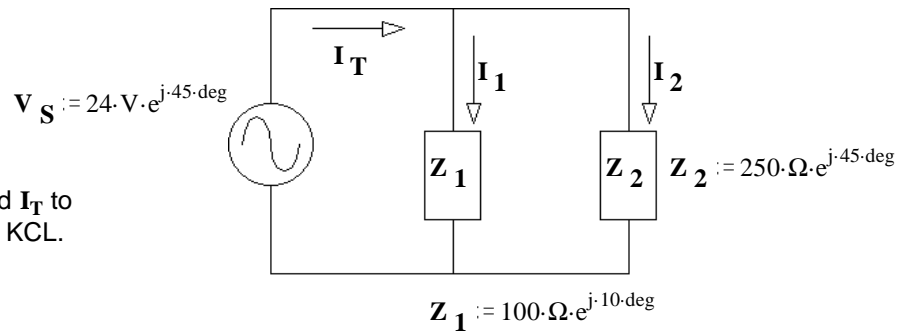
5. a) Find all the currents, I_1 , I_2 , and I_T .



b) Draw a phasor diagram showing I_1 , I_2 , and I_T to scale so that you can show that they obey KCL.


6. For the circuit shown, find the following:

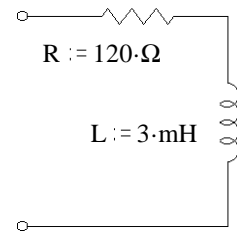- a) At what frequency would the magnitude of the total impedance be 240Ω ?
- b) At this frequency, what is the phase angle of the impedance?
- c) At this frequency, you want to add a capacitor in series to make the circuit appear purely resistive (the impedance has no imaginary component). Find the value of the capacitor.



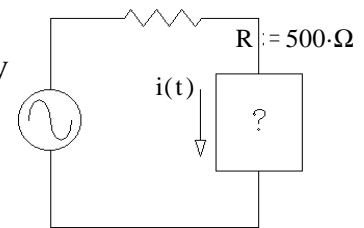7. You need to design a circuit in which the current $i(t)$ leads the voltage $v_S(t)$ by 36° of phase.

$$v_S(t) = 160 \cdot \cos(450 \cdot t) \cdot V$$



- a) What should go in the box: R, L, C?
- b) Find its value.

Answers

- 1. $382\Omega / -40.2^\circ$
- 2. $Z_1 = (19.2 - 33.3j) \cdot \Omega$ $Z_2 = (46.0 + 19.6j) \cdot \Omega$
- 3. a) $60 / 36.87^\circ$ mA b) $11.54 / 21^\circ$ V c) i)
- 4. a) $172 / 53.4^\circ$ Ω b) phase angle > 0 , resistor and inductor
c) i) d) ii)
- 5. a) $(0.197 + 0.138j) \cdot A + 0.096 \cdot A = 0.293 + 0.138j \cdot A$
- 6. a) 11·kHz b) 60° c) $0.0694 \cdot \mu F$
- 7. a) C b) $6.12 \cdot \mu F$

