

ECE 1250 Lecture 1 Electrical & Computer Engineering Design

Lab section issues & waiting lists

Talk about the syllabus.

Problem sessions _____



HW # 1 due Friday by 5:00 pm in a yet-to-be-determined locker

WARNING: HWs are often due on non-class days.


How to survive

1. Easiest way to get through school is to actually learn and try to retain what you are asked to learn. Even if you're too busy, don't lose your good study practices. What you "just get by" on today will cost you later.
Don't fall for the "I'll never need to know this" trap. Sure, much of what you learn you may not use, but you will need some of it, some day. Y you will need, either in the current class, or future classes, or maybe sometime in your career. Don't waste time second-guessing the curriculum, It'll still be easier to just do your best to learn and retain.
2. Don't fall for the "traps".
Homework answers, Problem session solutions, Posted solutions, Lecture notes.
3. KEEP UP! Use calendar.
4. Make "permanent notes" after you've finished a subject or section and feel that you know it.

Lecture


Basic electrical quantities	Letter used	Units	Fluid Analogy
Charge, actually moves	Q	Coulomb (C)	m ³
Current, like fluid flow	$I = \frac{Q}{\text{sec}}$	Amp (A, mA, μ A,...)	$\frac{\text{m}^3}{\text{sec}}$
Voltage, like pressure	V or E	volt (V, mV, kV,...)	$\text{Pa} = 1 \cdot \frac{\text{N}}{\text{m}^2}$
Resistance 	$R = \frac{V}{I}$	Ohm (Ω , k Ω , M Ω ,...)	
Conductance 	$G = \frac{1}{R}$	Siemens (S, also mho, old unit)	
Power = energy/time	$P = V \cdot I$	Watt (W, mW, kW, MW,...)	W

Symbols (ideal)






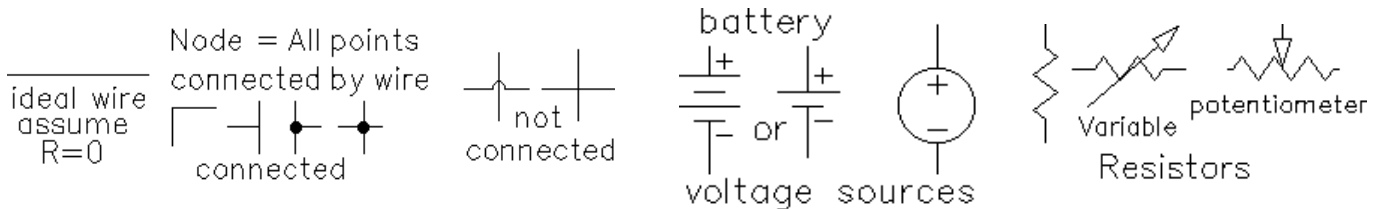


KCL, Kirchhoff's Current Law

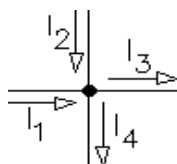$I_{\text{in}} = I_{\text{out}}$ of any point, part, or section



$$I_1 + I_2 = I_3 + I_4$$

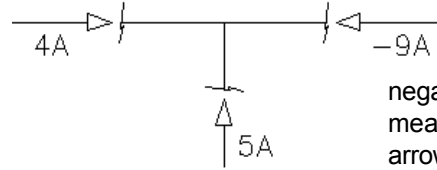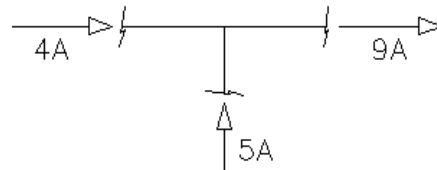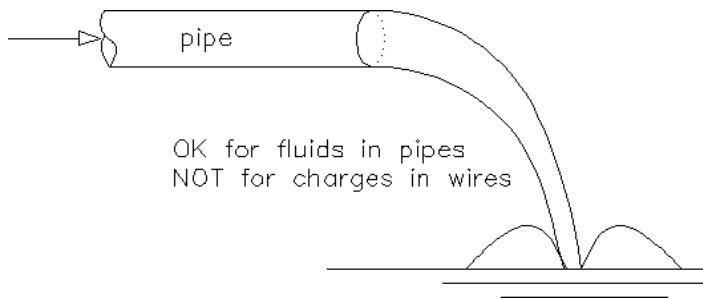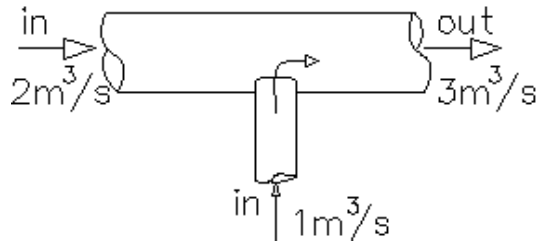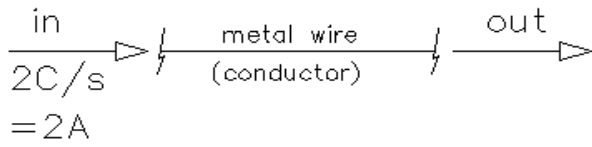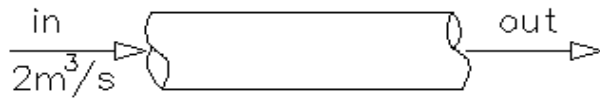

negative current means the direction arrow is wrong

Conductors

Nonconductors

Massless fluid in our analogy

No gravity effects

No Bernoulli effects



Reasonable because:

Electron mass is $9.11 \cdot 10^{-31} \cdot \text{kg}$

Electron charge is $-1.6 \cdot 10^{-16} \cdot \text{C}$

Negative charge flows in negative direction


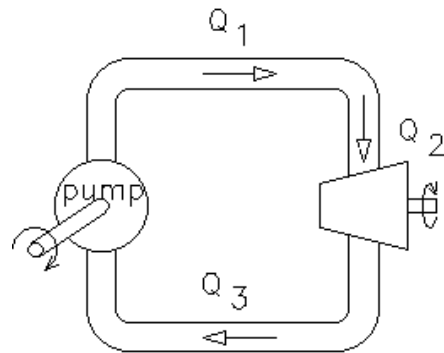
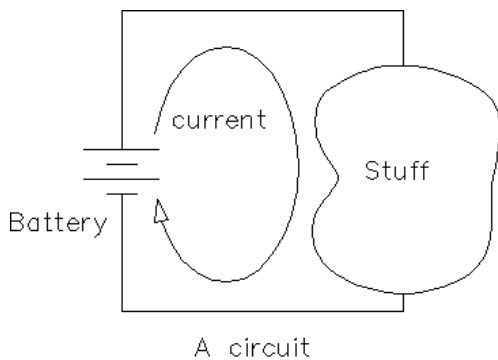
Battery also obeys KCL
No accumulation of charge anywhere,
so it must circulate around
Leads to the concept of a "Circuit"



Voltage is like pressure

KVL, Kirchhoff's Voltage Law

$$V_{\text{gains}} = V_{\text{drops}}$$

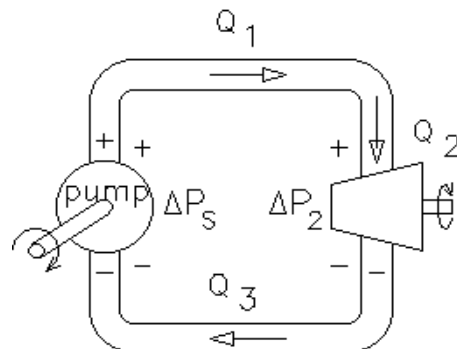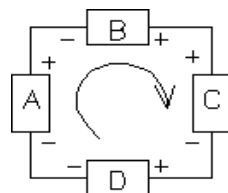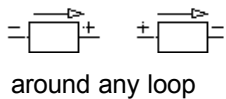

ECE 1250 Lecture 1 & 2 notes p3

First Class period usually ends here, pick up in next lecture


Handouts & Copy Center Packets

Labs Start -- Bring Notebook

Ideal elements

Batteries or voltage sources always the same voltage regardless of current

Wires have no resistance

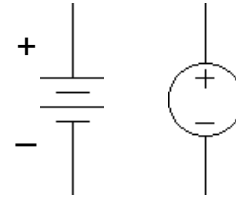

Resistors


Basic electrical quantities

		Unit
Resistance	$R = \frac{V}{I}$	Ohm (Ω , $k\Omega$, $M\Omega$,...)
Conductance	$G = \frac{1}{R}$	Siemens (S, also mho, old unit)
Power energy/time	$P = V \cdot I$	Watt (W, mW, kW, MW,...)

Resistors

Ohm's law

$$V = I \cdot R$$

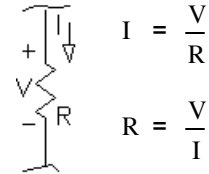

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

ideal

Resistors

series:

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

Exactly the **same current** through each resistor

Voltage divider:

$$V_{R_n} = V_{total} \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$


parallel:

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$



Exactly the **same voltage** across each resistor

current divider:
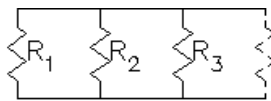
$$I_{R_n} = I_{total} \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$



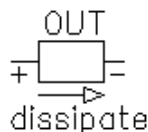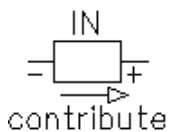Power $P_{IN} = P_{OUT}$ for resistor circuits



$$P = V \cdot I \text{ for everything}$$

$$= I^2 \cdot R = \frac{V^2}{R} \text{ for resistors}$$

DC Notes

ECE 1250 / 00


A.Stolp
2/8/00, rev 1/28/06

Basic electrical quantities

Unit


Charge, actually moves	Q	Coulomb (C)
Current, like fluid flow	$I = \frac{Q}{s}$	Amp (A, mA, μ A,...)
Voltage, like pressure	V	volt (V, mV, kV,...)
Resistance	$R = \frac{V}{I}$	Ohm (Ω , k Ω , M Ω ,...)
Conductance	$G = \frac{1}{R}$	Siemens (S, old unit mho)
Power energy/time	$P = V \cdot I$	Watt (W, mW, kW, MW,...)

Schematic symbols

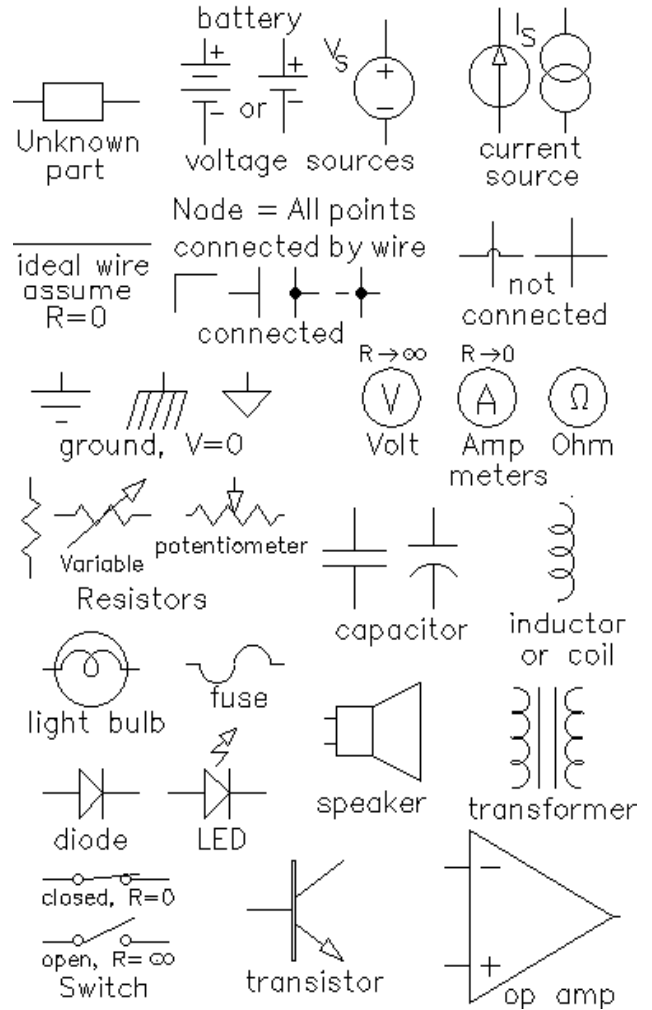



KCL, Kirchoff's Current Law

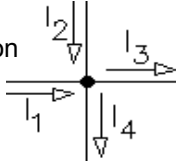$I_{in} = I_{out}$ of any point, part, or section




KVL, Kirchoff's Voltage Law

$V_{gains} = V_{drops}$ around any loop

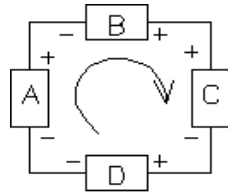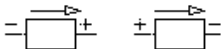


Node = all points connected by wire, all at same voltage (potential)

Ohm's law (resistors)

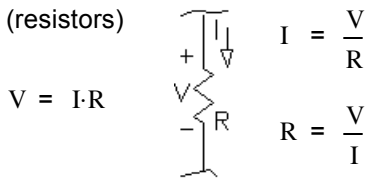

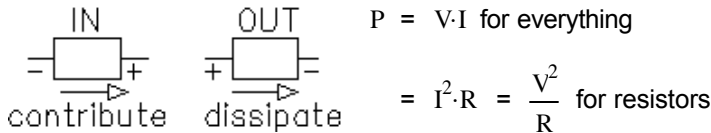Power $P_{IN} = P_{OUT}$ for resistor circuits



Maximum power transfer: $R_L = R_{Th}$
Load = Thevenin's


Resistors

series: $R_{eq} = R_1 + R_2 + R_3 + \dots$

Exactly the **same current** through each resistor

parallel: $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$

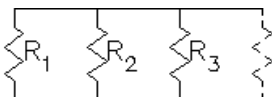Exactly the **same voltage** across each resistor



Voltage divider:

$$V_{Rn} = V_{total} \cdot \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$

current divider:

$$I_{Rn} = I_{total} \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

Multiple unknowns:

1. Combine resistors into equivalents where possible.
2. Use superposition if there are multiple sources and you know all the resistors.
3. Use KCL, KVL, & Ohm's laws to write multiple equations and solve.