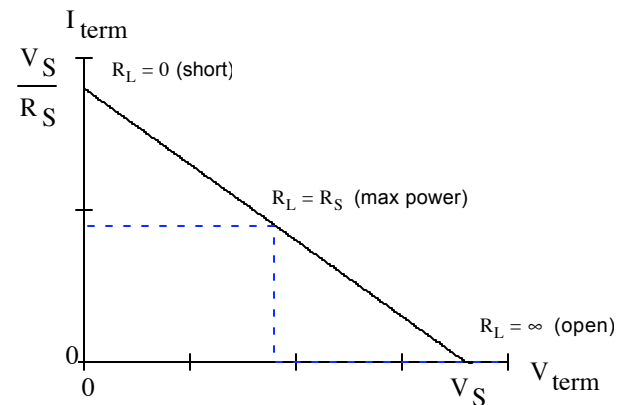
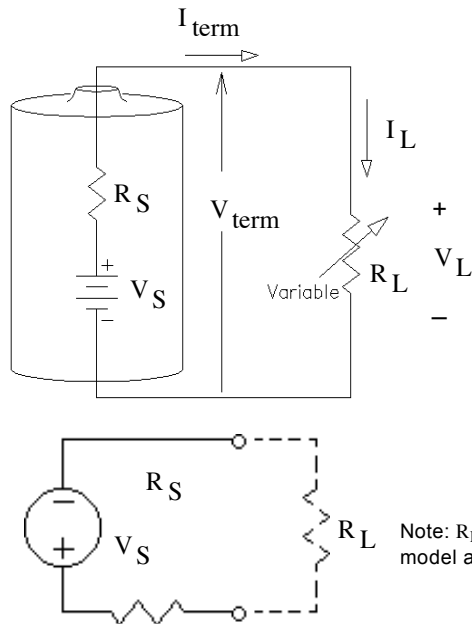
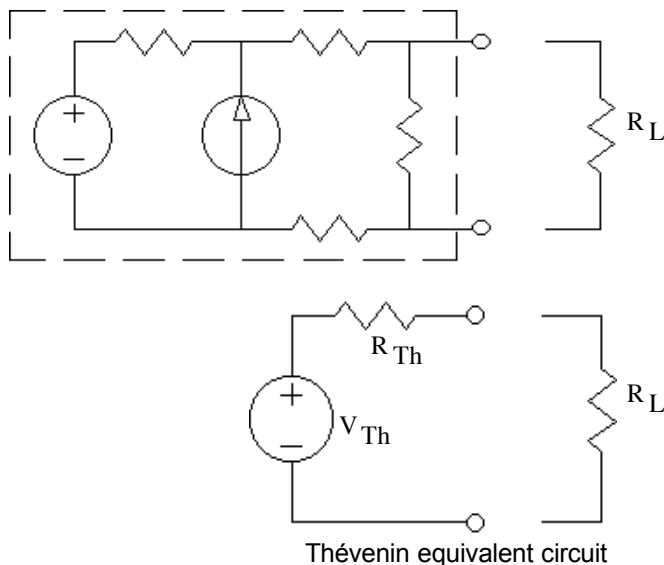


Model of a Real Source

Real sources are not ideal, but we will model them with two ideal components.




**Thévenin Equivalent Circuit**

The same model can be used for any combination of sources and resistors.

**Thévenin equivalent**

To calculate a circuit's Thévenin equivalent:

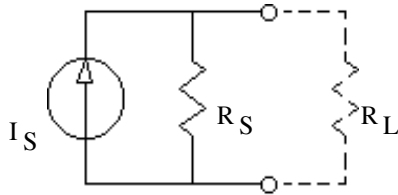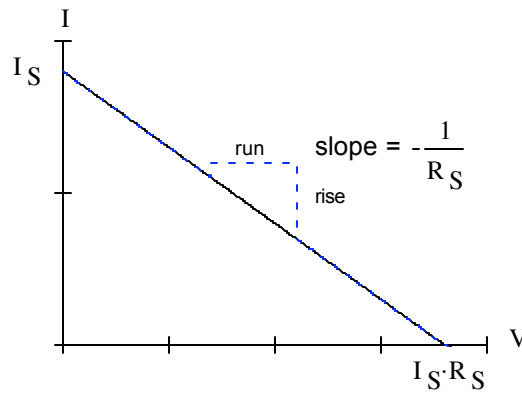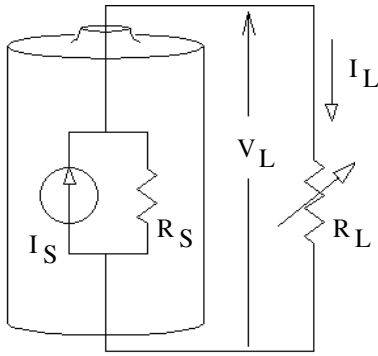- 1) Remove the load and calculate the open-circuit voltage where the load used to be.
This is the Thévenin voltage (V_{Th}).
- 2) Zero all the sources.
(To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals.
(DO NOT include the load in this resistance.) This is the Thévenin source resistance R_{Th} .
- 4) Draw the Thévenin equivalent circuit and add your values.




Note: R_L is not part of the Norton equivalent and does not need to be shown.

Norton equivalent

To calculate a circuit's Norton equivalent:

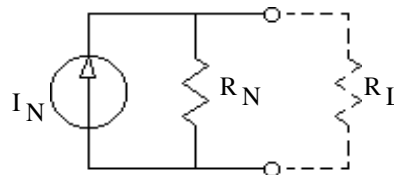- 1) Replace the load with a short (a wire) and calculate the short-circuit current in this wire.
This is the Norton current (I_N). Remove the short.
- 2) Zero all the sources.
(To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)
- 3) Compute the total resistance between the load terminals.
(DO NOT include the load in this resistance.) This is the Norton source resistance (R_N).
(Exactly the same as the Thévenin source resistance (R_{Th})).
- 4) Draw the Norton equivalent circuit and add your values.




OR (the more common way)...

- 1) Find the Thévenin equivalent circuit.
- 2) Convert to Norton circuit, then >>>


$$R_N = R_{Th}$$

and

$$I_N = \frac{V_{Th}}{R_{Th}}$$

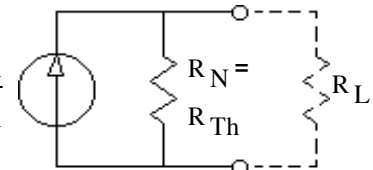

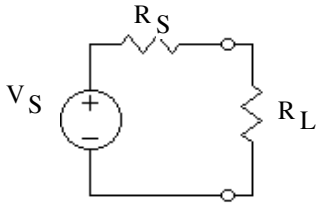Maximum power transfer If I wanted to maximize the power dissipated by the load, what R_L would I choose?



$$P_L = \frac{V_L^2}{R_L} = \left(\frac{R_L}{R_S + R_L} \cdot V_S \right)^2 \cdot \frac{1}{R_L} = \frac{R_L^2}{(R_S + R_L)^2} \cdot V_S^2 \cdot \frac{1}{R_L}$$

$$= \frac{R_L^2}{R_S^2 + 2 \cdot R_S \cdot R_L + R_L^2} \cdot V_S^2 \cdot \frac{1}{R_L} = \frac{R_L}{R_S^2 + 2 \cdot R_S \cdot R_L + R_L^2} \cdot V_S^2$$

$$= \frac{1}{\frac{R_S^2}{R_L} + 2 \cdot R_S + R_L} \cdot V_S^2$$


Next step would be to differentiate $\frac{d}{dR_L} P_L(R_L)$, set this equal to 0 and solve for R_L to find the maximum

Unfortunately this function is a pain to differentiate. What if we just differentiate the denominator and find its minimum, wouldn't that work just as well?

$$\frac{d}{dR_L} \left(\frac{R_S^2}{R_L} + 2 \cdot R_S + R_L \right) = -1 \cdot \frac{R_S^2}{R_L^2} + 0 + 1 = 0$$

Maximum power transfer happens when: $R_L = R_S$


Just what we saw in Example 1

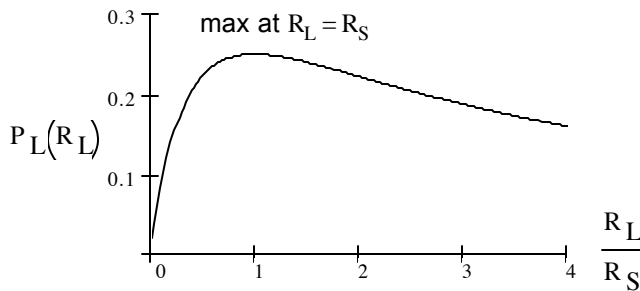

This is rarely important in power circuitry, where there should be plenty of power and R_S should be small. It is much more likely to be important in signal circuitry where the voltages can be very small and the source resistance may be significant -- say a microphone or a radio antenna.

What about efficiency?

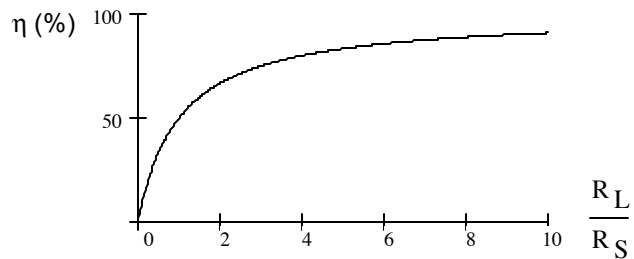
$$\frac{P_L(R_L)}{P_S(R_L)} = \frac{I^2 \cdot R_L}{I^2 \cdot (R_S + R_L)} = \frac{R_L}{R_S + R_L}$$




ECE 1250 Lecture 5 & 6 notes p4

Ex 1 A NiCad Battery pack is used to power a cell phone. When the phone is switched on the battery pack voltage drops from 4.80 V to 4.65 V and the cell phone draws 50 mA. $V_S := 4.80 \cdot V$ $V_{50} := 4.65 \cdot V$

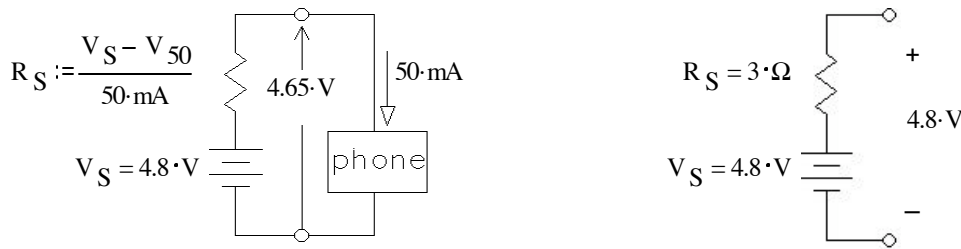
a) Draw a simple, reasonable model of the battery pack using ideal parts. Find the value of each part.



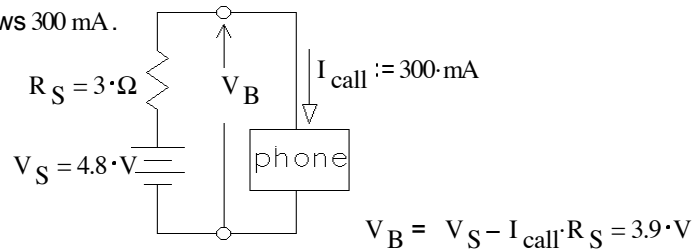b) The cell phone is used to make a call. Now it draws 300 mA. What is the battery pack voltage now?



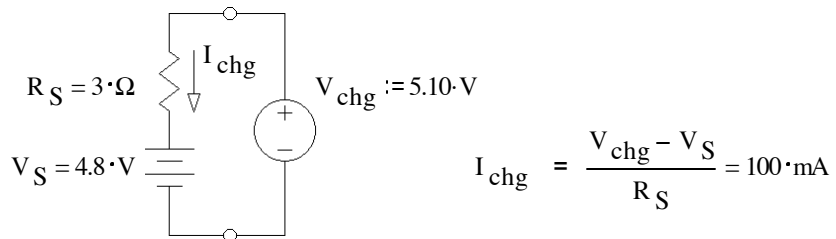c) The battery pack is placed in a charger. The charger supplies 5.10 V. How much current flows into the battery pack?




d) How much energy does the charger supply in 5 minutes?

$$5.10 \cdot V \cdot 100 \cdot \text{mA} \cdot 5 \cdot \text{min} \cdot \frac{60 \cdot \text{sec}}{1 \cdot \text{min}} = 153 \cdot \text{joule}$$

e) Is all this energy stored in the battery?


No, some is wasted as heat in R_S and more may be lost in the electrical-to-chemical transition.

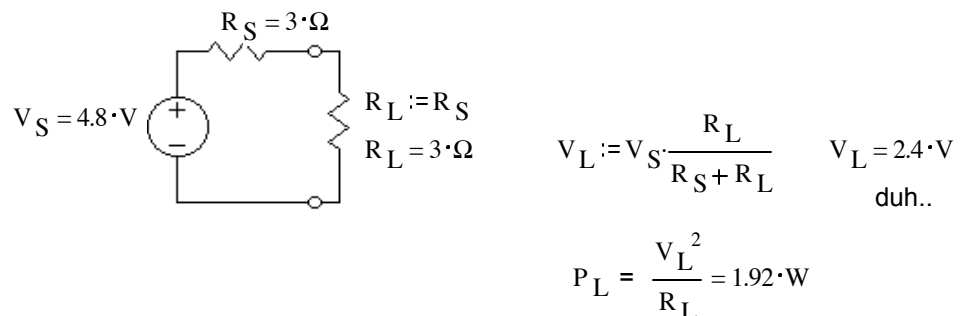f) This battery pack is hooked to a load resistor. What is the maximum power that this battery pack could supply to the load resistor, and what would be the value load resistor?




ECE 1250 Lecture 5 & 6 notes p5 Thévenin & Norton Examples

Ex 2 Find the Thévenin equivalent:

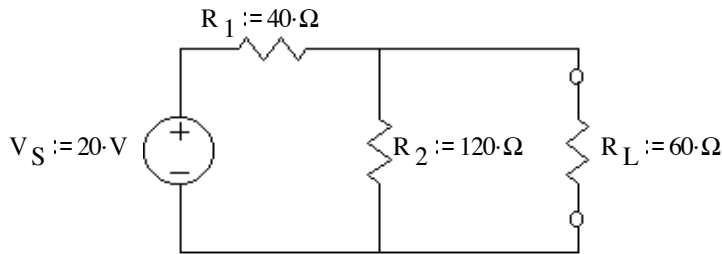


To calculate a circuit's Thévenin equivalent:

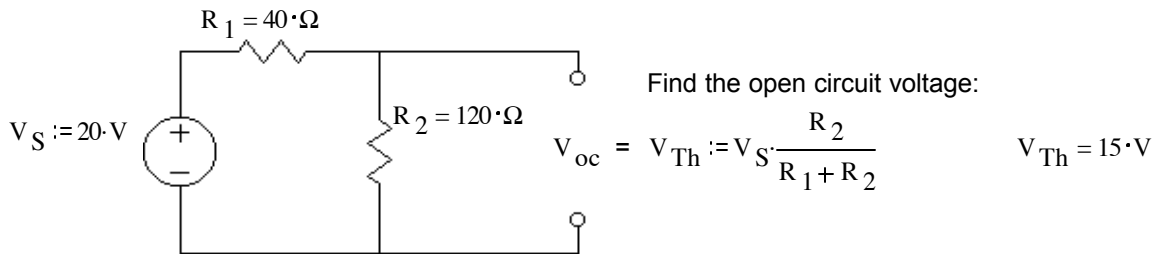- 1) Remove the load and calculate the open-circuit voltage where the load used to be. This is the Thévenin voltage (V_{Th}).




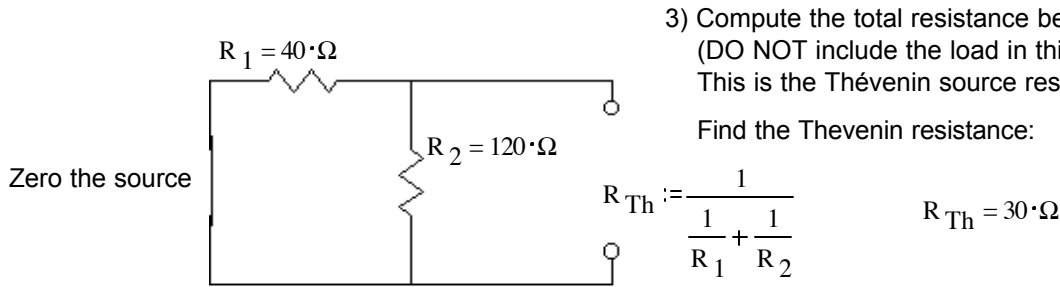- 2) Zero all the sources. (To zero a voltage source, replace it with a short. To zero a current source, replace it with an open.)




- 4) Draw the Thévenin equivalent circuit and add your values.


Thevenin equivalent circuit:

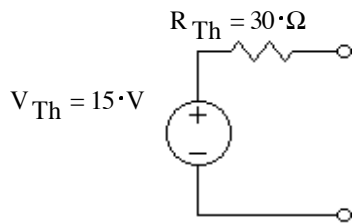


If the load were reconnected:

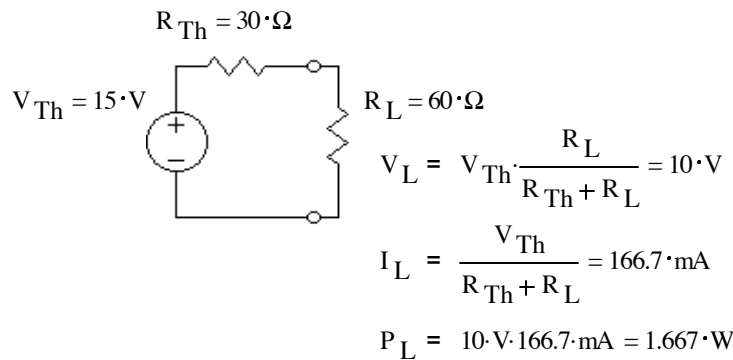

- b) Find the Norton equivalent circuit:

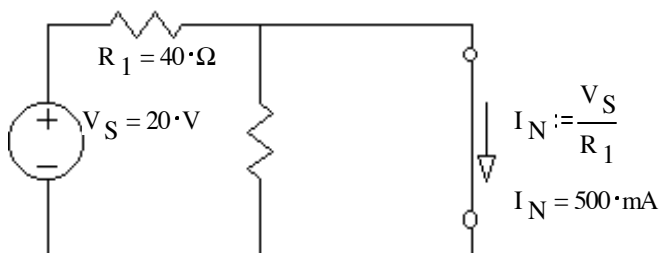

Norton equivalent circuit:

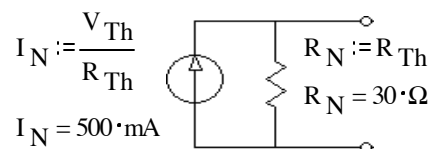

ECE 1250 Lecture 5 & 6 notes p6



c) Show that the Thévenin circuit is indeed equivalent to the original at several values of R_L .

	Original Circuit		Thévenin Circuit	
R_L	V_L	I_L	I_L	V_L
$R_L := 0 \cdot \Omega$	0 V	$\frac{V_S}{R_1} = 500 \cdot \text{mA}$	$\frac{V_{Th}}{R_{Th} + R_L} = 500 \cdot \text{mA}$	$500 \cdot \text{mA} \cdot 0 \cdot \Omega = 0 \cdot \text{V}$
Using either numbers: $P_L = V_L \cdot I_L = 0 \cdot \text{W}$				
$R_L := 10 \cdot \Omega$	$R_o := \frac{1}{\frac{1}{R_2} + \frac{1}{R_L}}$	$R_o = 9.231 \cdot \Omega$	$I_L := \frac{V_{Th}}{R_{Th} + R_L}$	$V_L := I_L \cdot R_L$
	$V_L = V_S \cdot \frac{R_o}{R_1 + R_o} = 3.75 \cdot \text{V}$		$I_L = 375 \cdot \text{mA}$	$V_L = 3.75 \cdot \text{V}$
		$I_L = \frac{V_L}{R_L} = 375 \cdot \text{mA}$	Using either numbers: $P_L = V_L \cdot I_L = 1.406 \cdot \text{W}$	


Repeat these calculations for a number of load resistors

$R_{L_i} :=$	R_{o_i}	$V_L = \frac{V_S \cdot R_{o_i}}{R_1 + R_{o_i}}$	$I_L = \frac{V_{L_i}}{R_{L_i}}$	$I_L = \frac{V_{Th}}{R_{Th} + R_{L_i}}$	$V_L = \frac{I_{L_i} \cdot R_{L_i}}{}$	$P_{L_i} = \frac{P_{L_i}}{}$
	Ω	V	mA	mA	V	W
0·Ω	0	0	0	500	0	0
1·Ω	0.992	0.484	483.871	483.871	0.484	0.234
10·Ω	9.231	3.75	375	375	3.75	1.406
20·Ω	17.143	6	300	300	6	1.8
30·Ω	24	7.5	250	250	7.5	1.875 max
40·Ω	30	8.571	214.286	214.286	8.571	1.837
60·Ω	40	10	166.667	166.667	10	1.667
120·Ω	60	12	100	100	12	1.2
240·Ω	80	13.333	55.556	55.556	13.333	0.741
∞·Ω	120	15	0	0	15	0


Plots

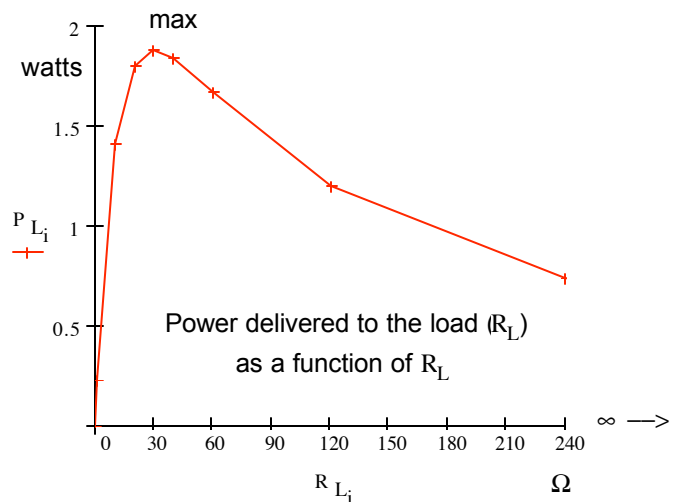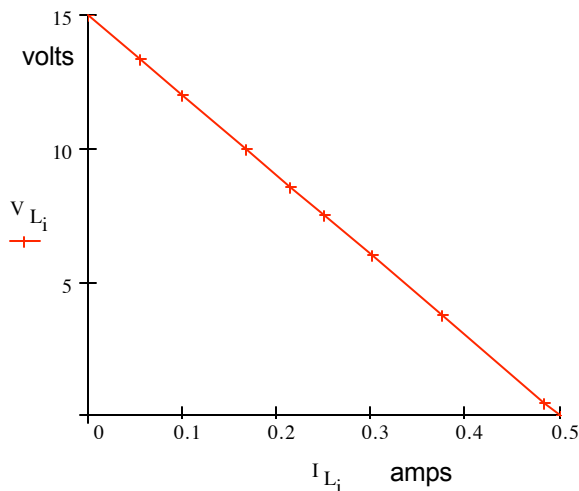

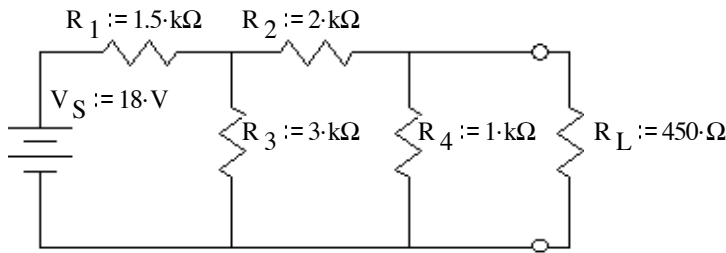
Ex 3 a) Find and draw the Thévenin equivalent circuit.



Find the open circuit voltage:

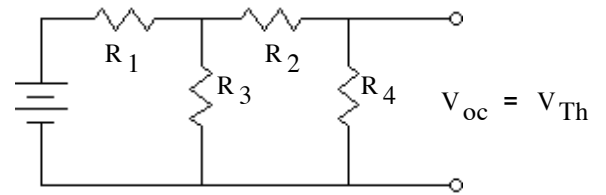

First do some simplification:

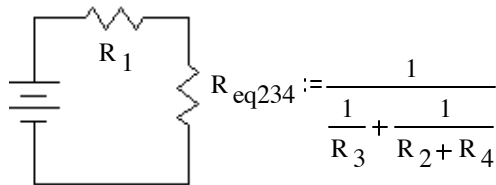


$$R_{eq234} := \frac{1}{\frac{1}{R_3} + \frac{1}{R_2 + R_4}}$$

$$R_{eq234} = 1.5 \cdot k\Omega$$

$$V_{234} := \frac{R_{eq234}}{R_1 + R_{eq234}} \cdot V_S$$

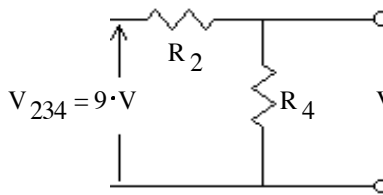
Divide this voltage between R_2 and R_4 :



$$V_{Th} := \frac{R_4}{R_2 + R_4} \cdot V_{234}$$

$$V_{Th} = 3 \cdot V$$


Find the Thévenin resistance:

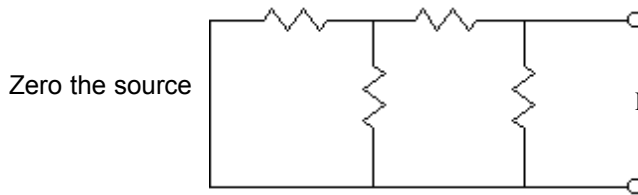

$$R_{Th} := \frac{1}{\frac{1}{R_4} + \frac{1}{R_2 + \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_3}}\right)}}$$

$$R_{Th} = 750 \cdot \Omega$$

Thévenin equivalent circuit:

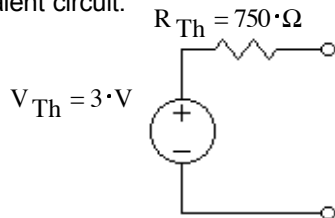

If the load were reconnected:


$$V_L := V_{Th} \cdot \frac{R_L}{R_{Th} + R_L} \quad V_L = 1.125 \cdot V$$

$$I_L := \frac{V_{Th}}{R_{Th} + R_L} \quad I_L = 2.5 \cdot mA$$

b) What value of R_L would result in the maximum power delivery to R_L ?

$$\text{For maximum power transfer} \quad R_L = R_{Th} = 750 \cdot \Omega$$

c) What is the maximum power transfer?


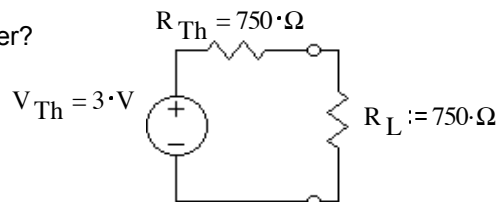


$$V_L := \frac{V_{Th}}{2}$$

$$P_L = \frac{V_L^2}{R_L} = 3 \cdot mW$$

ECE 1250 Lecture 5 & 6 notes p8

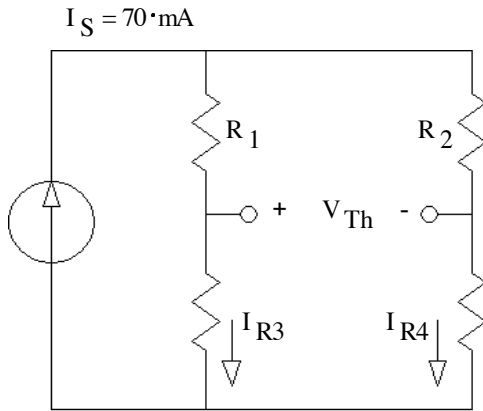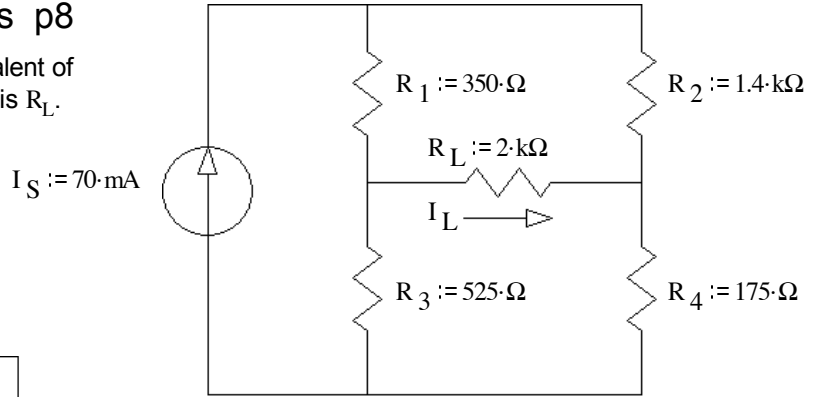
Ex 3 a) Find and draw the Thévenin equivalent of the circuit shown. The load resistor is R_L .




$$I_{R3} := I_S \cdot \frac{\frac{1}{R_1 + R_3}}{\frac{1}{R_1 + R_3} + \frac{1}{R_2 + R_4}} \quad I_{R3} = 45 \text{ mA}$$

$$I_{R4} := I_S - I_{R3} \quad I_{R4} = 25 \text{ mA}$$

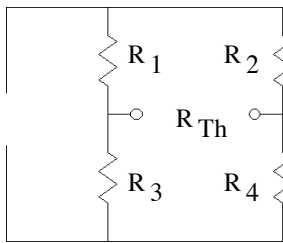
$$V_{Th} := I_{R3} \cdot R_3 - I_{R4} \cdot R_4$$


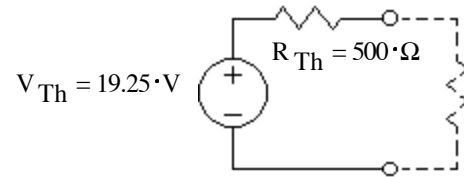
$$R_{Th} := \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4}}$$



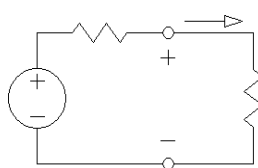
b) Find the load current using your Thévenin equivalent circuit.




$$I_L := \frac{V_{Th}}{R_L + R_{Th}} \quad I_L = 7.7 \text{ mA}$$

b) Find and draw the Norton equivalent circuit.

$$I_N := \frac{V_{Th}}{R_{Th}}$$

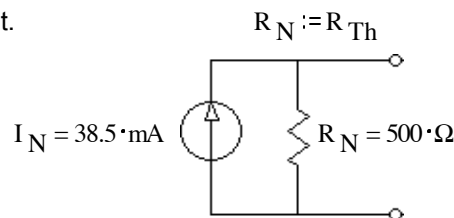

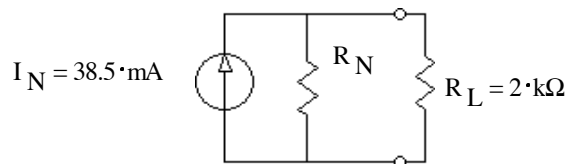c) Use your Norton equivalent circuit to find the current through the load.



$$I_L := \frac{\frac{1}{R_L}}{\left(\frac{1}{R_N} + \frac{1}{R_L}\right)} \cdot I_N$$

$$I_L = 7.7 \text{ mA} \quad \text{same as above}$$

$$V_L := I_L \cdot R_L$$

$$V_L = 15.4 \text{ V}$$