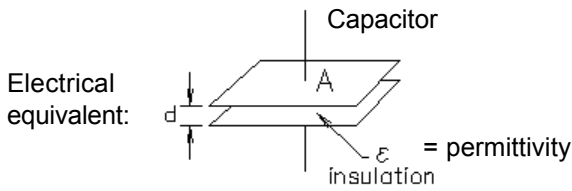


# ECE 1250 Capacitor Lecture Notes

Now that we have voltages and currents which can be functions of time, it's time to introduce the capacitor.



$$C = \epsilon \cdot \frac{A}{d} = \frac{Q}{V} = \frac{dq}{dv}$$


Units: farad =  $\frac{\text{coul}}{\text{volt}} = \frac{\text{amp} \cdot \text{sec}}{\text{volt}}$

$\mu\text{F} = 1 \cdot 10^{-6} \cdot \text{farad}$

$\text{pF} = 1 \cdot 10^{-12} \cdot \text{farad}$

For drawings of capacitors and info about tolerances, see Ch.3 of textbook.

Fluid Model:

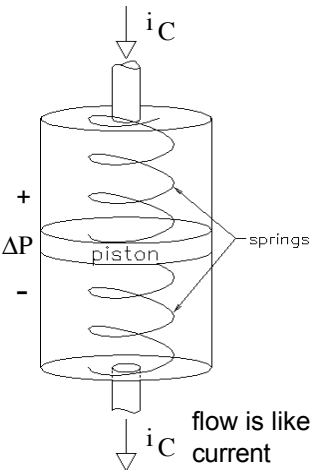

Basic equations you should know:

$$C = \frac{Q}{V}$$

$$v_C = \frac{1}{C} \int_{-\infty}^t i_C dt = \frac{1}{C} (\text{the accumulation of current})$$

/ initial voltage


Or...  $v_C = \frac{1}{C} \int_0^t i_C dt + v_C(0)$

Or...  $\Delta v_C = \frac{1}{C} \int_{t_1}^{t_2} i_C dt$


Energy stored in electric field:  $W_C = \frac{1}{2} \cdot C \cdot V_C^2$

Capacitor voltage **cannot** change instantaneously

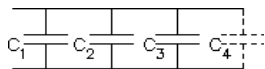**parallel:**  $C_{eq} = C_1 + C_2 + C_3 + \dots$



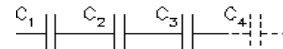**series:**  $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



Capacitors are the only "backwards" components.


## Sinusoids

$$i_C(t) = I_p \cdot \cos(\omega t)$$

$$v_C(t) = \frac{1}{C} \int i_C dt = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \sin(\omega t) = \frac{1}{C} \cdot \frac{1}{\omega} \cdot I_p \cdot \cos(\omega t - 90\text{-deg})$$


indefinite integral       $\sqrt{V_p}$        $\sqrt{V_p}$

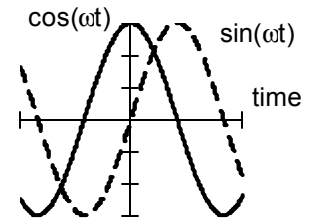Voltage "lags" current, makes sense, current has to flow in first to charge capacitor.


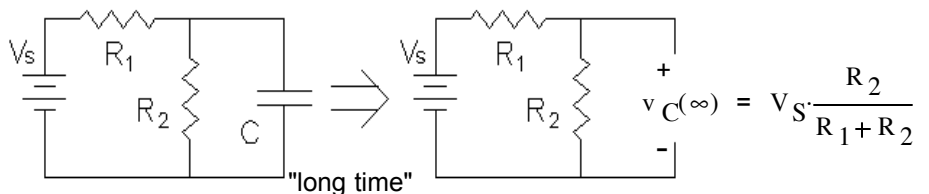
## Steady-state or Final conditions

If a circuit has been connected for "a long time", then it has reached a steady state condition. that means the currents and voltages are no longer changing.



$$\frac{d}{dt} v_C = 0 \quad i_C = C \cdot \frac{d}{dt} v_C = 0$$

no current means it looks like an open


**Example**

The voltage across a 0.5 μF capacitor is shown below. Make an accurate drawing of the capacitor current. Label the y-axis of your graph (I've already done the time-axis).

The accuracy of your plot at 0, 2, 6, and 8 ms is important, so calculate those values and plot or label them carefully. Between those points your plot must simply be the correct shape.


C := 0.5·μF

The curve is 2<sup>nd</sup> order

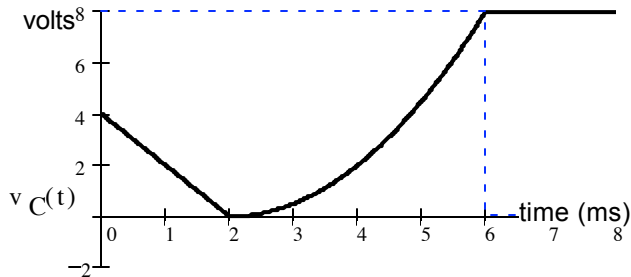

1 - 2ms:  $i_C = C \cdot \frac{\Delta V}{\Delta t} = 0.5 \cdot \mu\text{F} \cdot \frac{-4\text{V}}{2\text{ms}} = -1 \text{ mA}$

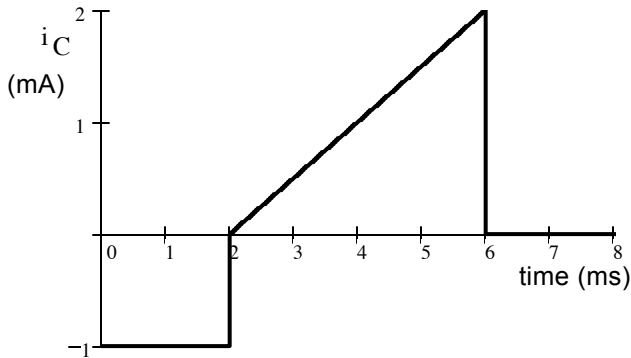2ms - 6ms: Initial slope is zero and the final slope is positive, so the current must be a triangle that starts at zero and ends at some height.



$$\Delta v_C(t) = \frac{1}{C} \int_0^t i_C(t) dt$$

$$8 \cdot \text{V} = \frac{1}{C} \left( \frac{4 \cdot \text{ms} \cdot \text{height}}{2} \right)$$

$$\text{height} = 8 \cdot \text{V} \cdot \frac{C \cdot 2}{4 \text{ ms}} = 2 \cdot \text{mA}$$

6ms - 8ms: Slope is zero, so the current must be zero.

**RC first-order transient circuits**

For all first order transients:  $v_X(t) = v_X(\infty) + (v_X(0) - v_X(\infty)) \cdot e^{-\frac{t}{\tau}}$        $i_X(t) = i_X(\infty) + (i_X(0) - i_X(\infty)) \cdot e^{-\frac{t}{\tau}}$

**Find the initial condition**  $v_X(0)$  or  $i_X(0)$



Find the capacitor voltage just before time  $t=0$ ,  $v_C(0^-)$ . This will be the same just after  $t=0$ ,  $v_C(0^+)$ . The capacitor voltage cannot change instantly. (If the initial condition is zero then the capacitor will look like a short just after  $t=0$ .) Use normal circuit analysis to find your desired variable:  $v_X(0)$  or  $i_X(0)$

**Find the final condition** ("steady-state" or "forced" solution)


Capacitors are opens. Solve by DC analysis to find  $v_X(\infty)$  or  $i_X(\infty)$

**RC Time constant** =  $\tau = R_{Th} \cdot C$

Sample circuit

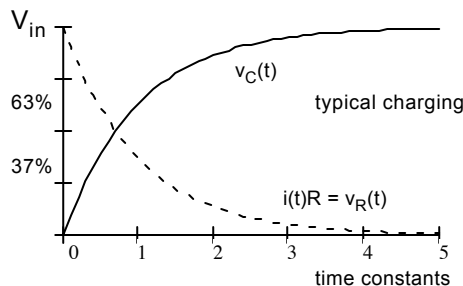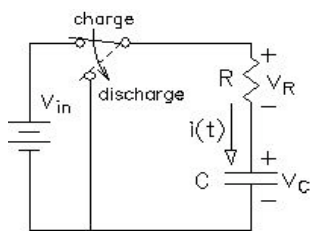


**Curves**

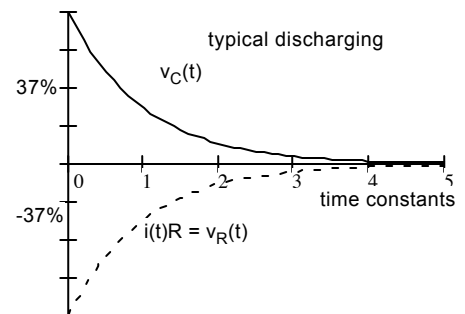

# ECE 1250 Inductor Lecture Notes

Fluid Model:

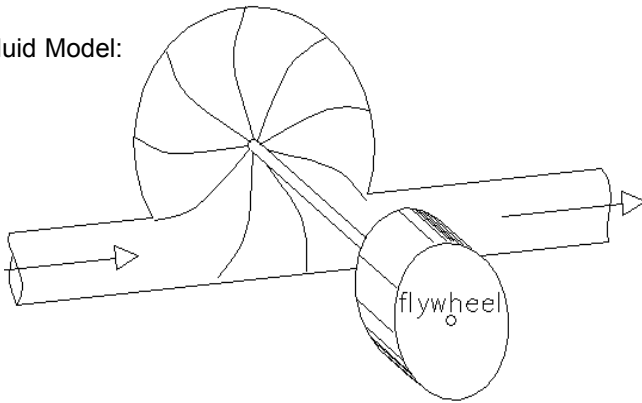

Basic equations you should know:

$$v_L = L \frac{d}{dt} i_L$$

Energy stored in electric field:  $W_L = \frac{1}{2} \cdot L \cdot I_L^2$


Inductor current **cannot** change instantaneously

Units: henry =  $\frac{\text{volt} \cdot \text{sec}}{\text{amp}}$

$$\text{mH} = 10^{-3} \cdot \text{H} \quad \mu\text{H} = 10^{-6} \cdot \text{H}$$


series:

$$L_{eq} = L_1 + L_2 + L_3 + \dots$$

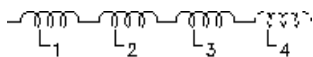

parallel:
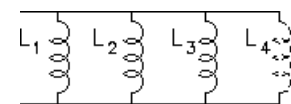
$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$$




Sinusoids

$$i_L(t) = I_p \cdot \cos(\omega t)$$


$$v_L(t) = L \frac{d}{dt} i_L = L \omega (-I_p \sin(\omega t)) = L \omega I_p \cos(\omega t + 90 \text{ deg})$$

$\underbrace{\quad}_{V_p}$ 
 $\underbrace{\quad}_{V_p}$

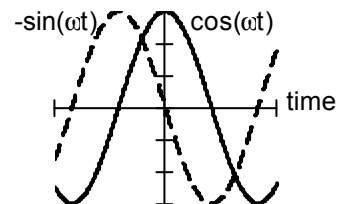Voltage "leads" current, makes sense, voltage has to present to make current change, so voltage comes first.



Electrical equivalent:

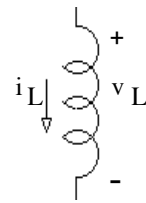

$$L = \mu_o \cdot N^2 \cdot K$$

$\mu$  is the permeability of the inductor core

$K$  is a constant which depends on the inductor geometry

$N$  is the number of turns of wire

$$i_L = \frac{1}{L} \int_{-\infty}^t v_L dt$$

$$\text{Or... } i_L = \frac{1}{L} \int_0^t v_L dt + i_L(0)$$

/ initial current

$$\text{Or... } \Delta i_L = \frac{1}{L} \int_{t_1}^{t_2} v_L dt$$