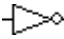
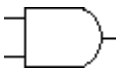

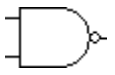
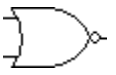


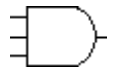

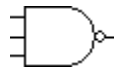



Logic Gates

NOT 

A	\bar{A}
0	1
1	0

A	B	AND  A · B	OR  A + B	NAND  $\overline{(A \cdot B)}$	NOR  $\overline{(A + B)}$	XOR  A ⊕ B	XNOR  A ⊙ B
0	0	0	0	1	1	0	1
0	1	0	1	1	0	1	0
1	0	0	1	1	0	1	0
1	1	1	1	0	0	0	1

A	B	C	AND  A · B · C	OR  A + B + C	NAND  $\overline{(A \cdot B \cdot C)}$	NOR  $\overline{(A + B + C)}$
0	0	0	0	0	1	1
0	0	1	0	1	1	0
0	1	0	0	1	1	0
0	1	1	0	1	1	0
1	0	0	0	1	1	0
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	0	0

etc..

Logic Identities of Boolean Algebra

(There are more, but they're the same as normal algebra)

$A \cdot 1 = A$ $A + 0 = A$
 $A \cdot 0 = 0$ $A + 1 = 1$ (1st that's not like normal)
 $A \cdot A = A$ $A + A = A$
 $A \cdot \bar{A} = 0$ $A + \bar{A} = 1$

$A \oplus B = \bar{A} \cdot \bar{B} + A \cdot B$
 $\overline{A \oplus B} = A \odot B = A \cdot \bar{B} + \bar{A} \cdot B$

$A + A \cdot B = A$
 $A + \bar{A} \cdot B = A + B$

DeMorgan's Theorem

