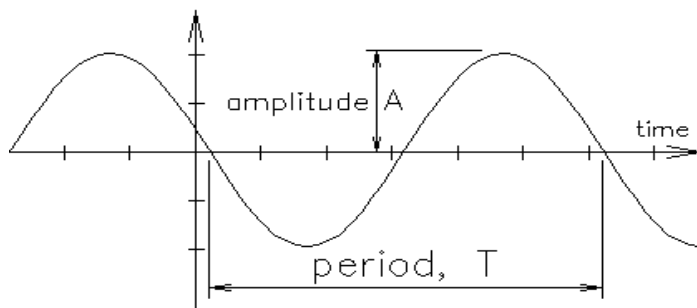


Phasor analysis with impedances, For steady-state sinusoidal response ONLY

Sinusoidal AC



T = Period = repeat time

f = frequency, cycles / second $f = \frac{1}{T} = \frac{\omega}{2\pi}$


ω = radian frequency, radians/sec $\omega = 2\pi \cdot f$

A = amplitude

Phase: $\phi = -\frac{\Delta t}{T} \cdot 360 \cdot \text{deg}$

or: $\phi = -\frac{\Delta t}{T} \cdot 2\pi \cdot \text{rad}$

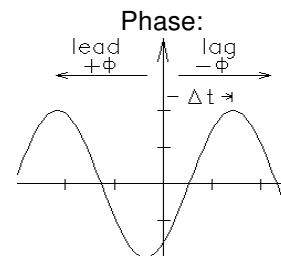$y(t) = A \cdot \cos(\omega \cdot t + \theta)$



Phasor analysis The math is all based on the Euler's equation

Euler's equation $e^{j\alpha} = \cos(\alpha) + j \cdot \sin(\alpha)$


$\cos(\alpha) = \frac{e^{j\alpha} + e^{-j\alpha}}{2}$

OR:

$\sin(\theta) = \frac{e^{j\alpha} - e^{-j\alpha}}{2 \cdot j}$

$e^{j(\omega \cdot t + \theta)} = \cos(\omega \cdot t + \theta) + j \cdot \sin(\omega \cdot t + \theta)$

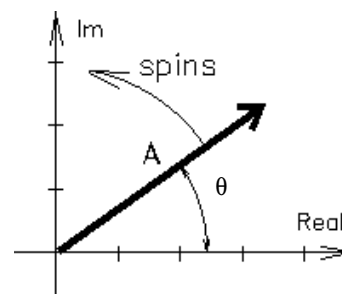$\text{Re}[e^{j(\omega \cdot t + \theta)}] = \cos(\omega \cdot t + \theta)$



If we freeze this at time $t=0$, then we can represent $\cos(\omega \cdot t + \theta)$ by $e^{j\theta}$ That's the phasor

Phasor

voltage: $v(t) = V_p \cdot \cos(\omega \cdot t + \phi)$ $V(\omega) = V_p \cdot e^{j\phi}$

current: $i(t) = I_p \cdot \cos(\omega \cdot t + \phi)$ $I(\omega) = I_p \cdot e^{j\phi}$

Phasors are drawn on a complex plane.

Phasors are used for adding and subtracting sinusoidal waveforms.

Ex1. Add the sinusoidal voltages $v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30 \cdot \text{deg})$

and $v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15 \cdot \text{deg})$

using phasor notation, draw a phasor diagram of the three phasors, then convert back to time domain form.

$v_1(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30 \cdot \text{deg})$

$V_1(\omega) = 4.5V \angle -30^\circ$ or: $V_1(\omega) = 4.5 \cdot V \cdot e^{-j30 \cdot \text{deg}}$

and



$v_2(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15 \cdot \text{deg})$

$V_2(\omega) = 3.2V \angle 15^\circ$ or: $V_2(\omega) = 3.2 \cdot V \cdot e^{j15 \cdot \text{deg}}$

I'm going to drop the (ω) notation from the phasor notation, it gets cumbersome, but remember that phasors are in the frequency domain..

$V_1 = 4.5V \angle -30^\circ$ or: $V_1 := 4.5 \cdot V \cdot e^{-j30 \cdot \text{deg}}$

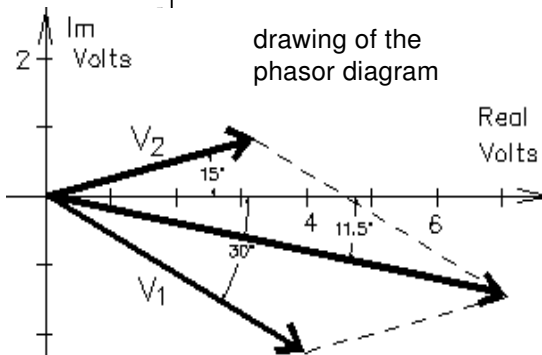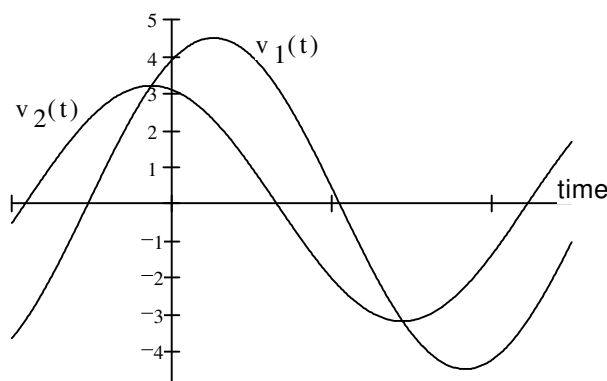$V_2 = 3.2V \angle 15^\circ$ or: $V_2 := 3.2 \cdot V \cdot e^{j15 \cdot \text{deg}}$



Intro to Phasors p2

Add like vectors, first change to the rectangular form

$$\begin{array}{llll}
 \mathbf{V}_1 = 4.5\text{V} \angle -30^\circ & 4.5 \cdot \text{V} \cdot \cos(-30 \cdot \text{deg}) = 3.897 \cdot \text{V} & 4.5 \cdot \text{V} \cdot \sin(-30 \cdot \text{deg}) = -2.25 \cdot \text{V} & \mathbf{V}_1 = 3.897 - 2.25j \cdot \text{V} \\
 \mathbf{V}_2 = 3.2\text{V} \angle 15^\circ & 3.2 \cdot \text{V} \cdot \cos(15 \cdot \text{deg}) = 3.091 \cdot \text{V} & 3.2 \cdot \text{V} \cdot \sin(15 \cdot \text{deg}) = 0.828 \cdot \text{V} & \mathbf{V}_2 = 3.091 + 0.828j \cdot \text{V} \\
 & \text{Add real parts: } 3.897 + 3.091 = 6.988 & & \mathbf{V}_3 := \mathbf{V}_1 + \mathbf{V}_2 \\
 & \text{Add imaginary parts: } -2.25 + 0.828 = -1.422 & & \mathbf{V}_3 = 6.988 - 1.422j \cdot \text{V} \quad \text{sum}
 \end{array}$$

Change \mathbf{V}_3 back to polar coordinates:

$$\sqrt{6.988^2 + 1.422^2} = 7.131 \quad \text{atan}\left(\frac{-1.422}{6.988}\right) = -11.502 \cdot \text{deg}$$

OR, in Mathcad notation (you' ll see these in future solutions):

$$|\mathbf{V}_3| = 7.131 \cdot \text{V} \quad \arg(\mathbf{V}_3) = -11.5 \cdot \text{deg}$$

Change \mathbf{V}_3 back to the time domain:

$$v_3(t) = v_1(t) + v_2(t) = 7.13 \cdot \cos(\omega t - 11.5 \cdot \text{deg}) \cdot \text{V}$$

Ex 2. Two sinusoidal voltages: $v_1(t) = 5 \cdot \text{V} \cdot \cos(\omega t + 36.87 \cdot \text{deg})$ and $v_2(t) = 3.162 \cdot \text{V} \cdot \cos(\omega t - 18.44 \cdot \text{deg})$

a) using phasor notation, find $v_3 = v_1 - v_2$

$$\mathbf{V}_1 := 5 \cdot \text{V} \cdot e^{j(36.87 \cdot \text{deg})} \quad \begin{array}{l} 5 \cdot \text{V} \cdot \cos(36.87 \cdot \text{deg}) = 4 \cdot \text{V} \\ 5 \cdot \text{V} \cdot \sin(36.87 \cdot \text{deg}) = 3 \cdot \text{V} \end{array}$$

$$\mathbf{V}_1 = 4 + 3j \cdot \text{V}$$

$$\mathbf{V}_2 := 3.162 \cdot \text{V} \cdot e^{j(-18.44 \cdot \text{deg})} \quad \begin{array}{l} 3.162 \cdot \text{V} \cdot \cos(-18.44 \cdot \text{deg}) = 3 \cdot \text{V} \\ 3.162 \cdot \text{V} \cdot \sin(-18.44 \cdot \text{deg}) = -1 \cdot \text{V} \end{array}$$

$$\mathbf{V}_2 = 3 - j \cdot \text{V}$$

Subtract real parts: $4 \cdot \text{V} - 3 \cdot \text{V} = 1 \cdot \text{V}$

Subtract imaginary parts: $3 \cdot \text{V} - (-1 \cdot \text{V}) = 4 \cdot \text{V}$

$$\mathbf{V}_3 := \mathbf{V}_1 - \mathbf{V}_2 \quad \mathbf{V}_3 = 1 + 4j \cdot \text{V}$$

$$\text{Magnitude: } \sqrt{(1 \cdot \text{V})^2 + (4 \cdot \text{V})^2} = 4.123 \cdot \text{V}$$



$$\text{Angle: } \text{atan}\left(\frac{4 \cdot \text{V}}{1 \cdot \text{V}}\right) = 75.96 \cdot \text{deg}$$

OR:

$$|\mathbf{V}_3| = 4.123 \cdot \text{V}$$

$$\arg(\mathbf{V}_3) = 75.96 \cdot \text{deg}$$
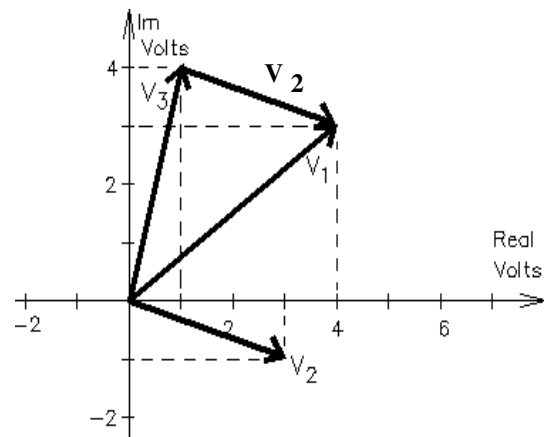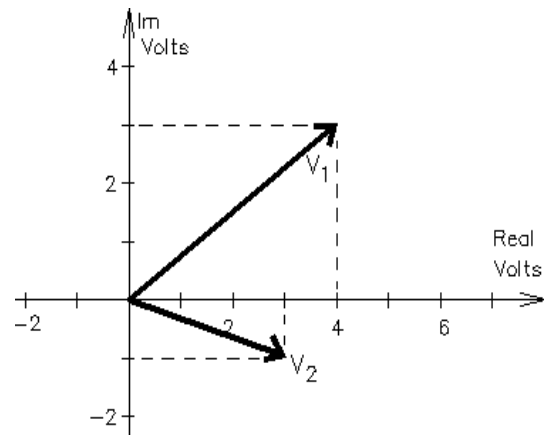
$$\text{So: } v_3(t) = v_1(t) - v_2(t) = 4.123 \cdot \text{V} \cdot \cos(\omega t + 75.96 \cdot \text{deg}) \cdot \text{V}$$



What about Capacitors and Inductors?

Capacitors and Inductors in AC circuits cause 90° phase shifts between voltages and currents because they integrate and differentiate. But... integration and differentiation is a piece-of-cake in phasors.

Intro to Phasors p2

Intro to Phasors p3

Calculus


$$\frac{d}{dt} [A \cdot e^{j(\omega t + \theta)}] = j \cdot \omega \cdot A \cdot e^{j(\omega t + \theta)} = \omega \cdot A \cdot e^{j(\omega t + \theta + 90 \text{ deg})} = \omega \cdot A \cdot e^{j(\theta + 90 \text{ deg})}$$

Drop the ωt ($t=0$) to get:

$$\int A \cdot e^{j(\omega t + \theta)} dt = \frac{1}{j \cdot \omega} \cdot A \cdot e^{j(\omega t + \theta)} = \frac{1}{\omega} \cdot A \cdot e^{j(\omega t + \theta - 90 \text{ deg})} = \frac{1}{\omega} \cdot A \cdot e^{j(\theta - 90 \text{ deg})}$$

Impedance (like resistance)

Inductor

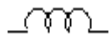

$$v_L = L \cdot \frac{d}{dt} i_L = L \cdot \frac{d}{dt} I_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot L \cdot [I_p \cdot e^{j(\omega t + \theta)}]$$

in phasor notation ----> $V_L(\omega) = j \cdot \omega \cdot L \cdot I(\omega)$

AC impedance

$$Z_L = j \cdot \omega \cdot L$$

Capacitor



$$i_C = C \cdot \frac{d}{dt} v_C = C \cdot \frac{d}{dt} V_p \cdot e^{j(\omega t + \theta)} = j \cdot \omega \cdot C \cdot [V_p \cdot e^{j(\omega t + \theta)}]$$

in phasor notation ----> $I_C(\omega) = j \cdot \omega \cdot C \cdot V(\omega)$

$$V_C(\omega) = \frac{1}{j \cdot \omega \cdot C} \cdot I(\omega)$$

$$Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$$

Resistor




$$v_R = i_R \cdot R$$

$$V_R(\omega) = R \cdot I(\omega)$$

$$Z_R = R$$

You can use impedances just like resistances as long as you deal with the complex arithmetic. ALL the DC circuit analysis techniques will work with AC.

series:

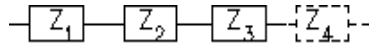


$$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots$$

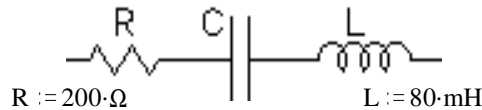Example:

$$f := 500 \text{ Hz}$$

$$\omega := 2 \cdot \pi \cdot f = \omega = 3141.6 \frac{\text{rad}}{\text{sec}}$$



$$R := 200 \cdot \Omega$$

$$C := 0.6 \cdot \mu\text{F}$$

$$L := 80 \text{ mH}$$

$$j \cdot \omega \cdot L = 251.327j \cdot \Omega$$

$$\frac{1}{j \cdot \omega \cdot C} = -530.516j \cdot \Omega$$

$$Z_{eq} := R + \frac{1}{j \cdot \omega \cdot C} + j \cdot \omega \cdot L = 200 \cdot \Omega - 530.5j \cdot \Omega + 251.3j \cdot \Omega = 200 - 279.2j \cdot \Omega \quad \text{rectangular form}$$

$$\sqrt{(200 \cdot \Omega)^2 + (279.2 \cdot \Omega)^2} = 343.4 \cdot \Omega \quad \text{atan}\left(\frac{-279.2 \cdot \Omega}{200 \cdot \Omega}\right) = -54.38 \cdot \text{deg}$$

$$Z_{eq} = 343.4 \Omega \angle -54.4^\circ \quad \text{polar form}$$

$$\text{If: } V := 12 \cdot V \cdot e^{j0 \text{ deg}}$$

$$I := \frac{V}{Z_{eq}} = \frac{12 \cdot V}{343.4 \cdot \Omega} = 34.945 \cdot \text{mA} \quad \angle 0 - -54.4 = 54.4 \text{ deg}$$

$$I = 34.95 \text{ mA} \angle 54.4^\circ = I = 20.348 + 28.405j \cdot \text{mA}$$

Voltage divider:

$$V_{Zn} = V_{total} \cdot \frac{Z_n}{Z_1 + Z_2 + Z_3} + \dots$$


Note: $\frac{1}{j} = -j = 1 \angle -90^\circ$

$$\text{Eg: } V_C := V \cdot \frac{\frac{1}{j \cdot \omega \cdot C}}{Z_{eq}} = 12 \cdot V \cdot e^{j0 \text{ deg}} \cdot \frac{530.516 \cdot e^{-j90 \text{ deg}} \cdot \Omega}{343.4 \cdot e^{-j54.38 \text{ deg}} \cdot \Omega}$$

$$12 \cdot V \cdot \frac{530.516 \cdot \Omega}{343.4 \cdot \Omega} = 18.539 \cdot V \quad \angle 0 + -90 - -54.4 = -35.6 \text{ deg}$$

$$V_C = 18.54 \text{ V} \angle -35.6^\circ = V_C = 15.069 - 10.795j \cdot V$$


parallel:

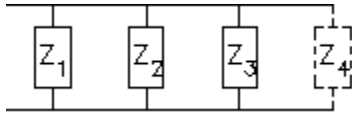

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

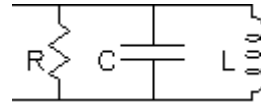Example:

$$f := 500 \cdot \text{Hz} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 3141.6 \cdot \frac{\text{rad}}{\text{sec}}$$



$$R := 200 \cdot \Omega \quad C := 0.6 \cdot \mu\text{F} \quad L := 80 \cdot \text{mH}$$

$$j \cdot \omega \cdot L = 251.327j \cdot \Omega \quad \frac{1}{\omega \cdot L} = 3.979 \cdot 10^{-3} \cdot \frac{1}{\Omega}$$

$$\frac{1}{j \cdot \omega \cdot C} = -530.516j \cdot \Omega$$

$$\omega \cdot C = 1.885 \cdot 10^{-3} \cdot \frac{1}{\Omega}$$

$$Z_{eq} := \frac{1}{\frac{1}{R} + \frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} + \frac{1}{j \cdot \omega \cdot L}} = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C - \frac{j}{\omega \cdot L}} = \frac{1}{\frac{1}{200 \cdot \Omega} + 1.885 \cdot 10^{-3} \cdot j - 3.979 \cdot 10^{-3} \cdot j \cdot \frac{1}{\Omega}}$$

$$= \frac{1}{\left(5 \cdot 10^{-3} - 2.094 \cdot 10^{-3} \cdot j\right) \cdot \frac{1}{\Omega}} = \frac{5 \cdot 10^{-3} + 2.094 \cdot 10^{-3} \cdot j}{2.93848 \cdot 10^{-5}} = 170.156 + 71.261j \cdot \Omega$$

If you want the answer in polar form, it's easier to convert the denominator first.

$$\sqrt{\left(5 \cdot 10^{-3} \cdot \frac{1}{\Omega}\right)^2 + \left(2.094 \cdot 10^{-3} \cdot \frac{1}{\Omega}\right)^2} = 5.4 \cdot 10^{-3} \cdot \frac{1}{\Omega} \quad \text{atan}\left(\frac{2.094 \cdot 10^{-3} \cdot \Omega}{5 \cdot 10^{-3} \cdot \Omega}\right) = 22.72 \cdot \text{deg}$$

$$\frac{1}{5.4 \cdot 10^{-3} \cdot \frac{1}{\Omega}} = 185.185 \cdot \Omega$$

$$Z_{eq} = 185.2 \angle 22.7^\circ$$

$$\text{If: } V := 12 \cdot \text{V} \cdot e^{j0 \cdot \text{deg}} \quad I := \frac{V}{Z_{eq}} = \frac{12 \cdot \text{V}}{185.2 \cdot \Omega} = 64.795 \cdot \text{mA} \quad \angle 0 - 22.7 = -22.7 \text{ deg}$$

$$I = 60 - 25.127j \cdot \text{mA}$$

Current divider:

$$I_{Z_n} = I_{\text{total}} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots} \quad \text{Eg: } I_L := I \cdot \frac{\frac{1}{j \cdot \omega \cdot L}}{\frac{1}{R} + j \cdot \omega \cdot C + \frac{1}{j \cdot \omega \cdot L}} = I \cdot \frac{Z_{eq}}{j \cdot \omega \cdot L}$$

$$= 64.795 \cdot \text{mA} \cdot e^{j22.7 \cdot \text{deg}} \cdot \frac{185.2 \cdot e^{-j22.7 \cdot \text{deg}} \cdot \Omega}{251.327 \cdot e^{j90 \cdot \text{deg}} \cdot \Omega}$$

$$= 64.795 \cdot \text{mA} \cdot \frac{185.2 \cdot \Omega}{251.327 \cdot \Omega} = 47.747 \cdot \text{mA} \quad \angle 22.7 + -22.7 - 90 = -90 \text{ deg} \quad I_L = -47.746j \cdot \text{mA}$$