
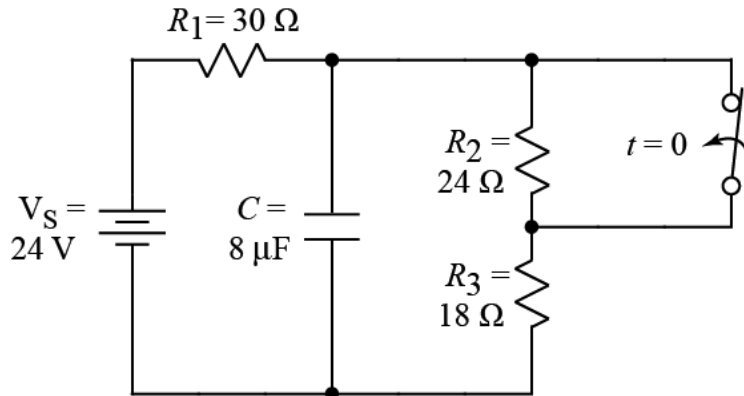


Ex:

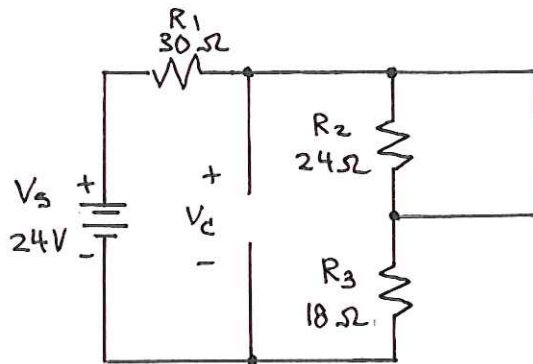

- The switch has been open for a long time and is closed (as shown) at  $t = 0$ .
- Find the initial and final conditions and write the full expression for  $v_C(t)$ , including all the constants that you find.

sol'n: At  $t=0^-$ , the switch is open and  $C = \text{open}$ :




We find  $v_C(0^-) = V$  across  $R_2 + R_3$  by using a  $V$ -divider.

$$v_C(0^-) = V_S \frac{R_2 + R_3}{R_1 + R_2 + R_3} = 24V \cdot \frac{24\Omega + 18\Omega}{30\Omega + 24\Omega + 18\Omega}$$

$$v_C(0^-) = 24V \cdot \frac{42\Omega}{72\Omega} = 14V$$

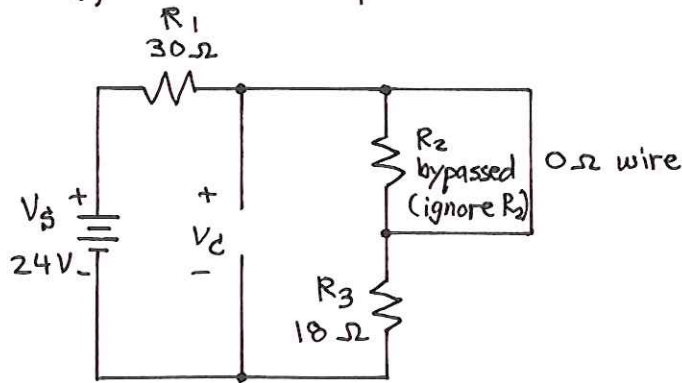For  $t \rightarrow \infty$ , the switch is closed, bypassing  $R_2$ , and  $C = \text{open}$ .




Again, we have a V-divider.

$$V_c(t \rightarrow \infty) = V_s \frac{R_3}{R_1 + R_3} = 24V \frac{18\Omega}{30\Omega + 18\Omega}$$

$$V_c(t \rightarrow \infty) = 24V \cdot \frac{18\Omega}{48\Omega} = 9V$$

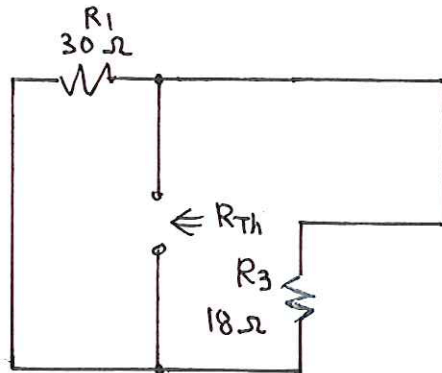For the time constant,  $\tau = R_{Th} C$ , we find  $R_{Th}$  looking into the circuit from the terminals where  $C$  is connected. We turn off  $V_s$ , which becomes a wire.



$$R_{Th} = 30\Omega \parallel 18\Omega = 6\Omega \cdot 5 \parallel 3 = 6\Omega \cdot \frac{15}{8} = \frac{90}{8}\Omega$$

$$\tau = R_{Th} C = \frac{90}{8}\Omega \cdot 8\mu F = 90\mu s$$

We now use the general sol'n for RC probs:

$$V_c(t) = V_c(t \rightarrow \infty) + [V_c(0^+) - V_c(t \rightarrow \infty)] e^{-t/\tau}$$

where  $V_c(0^+) = V_c(0^-)$  (C voltage doesn't jump)

$$V_c(t) = 9V + (14V - 9V) e^{-t/90\mu s}$$

or

$$V_c(t) = 9V + 5V e^{-t/90\mu s}$$