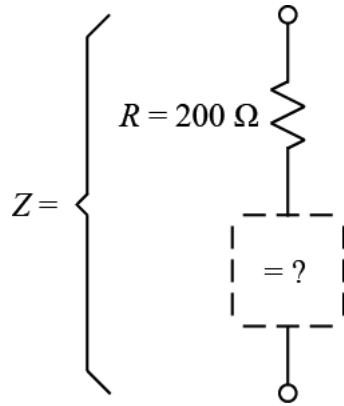


Ex:




The total impedance of the above circuitry is  $Z = |Z|e^{j40^\circ}$ . We don't know the magnitude of  $Z$ , but its phase angle is  $+40^\circ$ .  $Z$  is made of a  $200\Omega$  resistor in series with one other part. What is that part? Give the type and value of the part, and draw the combination.

$$\omega = 3000 \text{ rad/sec}$$

sol'n: We can consider the magnitude and phase of  $Z$  in separate Ohm's law equations:

$$|Z| = \frac{|V|}{|I|} \quad \text{and} \quad \angle Z = \angle V - \angle I = 40^\circ$$

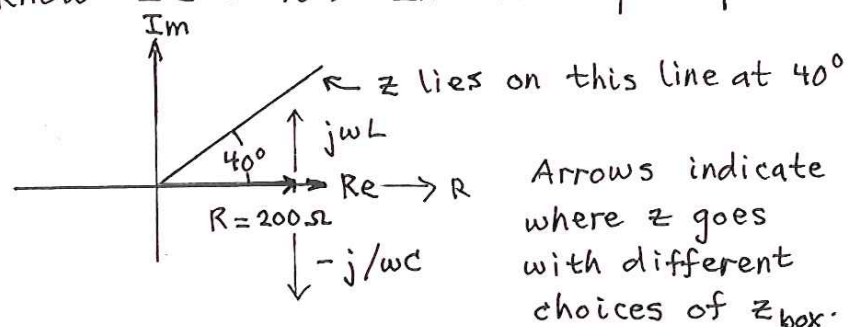Our value for  $Z$  is  $Z = 200\Omega + Z_{\text{box}}$ , and we know  $\angle Z = 40^\circ$ . In the complex plane:



From the diagram, we see we need  $j\omega L$ , with  $\angle R + j\omega L = 40^\circ$ .

$$40^\circ = \tan^{-1} \frac{\omega L}{R} \quad \text{or} \quad L = \frac{R}{\omega} \tan 40^\circ = \frac{200}{3000} (0.839) \approx 56 \text{ mH}$$