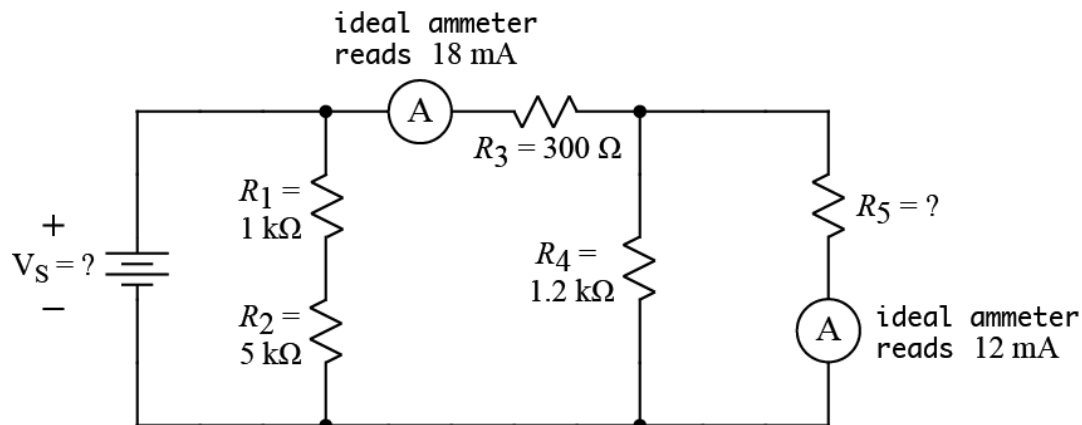





1.



Find the values of the following quantities of the above circuit.

- R_5
- V_S
- P_S (the power delivered by the V_S source)


2.

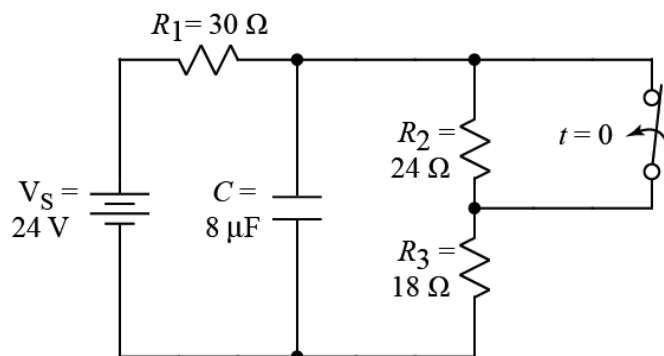

The switch has been open for a long time and is closed (as shown) at $t = 0$.

Find the initial and final conditions and write the full expression for $v_C(t)$, including all the constants that you find.


3.

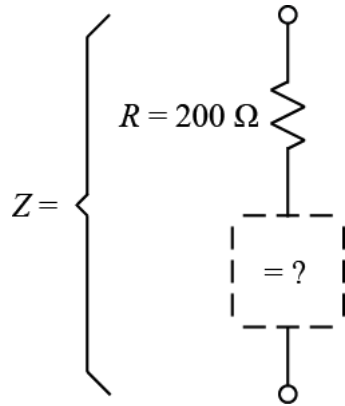

The total impedance of the above circuitry is $Z = |Z|e^{j40^\circ}$. We don't know the magnitude of Z , but its phase angle is $+40^\circ$. Z is made of a $200\ \Omega$ resistor in series with one other part. What is that part? Give the type and value of the part, and draw the combination.

$$\omega = 3000\ \text{rad/sec}$$

4.

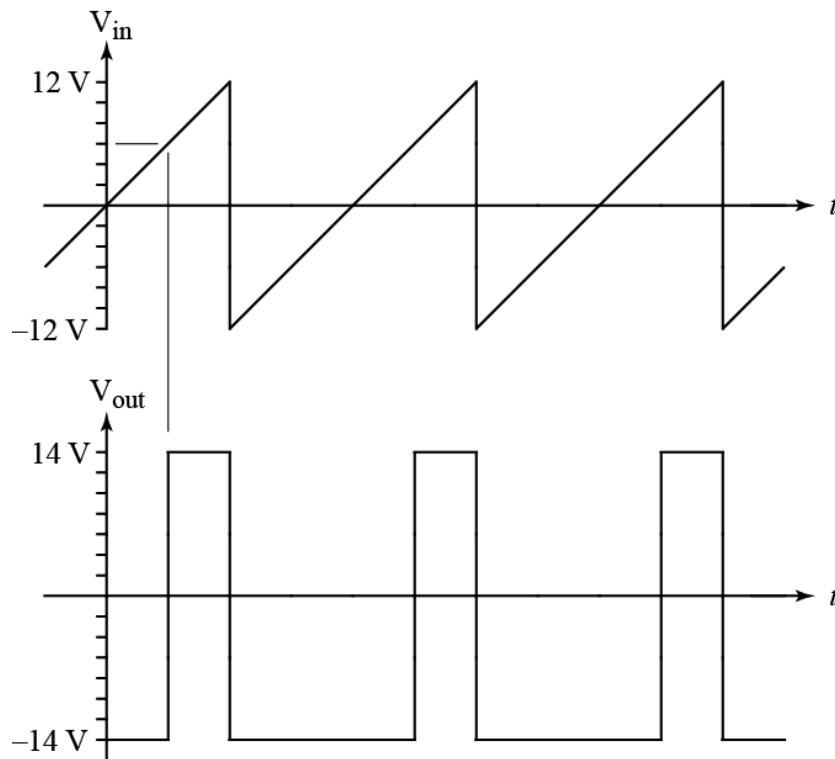

Using op-amps, power supplies, and resistors, draw a circuit to produce V_{out} from V_{in} . (Assume you have a function generator that produces V_{in} for you to use.) Show all relevant information in your circuit, including power supply voltages for op-amps.

5. Write a Matlab® function called `grades` that prints out the letter grade for a student based on the percent of possible points the student has earned during a semester. Use the classic grade scale used for this course (see Syllabus): 93% or higher = A, 90% or higher = A-, 87% or higher = B+, 83% or higher = B, etc.
6. Write a Matlab function called `RCplot` that plots the voltage on a capacitor versus time. Specifically, `RCplot` does the following:
 - i) Accepts three input values: `vzero`, `vinf`, and `tau` representing the initial voltage on the capacitor, the final voltage on the capacitor, and the time constant in the standard formula for capacitor voltage: $v_C = v_{inf} + (v_{zero} - v_{inf})e^{-t/\tau}$
 - ii) Test whether `tau` is negative and, if so, prints an error message and returns to the calling program.
 - iii) Creates an array called `t` containing time values from 0 to 1 ms (i.e., 0.001 sec) (inclusive) spaced by 1 μ sec (i.e., 10^{-6} seconds).
 - iv) Creates an array called `vC` containing capacitor voltage for each time in array `t`. (Use the standard formula for v_C , above.)
 - v) Plots v_C versus t as a blue line on an x-y plot.
 - vi) Labels the x-axis as "time", the y-axis as "voltage", and titles the plot "Capacitor Voltage".
7. Write a Matlab® script file that does the following:
 - i) Loads the sound file for Handel's Messiah into variable `y`.
 - ii) Shortens `y` to 8000 samples.
 - iii) Computes the Fast Fourier Transform (FFT) of `y` and stores it in `yfft`. (The values in `yfft` represent frequency content for frequencies 0 to 7999 Hz.)
 - iv) Multiplies the samples in `yfft` by the following function:

$$F(f) = \begin{cases} 1 + \frac{f}{2000} & 0 \leq f \leq 3999 \\ 1 + \frac{8000 - f}{2000} & 4000 \leq f \leq 7999 \end{cases}$$

where f is the frequency of the sample in `yfft`.

- v) Takes the inverse FFT of the modified `yfft` and stores it in `yout`.
- vi) Plays the sound in `yout`.

8. function mat_dist = word_dist(mat)

```
nrows = size(mat,1);
mat_dist = zeros(nrows);

for ind1 = 1:size(mat,1)
    for ind2 = 1:size(mat,1)
        mat_dist(ind1,ind2) = sum(abs(mat(ind1,:)-mat(ind2,:)));
    end
end
end
```

For the above Matlab® function, find the result of the following commands:

```
>> D = [1, 0, 1, 0; 0, 0, 1, 1; 1, 0, 0, 1; 0, 0, 0, 1];
>> wd = word_dist(D);
>> wd(find(wd(:,1)>0),:)
```

9. function sys_out = conv_v(sys_in,imp_resp)

```
sys_in2 = [sys_in, zeros(1,length(imp_resp)-1)];
for ind = 1:length(sys_in);
    sys_out(ind) = sum(sys_in2(ind:ind+length(imp_resp)-1)...
        .* imp_resp(end:-1:1));
end
end
```

For the above Matlab® function, find the result of the following commands:

```
>> vin = [3, 2, 6, 2, 8, 0, 1];
>> h = [1, 0, -1];
>> vout = conv_v(vin,h)
```