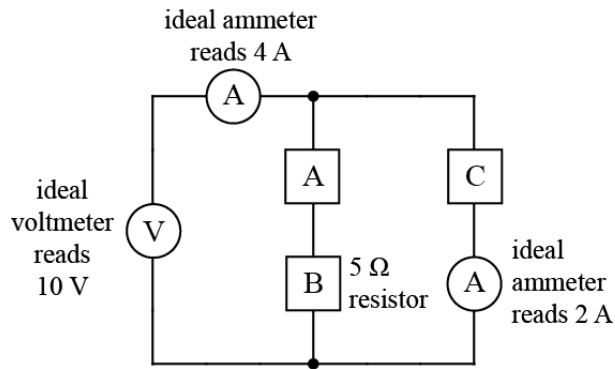





1.




If box A contains a resistor, find the value of that resistor.

2.

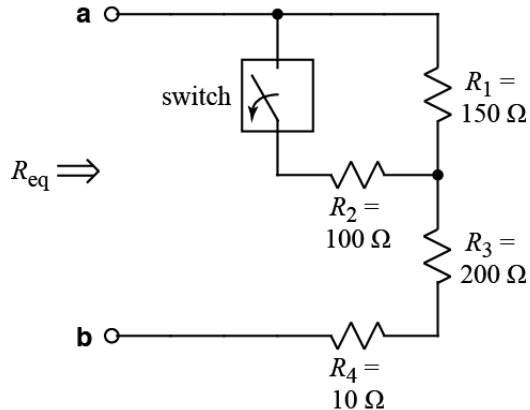


- Find the equivalent resistance from **a** to **b** with the switch open and then with the switch closed.
- If a voltage source is connected across **a** and **b** and this causes a voltage drop across R_4 of 2V, what is the voltage drop across R_3 ?

3.

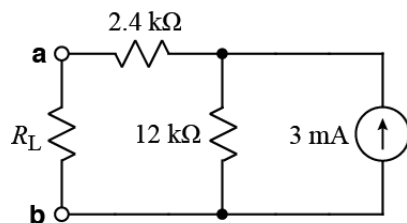


- Find the Thevenin equivalent of the above circuit (without R_L).
- Find the power supplied by the current source when R_L is Not connected.

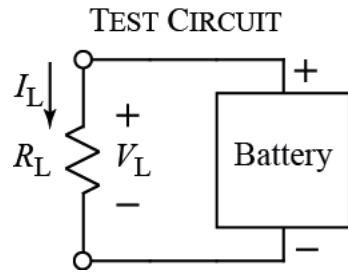4. a) Given the following data for a battery, find an appropriate model for the battery.



DATA		
R_L	V_L	I_L
0.5Ω	3 V	6 A
2Ω	4 V	2 A

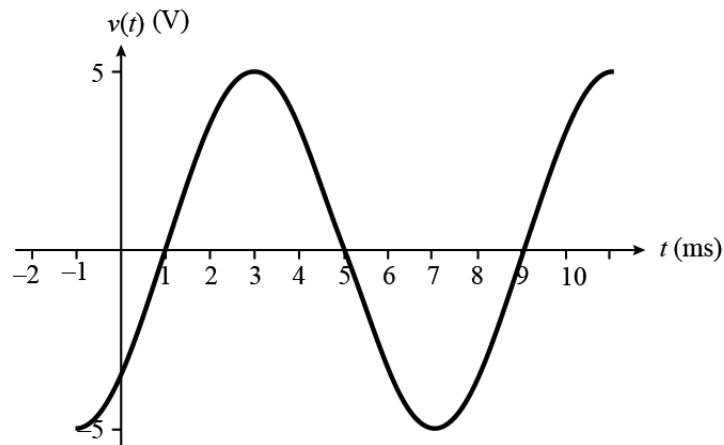- b) If the battery is placed in a charger that delivers 5V to the battery, how much power must the recharger supply to the battery?
5. a) $v(t) = A \cos(\omega t + \phi)$ is shown below. Find the values of A , ω , ϕ , and period T for $v(t)$.



- b) Find the average power for the PWM signal below driving a 10Ω resistor.

