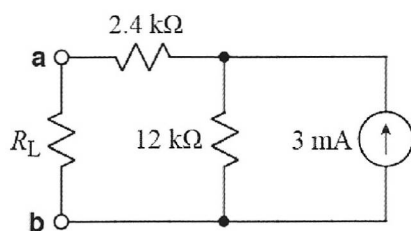





3.



- a) Find the Thevenin equivalent of the above circuit (without R_L).
- b) Find the power supplied by the current source when R_L is Not connected.


sol'n: a) $V_{Th} = V_{a,b}$ with no R_L

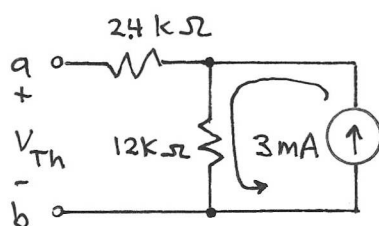


The $24k\Omega$ carries no current and has no V -drop. Also, all the current from the i -src must flow thru the $12k\Omega$. So V_{Th} equals the V -drop across the $12k\Omega$, and the V -drop across the $12k\Omega$ is $V_{Th} = 3mA \cdot 12k\Omega$:

$$V_{Th} = 36V$$

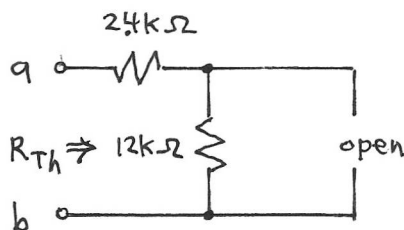We find R_{Th} by turning off the i -src and looking in from a, b . $R_{Th} = 12k\Omega + 24k\Omega = 14.4k\Omega$.



Our Thevenin equivalent:

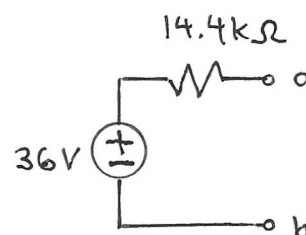

b) When R_L is not present, there is no current in the $2.4\text{k}\Omega$ resistor and no power consumed by it. The power supplied by the current source is the power consumed by the $12\text{k}\Omega$ resistor. From part (a), we know that 3mA flows in the $12\text{k}\Omega$, so we have the power from I^2R :

$$P_{i\text{-src}} = I^2R = (3\text{mA})^2 \cdot 12\text{k}\Omega = 108\text{mW}$$