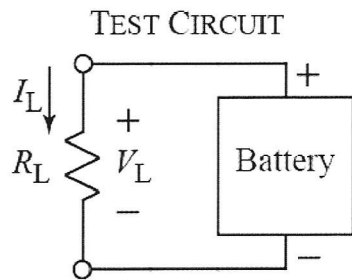



4. a) Given the following data for a battery, find an appropriate model for the battery.




DATA		
$R_L$	$V_L$	$I_L$
$0.5 \Omega$	3 V	6 A
$2 \Omega$	4 V	2 A

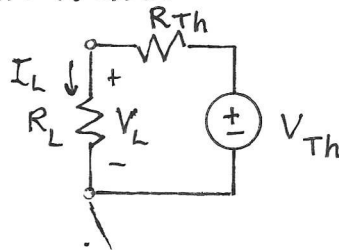- b) If the battery is placed in a charger that delivers 5V to the battery, how much power must the recharger supply to the battery?

sol'n: a) The battery acts like a  $V$ -source with an internal resistance, so we use a Thevenin equivalent.



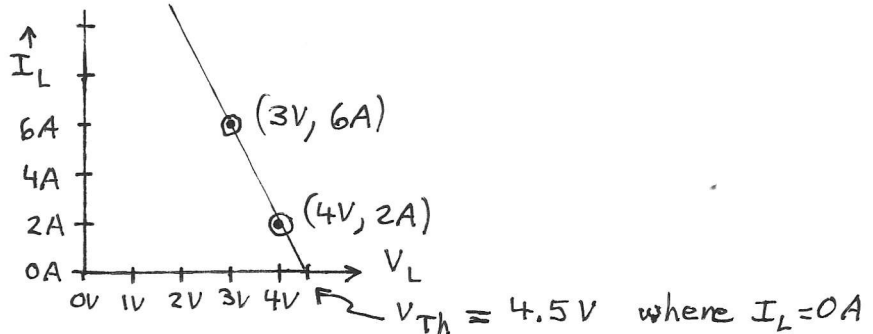We can use a graph to help us find the values of  $V_{TH}$  and  $R_{TH}$ .



From the graph it appears  $V_{TH} = 4.5V$ . We can use the slope to precisely determine  $V_{TH}$  and  $R_{TH}$ .

$$\text{slope } \frac{\Delta V_L}{\Delta I_L} = \frac{4V - 3V}{2A - 6A} = -\frac{1V}{4A}$$

Note that we use  $\Delta V/\Delta I$  because it gives us  $R_{Th}$ .

$$R_{Th} = -\text{slope} \frac{\Delta V}{\Delta I} = -\left(-\frac{1V}{4A}\right) = 0.25 \Omega$$

because  $R_{Th}$  from  $V_L = V_{Th} - V_{R_{Th}}$

To compute  $V_{Th}$ , we use  $I_L = 0$  (open circuit for  $R_L$ ).  $(V_{Th}, 0)$  is another point on the line.

$$\text{slope} \frac{\Delta V_L}{\Delta I_L} = \frac{V_{Th} - 4V}{0A - 2A} = -\frac{1}{4} \Omega$$


or

$$V_{Th} - 4V = -\frac{1}{4} \Omega (-2A) = \frac{1}{2} V$$


or

$$V_{Th} = 4V + \frac{1}{2} V = 4.5 V$$

Battery Model:

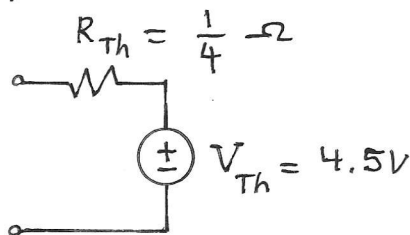

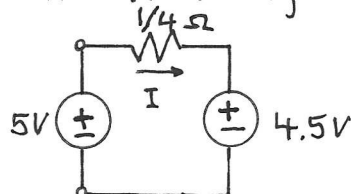- b) We have 5V on the output of the battery. The following is a circuit model.



$$\text{Current } I = \frac{5V - 4.5V}{1/4 \Omega} = 2A$$

The power is the voltage (5V) times the current.

$$P = VI = 5V \cdot 2A = 10W$$