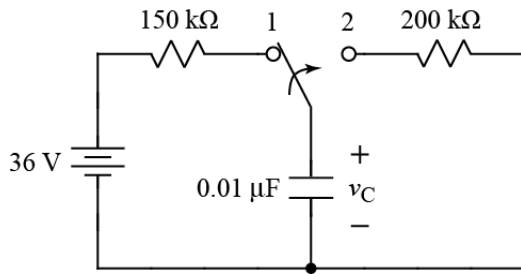




1.



After being on side 1 for a long time, the switch moves from side 1 to side 2 at  $t = 0$ .

- Find the value of  $v_C(t = 0)$ .
- Find an expression for  $v_C(t > 0)$ .
- Find the value of the energy stored by the capacitor at time  $t = 3\tau$  where  $\tau =$  time constant for circuit after  $t = 0$ .

**SOL'N:** a)  $v_C(t = 0) = 36 \text{ V}$ . C charges to voltage of power supply.


b)  $v_C(t \rightarrow \infty) = 0 \text{ V}$ ,  $R_{\text{Thev}} = 200 \text{ k}\Omega$  for  $t > 0$ .  $\tau = R_{\text{Thev}}C = 2 \text{ ms}$ .

$$v_C(t > 0) = 0 \text{ V} + [36 \text{ V} - 0 \text{ V}]e^{-t/2 \text{ ms}}$$

c)  $v_C(t = 3\tau) = 36 \text{ V} e^{-3} \approx 1.8 \text{ V}$ ,  $w_C = \frac{1}{2} CV^2 = \frac{1}{2} (0.01 \mu\text{F})(1.8)^2 \text{ J} = 16 \text{ nJ}$

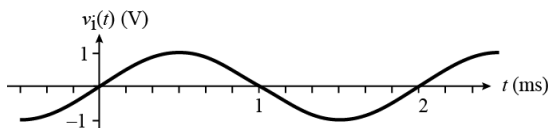
2.

A function generator outputs the following signal,  $v_i(t)$ .




Design op-amp circuits to output each of the following waveforms when  $v_i(t)$  is the input.

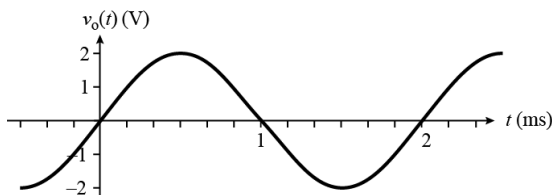You may use either one or two op-amps in each case.




a)

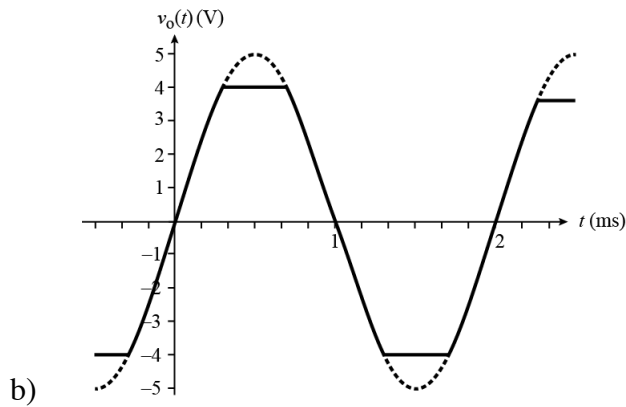sol'n: Non-inverting amp,  $R_f = R_s > 1 \text{ k}\Omega$




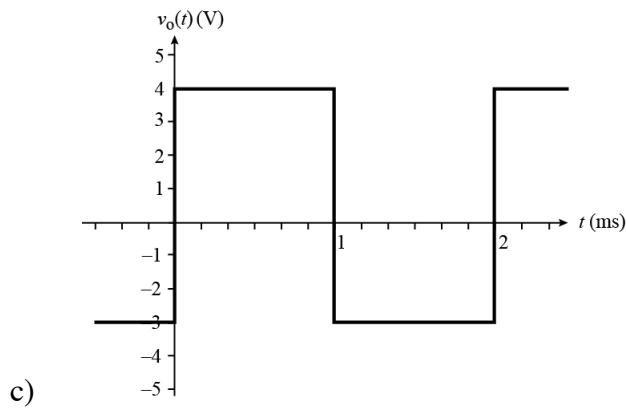sol'n: Non-inverting amp,  $R_f = 4R_s > 1 \text{ k}\Omega$   
clipped, so use pwr supply  $\pm 5 \text{ V}$ .



sol'n: Use comparator  $v_i$  vs  $0\text{V}$ ,  
pwr supply  $\pm 5 \text{ V}$ , then summing  
amp to add  $1\text{V}$ .

3.

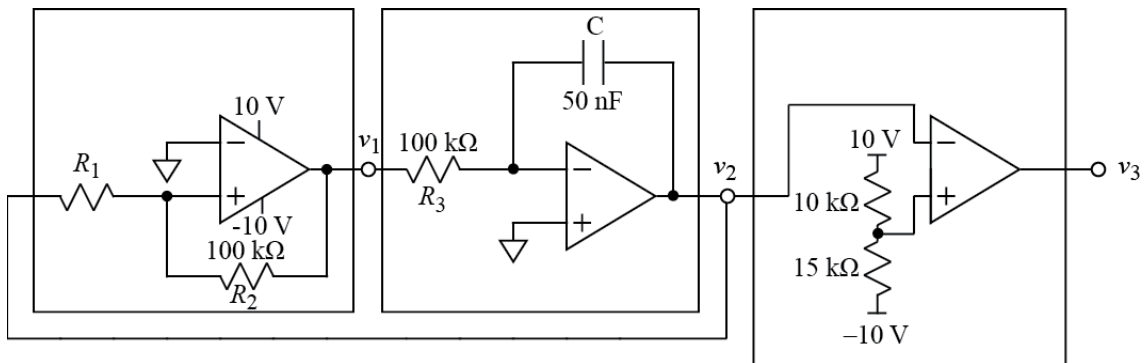

The above circuit is from Lab 4, but some of the component values have been changed.

- a) Find the minimum and maximum values allowed for  $R_1$  in order to achieve proper operation: 1) successfully generating a triangle wave (which requires that  $v_1$  switches from high to low and back), and 2) avoiding clipping that would occur if  $v_2$  exceeded the rail voltage for the op-amp.

**SOL'N:** a)  $R_1$  and  $R_2$  form V-divider between  $v_1$  and  $v_2$ .  $v_2$  must pull  $v_+$  of 1st op-amp below 0 V in order to switch  $v_1$  when  $v_1$  is  $-v_{\text{rail}}$  and  $v_2$  is  $+v_{\text{rail}}$ . Need  $R_1 < R_2$  for that to happen. So  $R_1 = 100 \text{ k}\Omega$  is the maximum. The other condition cannot occur, since if  $v_2$  hits the rail voltage, it will just stay there.  $v_1$  and  $v_2$  will then stay the same and switching will never occur.

b) Choose an allowed value for  $R_1$  and calculate the period of  $v_2(t)$ .

**SOL'N:** b) Many solutions. Key equations are:

$$0 \text{ V} = v_+ = \frac{v_1 R_1 + v_2 R_2}{R_1 + R_2} = \frac{-v_{\text{rail}} R_1 + v_2 R_2}{R_1 + R_2} \text{ solve for peak } v_2.$$

$$v_{2\text{peak}} = \frac{v_{\text{rail}} R_1}{R_2} = \frac{9 \text{ V} \cdot R_1}{100 \text{ k}\Omega}$$

$$\text{slope of } v_2 = -\frac{I}{C} = -\frac{v_1}{R_3 C} = -\frac{v_{\text{rail}}}{R_3 C} = \frac{-9 \text{ V}}{5 \text{ ms}} = -1.8 \text{ kV/s}$$

Half of period = time for  $v_2$  to go from -pk to +pk =  $2v_{2 \text{ pk}}$

or half period =  $2v_{2 \text{ pk}}/\text{slope of } v_2$ .

c) Draw a graph of  $v_2(t)$  and  $v_3(t)$  for at least one period of  $v_2(t)$ . Label all important times and voltages on the graph.

**SOL'N:** b)  $v_2(t)$  = triangle wave with slope and max  $v_2$  and period from (b).

$$0 \text{ V} = v_+ = \frac{v_1 R_1 + v_2 R_2}{R_1 + R_2} = \frac{-v_{\text{rail}} R_1 + v_2 R_2}{R_1 + R_2} \text{ solve for peak } v_2.$$

$v_3(t)$  is rectangular waveform. High voltage =  $+v_{\text{rail}} = 9 \text{ V}$ , low V =  $-9 \text{ V}$ .

$v_3(t)$  is high when  $v_2 > +2 \text{ V} = v_+$  of third op-amp.