

HW P1

$$1. a. (-4+5j)(2-4j) = -8 + 10j + 16j + 20 = 12 + 26j$$

$$\sqrt{12^2 + 26^2} = 28.6356 \quad \sqrt{4^2 + 5^2} \cdot \sqrt{2^2 + 4^2} = 28.6356$$

equal

$$b. \frac{-4+5j}{2-4j} \cdot \frac{(2+4j)}{(2+4j)} = \frac{(-4+5j)(2+4j)}{4+16} = \frac{-8-16j+10j-20}{20}$$

$$= \frac{-28-6j}{20} = \sqrt{\left(\frac{-28}{20}\right)^2 + \left(\frac{-6}{20}\right)^2} = 1.43$$

$$\frac{|z_1|}{|z_2|} = \frac{6.403}{4.47} = 1.43$$

equal

$$c. |z_1 + z_2| = |-4+5j + 2+4j| = |2+9j| = 9.2195$$

$$|z_1| + |z_2| = 6.403 + 4.47 = 10.873$$

Not equal

$$2. a. 98 = 8.4 \angle 90^\circ = 8.4j = 8.4e^{j90^\circ}$$

$$b. I = (5+12j) \mu A \quad F = 600 \text{ Hz} \quad \omega = 600 \cdot 2\pi = 3769.9$$

$$|I| = 13 \quad \tan^{-1}\left(\frac{12}{5}\right) = 67.38^\circ$$

$$i(t) = 13 \mu A \cos(3769.9t + 67.38^\circ)$$


$$3. a. v_1 + v_2 = 1.5V \cos(\omega t + 10^\circ) + 3.2V \cos(\omega t + 25^\circ)$$

$$1.477 + .26j + 2.9 + 1.35j = 4.377 + 1.61j$$

$$= 4.66 \cos(\omega t + 20.195^\circ)$$

$$b. v_1 - v_2 = 1.477 + .26j - 2.9 - 1.35j = -1.423 - 1.09j$$
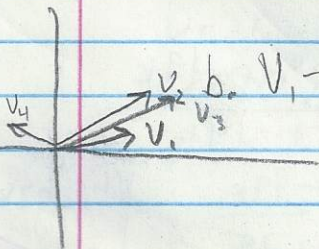
$$= 1.792 \cos(\omega t + 142.548^\circ)$$



4. $\omega = 60 \cdot 2\pi$ $L = 5.2 \text{ mH}$ $Z = j\omega L = 1.96j = \underline{1.96j \Omega}$

5. a. $Z = \frac{1}{j\omega C}$ $240 \Omega = \frac{1}{j(1.8)C}$ $240 j(1.8)C = 1$

$C = 3.68 \times 10^{-7} = \underline{.368 \mu\text{F}}$

b. $240 = j(1.8 \cdot 2\pi k)(L) = \underline{21.2 \text{ mH}}$

c. Linear. Due to L: 2x frequency = 2x impedance = 240 Ω

Due to C: 1/2 impedance = -120 Ω ($\frac{1}{j} = -j$)

d. $j(2.7 \cdot 2\pi k) 21.2 \text{ mH} + \frac{-j}{2\pi f \cdot .368 \mu\text{F}} = 359.65 - 160 = \underline{199.65 \Omega}$

6. a. $Z_{eq} = 330 \Omega + j(1k \cdot 2\pi)(100 \text{ m}) = \underline{330 \Omega + 200j \Omega}$

b. $330 + \frac{-j}{.22 \mu\text{F} \cdot 4\pi k} = \underline{330 \Omega - 361j \Omega}$

c. No values? = $R + j\omega L - \frac{j}{\omega C}$ $\omega = 8\pi \text{ kHz}$

d. $j(1.5 \cdot 2\pi k) \cdot 160 \text{ m} + 4k \parallel \frac{1}{j(1.5 \cdot 2\pi) \cdot 0.3 \mu}$

$= 15.08k + 4k \parallel -3.5kj$

$= 15.08k \Omega + \left(\frac{1}{4k} \parallel \frac{-1}{3.5kj} \right)^{-1}$

$= 15.08k \Omega + \frac{14kj}{3.5kj - 4k} \left(\frac{-4k - 3.5kj}{-4k - 3.5kj} \right)$

$= 15.08k \Omega + \frac{-56kj + 49k}{12.25k - 14k}$

$= 15.08k \Omega + \frac{-56kj}{-1.75} + \frac{-49k}{1.75} = \underline{(-12.92k + 32kj) \Omega}$

7. a. currents $10 / \sqrt{330^2 + 200\pi^2} \angle -\tan^{-1} \left(\frac{200\pi}{330} \right) = 14.1 \text{ mA} / 62.29^\circ$

b. $10 / \sqrt{330^2 + 361^2} \angle -\tan^{-1} \frac{361}{330} = 20.4 \text{ mA} / 47.63^\circ$

c. $I = \frac{V}{R} \Rightarrow I = \frac{100}{R + j\omega L - \frac{j}{\omega C}}$

d. $10 / \sqrt{12.92^2 + 32^2} \angle -\tan^{-1} \frac{32}{12.92} = 29 \text{ mA} / 68^\circ$

8. a. $V = \frac{I}{R} \quad R = \frac{V}{I} = \frac{14 \angle 16^\circ}{30 \text{ m} \angle 36^\circ} = \frac{14 \cos 16 + 14 \sin 16j}{30 \cos 36 + 30 \sin 36j}$

$$= \frac{13.458 + 3.86j (24.27 - 17.63j)}{24.27 + 17.63j (24.27 - 17.63j)}$$

$$= \frac{13.458 \cdot 24.27 + 13.458 \cdot (-17.63j) + 3.86j \cdot 24.27 + 3.86j \cdot (-17.63j)}{24.27^2 + 17.63^2}$$

626.24

$$= \frac{326.62 + 68 + 237.26j + 93.68j}{626.24}$$

$$= \frac{394.62}{626.24} - \frac{143.58}{626.24} = .63 - .229j$$

$$\frac{14 \angle 16}{30 \text{ m} \angle 36} = 466 = 438.5 - 159.6j \quad -180$$

$$\boxed{Z = 258.5 - 159.6j}$$

b. current (by 20°)

c. 20°

9. a. $20.336 + -45.677j$

$R = 20.336 \Omega$

$\omega = 6\pi$

$\omega C 45.677 = 1 \quad C = \frac{1}{6\pi \cdot 45.677}$

$C = 1.161 \mu F$

b. $20.336 + -45.677j \left(\frac{20.336 + 45.677j}{20.336 + 45.677j} \right)$

$= \frac{413.5 + 2086.39}{20.336 + 45.677j}$

$\frac{1}{Z_{eq}} = .02 \angle 66^\circ = \frac{1}{R} + j\omega C$
 $.008 + .01827j$

$R = 122.93 \Omega$


$C = .9693 \mu F$

10. a. $\left| \frac{V}{I} \right| = \frac{\sqrt{60^2 + 28^2}}{3.4} = 19.47$

b. $19.47 \cos 55^\circ = 11.167 \Omega$

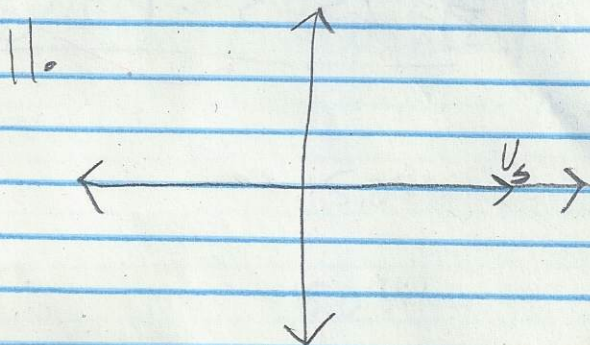c. V ahead of current, Inductor

$19.47 \sin 55^\circ = 15.949 = \frac{42.3 \text{ mH}}{2\pi \cdot 60}$



$Z = -j + 40$
 $\frac{1 \text{ k}\Omega}{12 \mu}$

$Z = 43.3j + 40 = 128.8 \Omega$
 $= 92.436 \angle -64.36^\circ$

$$11. V_s = 12 \angle 0^\circ \quad f = 500 \text{ Hz} \quad L = 12 \mu\text{F} \quad R = 40 \Omega$$

$$Z_{in} = -26.52j + 40 = 48 \angle -33.55^\circ$$

$$I = \frac{V}{R} = \frac{12 \angle 0^\circ}{48 \angle -33.55^\circ} = .25 \angle 33.55^\circ$$

$$I = .25 \angle 33.55^\circ$$

$$V_R = I R = 10 \angle 33.55^\circ$$

$$V_L = I R_L = 26.52 \angle -90^\circ \cdot .25 \angle 33.55^\circ \\ = 6.63 \angle -56.45^\circ$$

