
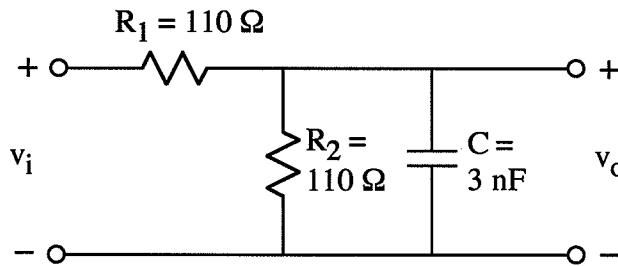


EX:

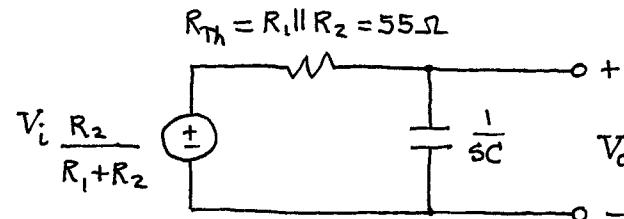

- Determine the transfer function V_o/V_i . Hint: Use a Thevenin equivalent to reduce the two R's to a single R.
- Plot $|V_o/V_i|$ versus ω .
- Find the cutoff frequency, ω_c .

sol'n: a) Use a Thevenin equivalent for v_i , R_1 , and R_2 :



We get the transfer function, $H(s)$, from the voltage-divider formula:

$$V_o(s) = V_i(s) \frac{R_2}{R_1 + R_2} \cdot \frac{1/sC}{1/sC + R_{Th}}$$

Divide by sides by $V_i(s)$ to obtain $H(s)$:

$$H(s) \equiv \frac{V_o(s)}{V_i(s)} = \frac{R_2}{R_1 + R_2} \frac{1/sC}{1/sC + R_{Th}}$$

A convenient form for $H(s)$ is $H(s) = k \frac{1}{1 + jX}$

where $k = \text{real constant}$

$X \equiv \text{real term involving } \omega \text{ and component values}$

In the present case, we multiply top and bottom of $H(s)$ by sC .

$$H(s) = \frac{R_2}{R_1 + R_2} \frac{1}{1 + s R_{Th} C} = \frac{R_2}{R_1 + R_2} \frac{1}{1 + j \omega R_{Th} C}$$


b) Since $\frac{1}{sC} = \frac{1}{0} = \infty @ \omega = 0$, $V_o = V_i \frac{R_2}{R_1 + R_2}$.

$$\therefore |H(s=j0)| = \frac{R_2}{R_1 + R_2} \text{ for } \omega = 0$$

Since $\frac{1}{sC} = \frac{1}{\infty} = 0 @ \omega = \infty$, we effectively have $C = \text{wire}$. Thus, $V_o = 0$.

$$\therefore |H(s=j\omega)| = 0 \text{ for } \omega = \infty$$

Between $\omega = 0$ and $\omega = \infty$, the C starts to become a short circuit and $|H(s)|$ decreases.

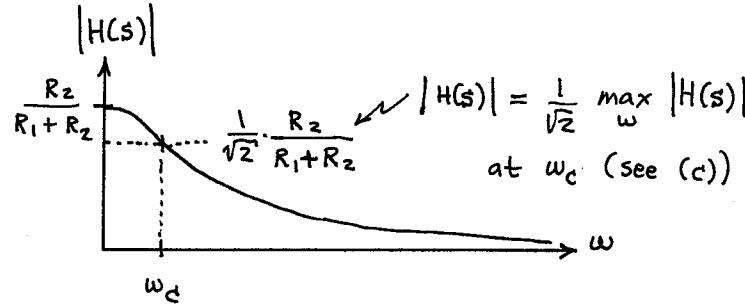

c) ω_c is the value of ω where $|H(s)|$ is

$$\frac{1}{\sqrt{2}} \text{ times } \max_w |H(s)|.$$

$$\text{In other words, } \frac{|H(j\omega_c)|}{\max_w |H(s)|} = \frac{1}{\sqrt{2}}.$$

In the present case, we have

$$\frac{|H(j\omega_c)|}{\max_w |H(s)|} = \frac{\frac{R_2}{R_1+R_2} \frac{1}{1+j\omega_c R_{Th}C}}{\frac{R_2}{R_1+R_2}} = \frac{1}{\sqrt{2}}$$

$$\text{or } \frac{1}{1+j\omega_c R_{Th}C} = \frac{1}{\sqrt{2}}$$

$$\text{or } 1+j\omega_c R_{Th}C = \sqrt{2}$$

$$\text{or } \sqrt{1^2 + (\omega_c R_{Th}C)^2} = \sqrt{2}$$

$$\text{or } 1 + (\omega_c R_{Th}C)^2 = \pm 2$$

Since $(\omega_c R_{Th}C)^2 > 0$, we must have

$$1 + (\omega_c R_{Th}C)^2 = 2$$

$$\text{or } (\omega_c R_{Th}C)^2 = 1 \quad \text{or } \omega_c R_{Th}C = \pm 1$$

$$\text{We must have } \omega_c R_{Th}C = +1 \text{ or } \omega_c = \frac{1}{R_{Th}C} = \frac{1}{55\Omega \cdot 3nF} = 6 \text{ Mr/s}$$