

For above bandpass filter find:

- a) ω_0 b) f_0 c) Q d) ω_{c1} e) f_{c1} f) ω_{c2} g) f_{c2} h) β

- ans: a) $\omega_0 = 1 \text{ M rad/s}$ d) $\omega_{c1} = 936 \text{ krad/s}$ g) $170 \text{ kHz} = f_{c2}$
 b) $f_0 = 159 \text{ kHz}$ e) $f_{c1} = 149 \text{ kHz}$ h) $\beta = 21.2 \text{ kHz}$
 c) $Q = 7.5$ f) $\omega_{c2} = 1.07 \text{ Mrad/s}$

sol'n: a) Derive the transfer function, $H(s=j\omega)$, and determine definitions of ω_0 and Q (for the sake of pedagogy).

We have a V-divider circuit:

$$V_o = V_i \cdot \frac{z_L \parallel z_C}{z_L \parallel z_C + R} \quad z_L \parallel z_C = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{L/C}{j(\omega L - 1/\omega C)}$$

$$H(j\omega) \equiv \frac{V_o}{V_i} = \frac{z_L \parallel z_C}{z_L \parallel z_C + R} = \frac{L/C}{\frac{L/C}{j(\omega L - 1/\omega C)} + R}$$

$$H(j\omega) = \frac{L/C}{L/C + R j(\omega L - 1/\omega C)} = \frac{1}{1 + jR(\omega C - 1/\omega L)}$$

The center frequency, ω_0 , is defined as: (for bandpass)

- 1) The frequency where $H(j\omega)$ is purely Real
 or 2) " " " $\angle H(j\omega) = 0$ (i.e. same as (1))
 or 3) " " " $|H(j\omega)|$ is maximum.

The third definition captures the concept of finding the ω that maximizes the magnitude gain.

(1) and (2) are equivalent to (3) by the following argument:

1) The max of $|H(j\omega)|$ occurs where $|H(j\omega)|^2$ is max.


$$\begin{aligned}
 2) \quad |H(j\omega)|^2 &= \frac{1}{\underbrace{\operatorname{Re}[H(j\omega)]^2}_{\text{denom}} + \underbrace{\operatorname{Im}[H(j\omega)]^2}_{\text{denom}}} \quad (\text{for } H(j\omega) \text{ in this prob.}) \\
 &= \frac{1}{\underbrace{1}_{\operatorname{Re}^2} + \underbrace{R^2(\omega C - 1/\omega L)^2}_{\operatorname{Im}^2}}
 \end{aligned}$$

3) Since ω only appears in Im^2 term, and since $\operatorname{Im}^2 \geq 0$ (squared real is ≥ 0), it follows that the smallest denominator for $H(j\omega)$ occurs when $\operatorname{Im}^2 = 0$.

$$\therefore \omega_0 C = \frac{1}{\omega_0 L} \quad \text{or} \quad \omega_0^2 = \frac{1}{LC} \quad \text{or} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

This works for $H(j\omega)$ of a certain form (that we always obtain for bandpass and bandreject filters). Suppose, however, that we were faced with the problem of finding $|H(j\omega)|$ max over ω for some other $H(j\omega)$. What might we do? We illustrate some useful tricks in the following derivation, (which is still tailored to the $H(j\omega)$ for this problem).

From calculus, max $|H(j\omega)|$ occurs when $\frac{d|H(j\omega)|}{d\omega} = 0$;

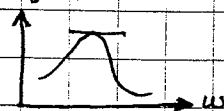

i.e. slope = 0 at max.

Unfortunately $\frac{d|H(j\omega)|}{d\omega}$ is messy; it has a $\frac{1}{\sqrt{\quad}}$ form.

To simplify matters, we observe that $\max_{\omega} |H(j\omega)|$

and $\max_{\omega} |H(j\omega)|^2$ occur at the same value of ω .

\therefore we solve $\frac{d}{d\omega} |H(j\omega)|^2 = 0$.

To simplify matters further, we write $|H(j\omega)|^2 = \frac{1}{G(j\omega)}$

where $G(j\omega) \equiv \text{denominator of } |H(j\omega)|^2 \equiv 1 + R^2(\omega C - 1/\omega L)^2$.

\therefore we solve $\frac{d}{d\omega} \frac{1}{G(j\omega)} = 0$

But this means, by the chain rule, that we have:

$$\frac{d}{d\omega} \frac{1}{G(j\omega)} = -\frac{1}{G(j\omega)^2} \frac{d}{d\omega} G(j\omega) = 0$$

So long as we avoid ω 's for which $G(j\omega)^2 = \infty$ (namely $\omega=0$ and $\omega=\infty$) we need only solve

$$\frac{d}{d\omega} G(j\omega) = 0 \quad (\text{i.e. either } -\frac{1}{G(j\omega)^2} = 0 \text{ or } \frac{d}{d\omega} G(j\omega) = 0).$$

$$\therefore 0 = \frac{d}{d\omega} G(j\omega) = \frac{d}{d\omega} [1 + R^2(\omega C - 1/\omega L)^2] = R^2 2(\omega C - 1/\omega L) \cdot \frac{d}{d\omega} (\omega C - 1/\omega L)$$

$$\text{or } 0 = R^2 \underbrace{2(\omega C - 1/\omega L)}_{\text{"0" or "0"}} \underbrace{(C + 1/\omega^2 L)}_{\text{"0"}}$$

Since $C, L, \omega \geq 0$ we can't have $C + 1/\omega^2 L = 0$.

$\therefore \omega_0 C - 1/\omega_0 L = 0$ or $\omega_0^2 = 1/LC$ or $\omega_0 = 1/\sqrt{LC}$.

Plug in #'s: $\omega_0 = \frac{1}{\sqrt{40\mu \cdot 25n}} = \frac{1}{\sqrt{1k\mu n}} = 1M \text{ rad/s}$

b) $\omega = 2\pi f \Rightarrow f_0 = \frac{\omega}{2\pi} = \frac{1M/s}{2\pi} = 159k/s \text{ or } 159 \text{ kHz}$

c) $Q \equiv \frac{f_0}{f_2 - f_1} = \frac{\text{center freq}}{\text{higher cutoff freq} - \text{lower cutoff freq}}$

To find the Q , we could use book formulas, but we'll derive f_{c1} and f_{c2} here.

By definition ω_{c1}, ω_{c2} are the frequencies where $|H(j\omega)| = \frac{1}{\sqrt{2}} |H(j\omega)|_{\text{max}}$

Since $\max_{\omega} |H(j\omega)| = 1$ we have:

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} \quad \text{or} \quad |H(j\omega_c)|^2 = \frac{1}{2}$$

$$\text{or} \quad \frac{1}{|H(j\omega_c)|^2} = 2 \quad \text{or} \quad 1 + R^2(\omega C - 1/\omega L)^2 = 2$$

$$\text{or} \quad R^2(\omega C - 1/\omega L)^2 = 1$$

We take the square root of both sides, and we must allow for a \pm or $-$ square root

$$R(\omega C - 1/\omega L) = \pm 1$$

Multiply both sides by $\frac{\omega}{RC}$:

$$\omega^2 - \frac{1}{LC} = \pm \frac{\omega}{RC} \quad \text{or} \quad \omega^2 \pm \frac{\omega}{RC} - \frac{1}{LC} = 0$$

Because of the $\pm \frac{\omega}{RC}$ term, we have two quadration

equations — each with two roots:

$$\omega_c = \frac{\pm 1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \quad \text{Are there four solutions? No!}$$

Since $\omega_c \geq 0$, there are only two solutions.

Since $\sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \geq \frac{1}{2RC}$ the two positive solutions are:

$$\omega_{c1} = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \quad \frac{1}{2RC} = \frac{1}{2 \cdot 300 \cdot 25n} = 66.7k/s$$

$$\omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \quad \frac{1}{LC} = (1M/s)^2$$

Now we may compute β and Q :

$$\beta = \omega_{c2} - \omega_{c1} = \frac{1}{RC}$$

$$Q = \frac{\omega_0}{\beta} = \frac{1}{\sqrt{LC}} = \frac{RC}{\sqrt{LC}} = R \sqrt{\frac{C}{L}}$$

Now we plug in #'s:

$$Q = 300 \cdot \frac{\sqrt{25n}}{\sqrt{40\mu}} = 7.5$$

$$d) \omega_{c1} = -66.7k + \sqrt{(66.7k)^2 + (1M)^2} / s = -66.7k + 1M = 933k/sec$$

small re (1M)²

Note: Ignoring the 66.7k inside the $\sqrt{\quad}$ results in an error of 3k/sec in our answer. The correct value is 936k/sec. The source of this error is also attributable to taking the difference of two values. Any errors in terms we take the difference of gets magnified. For example $1.0001M - 1.0000M = 100$, whereas $1.0001M - 1.00000M = 10$. A tiny change in the first quantity, (i.e. a 0.001% change) results in a 10% change in the outcome.

$$e) f_{c1} = \frac{\omega_{c1}}{2\pi} = \frac{936 \text{ k/s}}{2\pi} = 149 \text{ kHz}$$

$$f) \omega_{c2} = 66.7 \text{ k/s} + \sqrt{\underbrace{(66.7 \text{ k/s})^2}_{\text{small}} + (1 \text{ M/s})^2} = 1.07 \text{ M/s}$$

$$g) f_{c2} = \frac{\omega_{c2}}{2\pi} = \frac{149 \text{ kHz}}{2\pi} = 170 \text{ kHz}$$

$$h) \beta = \frac{1}{2\pi \cdot RC} \text{ Hz} = \frac{1}{2\pi \cdot 300 \cdot 25 \text{ n}} \text{ Hz} = 21.2 \text{ kHz}$$

Note: If we use $\frac{\omega_{c2} - \omega_{c1}}{2\pi} = \frac{1.07 \text{ M} - 933 \text{ k}}{2\pi} = 21.8 \text{ kHz}$,

a less accurate value. Again, problems arise from taking the (small) difference of two large values.