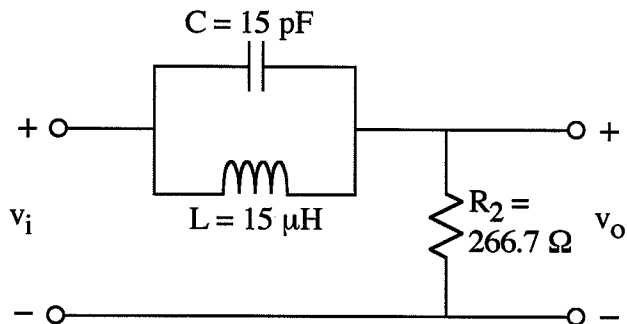



Ex:



For the band-reject filter shown above, calculate the following quantities:

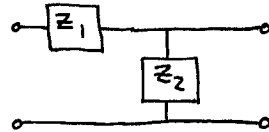- a) ω_0
- b) f_0
- c) ω_{C1} and ω_{C2} .
- d) β and Q

so(n: a) $\omega_0^2 = \frac{1}{LC}$ for RLC filters of simple form:



Z_1	Z_2
R	$\frac{1}{sC} + sL$
R	$\frac{1}{sC} \parallel sL$
$\frac{1}{sC} + sL$	$\frac{1}{sC} \parallel sL$
$\frac{1}{sC} \parallel sL$	R

$$\omega_0^2 = \frac{1}{15\mu\text{H} \cdot 15\text{pF}} = \frac{1}{(15\text{nS})^2}$$

$$\omega_0 = \frac{1}{15\text{nS}} = 66.7 \text{ Mr/s}$$

b) $f = \frac{\omega}{2\pi}$ $f_0 = \frac{\omega_0}{2\pi} = \frac{66.7 \text{ Mr/s}}{2\pi} = 10.6 \text{ Mr/s}$

c) $\omega_{C1, C2}$ are the frequencies where the magnitude of $H(s)$ is reduced by a factor of $\sqrt{2}$ relative to its max.

$$H(s) = \frac{R_2}{R_2 + sL \parallel \frac{1}{sC}}$$

$$sL \parallel \frac{1}{sC} = \frac{1}{\frac{1}{sL} + \frac{1}{\frac{1}{sC}}} = \frac{1}{\frac{1}{sL} + sC} = \frac{1}{j(\omega C - \frac{1}{\omega L})}$$

$$H(s) = \frac{R_2}{R_2 - j \frac{1}{\omega C - \frac{1}{\omega L}}}$$

We write $H(s)$ in form $H(s) = k \cdot \frac{1}{1 + jX}$

where $k \equiv \text{real}$ and $X \equiv \text{real}$.

$$H(s) = \frac{R_2}{R_2} \cdot \frac{1}{1 - j \frac{1}{R_2} \cdot \frac{1}{\omega C - \frac{1}{\omega L}}}$$

$$\max_{\omega} |H(s)| = 1 \quad \text{when } \omega = 0 \text{ (L = wire)} \\ \text{or } \omega \rightarrow \infty \text{ (C = wire)}$$

$$\text{Thus, } |H(j\omega_c)| = \frac{1}{\sqrt{2}} \cdot 1$$

$$\text{It follows that } \frac{1}{\left| 1 - j \frac{1}{R_2} \cdot \frac{1}{\omega_c C - \frac{1}{\omega_c L}} \right|} = \frac{1}{\sqrt{2}}$$

$$\text{or } 1 - j \frac{1}{R_2} \frac{1}{\omega_c C - \frac{1}{\omega_c L}} = 1 \pm j$$

$$\text{or } R_2 \left(\omega_c C - \frac{1}{\omega_c L} \right) = \pm 1$$

We rewrite this as a quadratic eqn.

Multiply both sides by $\frac{\omega_c}{RC}$, move $\pm \frac{\omega_c}{RC}$ to left.

$$\omega_c^2 \pm \frac{\omega_c}{RC} - \frac{1}{LC} = 0$$

$$\omega_{c1,2} = \pm \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

We must use $+\sqrt{\quad}$ since ω_c values must be > 0 .

$$\frac{1}{2RC} = \frac{1}{2 \cdot 266.7 \Omega \cdot 15 \text{ pF}} = \frac{1}{2 \cdot \frac{8}{3} \cdot 100 \Omega \cdot 5 \cdot 10^{-8} \text{ pF}}$$

$$= \frac{16}{8} = 125 \text{ Mr/s} = 25 \cdot \frac{15}{3} \text{ Mr/s}$$

$$\frac{1}{LC} = \omega_0^2 = (66.7 \text{ Mr/s})^2 = \left(\frac{200}{3} \text{ Mr/s}\right)^2$$

$$\sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} = \sqrt{125^2 + 66.7^2} \text{ Mr/s}$$

$$= \sqrt{\left(25 \cdot \frac{15}{3}\right)^2 + \left(25 \cdot \frac{8}{3}\right)^2} \text{ Mr/s}$$

$$= \frac{25 \cdot 17}{3} \text{ Mr/s}$$

$$\omega_{c1} = \frac{25}{3} (-15 + 17) \text{ Mr/s} = \frac{50}{3} \text{ Mr/s}$$

$$\omega_{c2} = \frac{25}{3} (15 + 17) \text{ Mr/s} = \frac{800}{3} \text{ Mr/s}$$

$$\omega_{c1} = 16.7 \text{ Mr/s} \quad \omega_{c2} = 266.7 \text{ Mr/s}$$

d) $\beta = \omega_{c2} - \omega_{c1} = \frac{1}{RC} = 2 \cdot \frac{1}{2RC} = 250 \text{ Mr/s}$

$$Q = \frac{\omega_0}{\beta} = \frac{66.7 \text{ Mr/s}}{250 \text{ Mr/s}} = 0.267$$