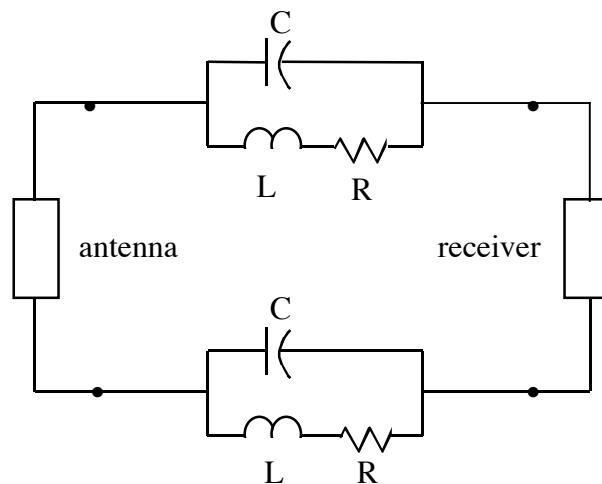


**EX:** The circuit shown below is a wave trap, used to prevent the signal from an amateur radio transmitter from entering the input of a TV receiver. Choose proper values of  $L$  and  $C$  if the transmitter frequency is 50 MHz, and  $R$  does not affect the resonant frequency appreciably. Explain how the circuit works. The bottom edge of Channel 2 is at 54 MHz.

What value of  $R$  would be required to make  $|Z|$  at 54 MHz of one of the resonant circuits equal to 1/10 of its value at resonance and what value of impedance would that be at 54 MHz?

Note: the frequencies here are in units of Hz rather than rad/s.



**ANS:** There is no unique answer. For  $C = 100 \text{ pF}$ , then  $L = 0.101 \text{ } \mu\text{H}$ ,  $R \approx 0.492 \text{ } \Omega$ ,  $|Z| \approx 205 \text{ } \Omega$  at 54 MHz.

**SOL'N:** The idea is that  $L$  parallel  $C$  will act like an open circuit at resonance. This prevents the interfering signal from reaching the receiver. With the  $R$  included, (but relatively small), the resonant frequency remains approximately the same:

$$\omega_o \equiv \frac{1}{\sqrt{LC}}$$

In units of Hz, we have

$$f_o \equiv \frac{\omega_o}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

Any L and C satisfying the following equation will yield the correct resonant frequency:

$$LC = \frac{1}{(2\pi f_o)^2} = \frac{1}{(2\pi 50 \cdot 10^6)^2} \text{ s}^2 \approx 10.1 \cdot \mu\text{ps}^2$$

One solution is C = 100 pF and L = 0.101  $\mu$ H.

Now we find the value for R.

At resonance, we have equal but opposite reactances for the L and C.

Define the reactances at  $\omega_o$  to be +jX and -jX. From the definition of  $\omega_o$ , we have  $X = \sqrt{L/C} = 31.8 \Omega$ .

At  $\omega_o$ , the impedance,  $z_o$ , of one side of the trap circuit, (i.e., one C in parallel with an L plus an R), is

$$z_o = \frac{(R + jX)(-jX)}{R + jX - jX} = \frac{X^2 - jRX}{R} = X \left( \frac{X}{R} - j \right).$$

For a frequency,  $k\omega_o$ , our L and C reactances become  $jkX$  and  $-jX/k$ , and we have

$$z_k = \frac{(R + jkX)(-jX/k)}{R + jkX - jX/k} = \frac{X^2 - jRX/k}{R + jX(k - 1/k)} = X \left( \frac{X - jR/k}{R + jX(k - 1/k)} \right),$$

or

$$z_k = X \left( \frac{\frac{X}{R} - j\frac{1}{k}}{1 + j\frac{X}{R}(k - 1/k)} \right).$$

We want  $|z_k/z_o| = 1/10$  when  $k = 54 \text{ MHz}/50 \text{ MHz} = 1.08$ .

If we define  $B \equiv X/R$ , we have

$$\frac{|z_k|}{|z_o|} = \frac{\left| \frac{B - j\frac{1}{k}}{1 + jB(k - \frac{1}{k})} \right|}{|B - j|} = \frac{1}{10}.$$

At this point, it is prudent to attempt an approximation. Because  $k \approx 1$ , we may approximate  $B - j/k$  as  $B - j$  and cancel terms to obtain a simpler equation:

$$\frac{|z_k|}{|z_o|} \approx \frac{1}{\left| 1 + jB(k - \frac{1}{k}) \right|} = \frac{1}{10}.$$

Inverting both sides and applying the definition of magnitude, we have

$$\left| 1 + jB(k - \frac{1}{k}) \right| = \sqrt{1^2 + \left[ B(k - \frac{1}{k}) \right]^2} = 10.$$

Solving for B, we have

$$\left[ B(k - \frac{1}{k}) \right]^2 = 99 \quad \text{or} \quad B = \frac{\sqrt{99}}{k - \frac{1}{k}} = \frac{\sqrt{99}}{1.08 - \frac{1}{1.08}} \approx 64.58.$$

Using  $R = X/B = 31.8 \Omega / 64.58$ , we have  $R = 0.492 \Omega$ .

At 54 MHz, we have

$$|z_k| = X \frac{\left| B - j\frac{1}{k} \right|}{\left| 1 + jB(k - 1/k) \right|} = X \frac{\left| B - j\frac{1}{k} \right|}{10} \approx X \frac{|B|}{10} = 31.8\Omega \frac{64.58}{10}$$

We obtain  $|z_k| \approx 205 \Omega$  at 54 MHz.