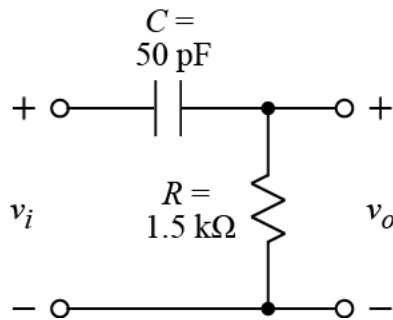


Ex:



$$v_i(t) = -4 + 2 \sum_{k=1}^{\infty} \frac{1}{k^2 + 1} \sin(k\omega_0 t) \text{ V}$$

Write the time-domain expression of the third harmonic (i.e., $k = 3$) of $v_o(t)$.

Note: $\omega_0 = \frac{10}{3} \text{ M r/s}$ for the Fourier series.

SOL'N: The third harmonic of $v_o(t)$, denoted here by $v_{i3}(t)$, is the response of the circuit to the third harmonic of the input signal,

$$v_{i3}(t) = 2 \cdot \frac{1}{k^2 + 1} \sin(k\omega_0 t) \Big|_{k=3} \text{ V.}$$

or

$$v_{i3}(t) = \frac{2}{10} \sin(3\omega_0 t) \text{ V} = \frac{1}{5} \sin\left(3 \cdot \frac{10 \text{ M}}{3} t\right) \text{ V}$$

or

$$v_{i3}(t) = \frac{1}{5} \sin(10 \text{ M} t) \text{ V}$$

We convert $v_{i3}(t)$ to a phasor, V_{i3} , and compute impedance values for $\omega = 3\omega_0 = 10 \text{ M r/s}$.

$$V_{i3} = -j \frac{1}{5}$$

$$\frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{-j \text{ } \Omega}{10 \text{ M} \cdot 50 \text{ p}} = -j 2 \text{ k} \Omega$$

The output phasor, V_{o3} , is found using a voltage-divider formula.

$$\begin{aligned}
 V_{o3} &= V_{i3} \cdot \frac{R}{R + \frac{1}{j\omega C}} = -j \frac{1}{5} \frac{1.5K}{1.5K - j2K} \text{ V} \\
 &= -j \frac{1}{5} \frac{3}{3-j4} \text{ V} = -j \frac{1}{5} \frac{3}{3-j4} \frac{3+j4}{3+j4} \text{ V} \\
 &= -j \frac{1}{5} \frac{3(3+j4)}{25} \text{ V} = \frac{1}{125} (12-j9) \text{ V} \\
 &= \frac{8(12-j9)}{8(125)} \text{ V} = 8(12-j9) \text{ mV} \\
 V_{o3} &= 96 - j72 \text{ mV}
 \end{aligned}$$

Thus, $v_{o3}(t) = 96 \text{ mV} \cos(10Mt) + 72 \text{ mV} \sin(10Mt)$

or $v_{o3}(t) = 120 \text{ mV} \cos(10Mt - 37^\circ)$