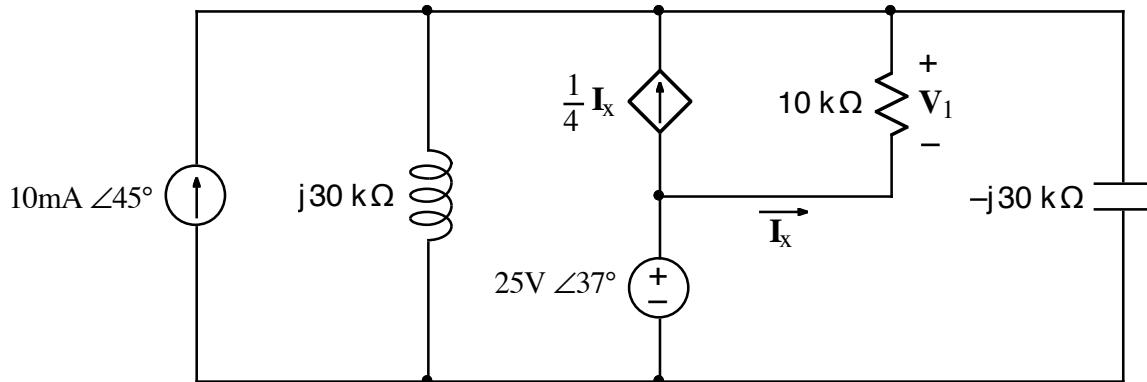


Ex:



- A frequency-domain circuit is shown above. Write the value of phasor \mathbf{V}_1 in polar form.
- Given $\omega = 25\text{ k rad/s}$, write a numerical time-domain expression for $v_1(t)$, the inverse phasor of \mathbf{V}_1 .

Sol'n: a) First, we eliminate unnecessary components. The $j30\text{ k}\Omega$ and $-j30\text{ k}\Omega$ in parallel behave like an open circuit:

$$\begin{aligned} j30\text{ k}\Omega \parallel -j30\text{ k}\Omega &= j30\text{ k}\Omega \cdot 1 \parallel -1 \\ &\approx j30\text{ k}\Omega \cdot \frac{-1}{0} \\ &= -j\infty\text{ }\Omega \text{ (open circuit)} \end{aligned}$$

Second, we convert the dependent source to an equivalent impedance. The voltage across the dependent source equals $-V_1$, which equals $-\mathbb{I}_x \cdot 10\text{ k}\Omega$.


$$V_1 = -\mathbb{I}_x \cdot 10\text{ k}\Omega$$

$$\text{Thus, } z_{eq} = \frac{-V_1}{\frac{1}{4}\mathbb{I}_x} = \frac{\mathbb{I}_x \cdot 10\text{ k}\Omega}{\frac{1}{4}\mathbb{I}_x} = 40\text{ k}\Omega.$$

The Reg in parallel with $10\text{ k}\Omega$ gives

$$\begin{aligned} 40\text{ k}\Omega \parallel 10\text{ k}\Omega &= 10\text{ k}\Omega \cdot 4 \parallel 1 \\ &= 10\text{ k}\Omega \cdot \frac{4}{5} \\ &= 8\text{ k}\Omega \end{aligned}$$

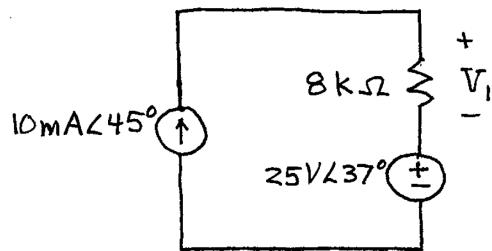Our circuit model is now much simpler than before:



Now we see that the V source has no effect, as it is in series with a current source.

$$V_1 = 10\text{ mA} \angle 45^\circ \cdot 8\text{ k}\Omega$$

$$V_1 = 80\text{ V} \angle 45^\circ$$

b) $v_1(t) = P^{-1}[V_1] = P^{-1}[80\text{ V} \angle 45^\circ] \quad \omega = 25\text{ rad/s}$

$$v_1(t) = 80 \cos(\omega t + 45^\circ)\text{ V} = 80 \cos(25t + 45^\circ)\text{ V}$$