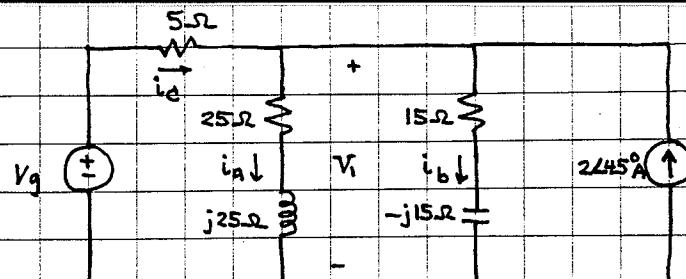


ex:



Given $I_b = 5 \angle 45^\circ A$ is phasor for current i_b .

a) Find: I_a , I_c , and V_g phasors.

sol'n: Define phasor voltage V_1 as shown.

$$V_1 = I_b \cdot (15\Omega - j15\Omega) \quad \text{Ohm's Law}$$

$$\text{and } V_1 = I_a \cdot (25\Omega + j25\Omega) \quad " " \text{ same } V$$

$$\therefore I_a = I_b \frac{15\Omega - j15\Omega}{25\Omega + j25\Omega} = I_b \frac{15}{25} \frac{1-j}{1+j}$$

$$\begin{aligned} 1+j &\text{ in first quadrant, } \theta = \pi/4 \\ 1-j &\text{ in fourth quadrant, } \theta = -\pi/4 \\ \frac{1-j}{1+j} &= \frac{\sqrt{2}e^{-j\pi/4}}{\sqrt{2}e^{j\pi/4}} = e^{-j\pi/2} = -j \end{aligned}$$

$$\begin{aligned} \therefore I_a &= I_b \frac{15}{25} (-j) & -j &= 1 \angle -90^\circ \\ &= 5 \angle 45^\circ \cdot \frac{3}{5} \cdot 1 \angle -90^\circ & &= 5 \cdot \frac{3}{5} \cdot 1 \angle 45^\circ - 90^\circ \\ &= 3 \angle -45^\circ A \end{aligned}$$

Now sum currents for V_1 node:

$$\begin{aligned} I_c &= I_a + I_b - 2 \angle 45^\circ A = 3 \angle -45^\circ + 5 \angle 45^\circ - 2 \angle 45^\circ A \\ &= 3 \angle -45^\circ + 3 \angle -45^\circ A \quad \text{same angle, can add magnitudes} \\ &= 3\sqrt{2} \angle 0^\circ A \end{aligned}$$

$$\begin{aligned} V_g &= I_c \cdot 5\Omega + I_b (15 - j15\Omega) = 3\sqrt{2} \cdot 5\Omega + 5 \angle 45^\circ \cdot 15\sqrt{2} \angle -45^\circ V \\ &= 15\sqrt{2} V + 7.5\sqrt{2} V = 90\sqrt{2} V \end{aligned}$$

$5 \cdot 15\sqrt{2} \angle 45^\circ - 45^\circ$

b) If $\omega = 800 \text{ rad/s}$, write expressions for $i_L(t)$, $i_C(t)$, $v_g(t)$.

$$\text{Sol'n: } I_L = 3\angle -45^\circ \text{ A} \quad -45^\circ = -\frac{\pi}{4} \text{ rad}$$

$$\therefore i_L(t) = 3 \cos\left(\omega t - \frac{\pi}{4}\right)$$

$$I_C = 3\sqrt{2} \angle 0^\circ \text{ A}$$

$$\therefore i_C(t) = 3\sqrt{2} \cos(\omega t)$$

$$V_g = 90\sqrt{2} \text{ V} \quad \text{or} \quad 90\sqrt{2} \angle 0^\circ \text{ V}$$

$$\therefore v_g(t) = 90\sqrt{2} \cos(\omega t)$$