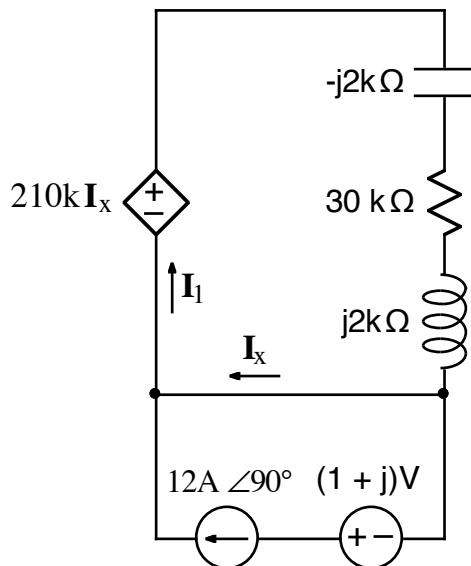


Ex:




- A frequency-domain circuit is shown above. Write the value of phasor \mathbf{I}_1 in polar form.
- Given $\omega = 2\text{k rad/s}$, write a numerical time-domain expression for $i_1(t)$, the inverse phasor of \mathbf{I}_1 .

Sol'n: a) We first eliminate unnecessary components:

- The $-j2k\Omega$ and $j2k\Omega$ sum to 0Ω and act like a wire.
- The $(1+j)V$ source is in series with a current source, allowing us to ignore it.

New circuit model:

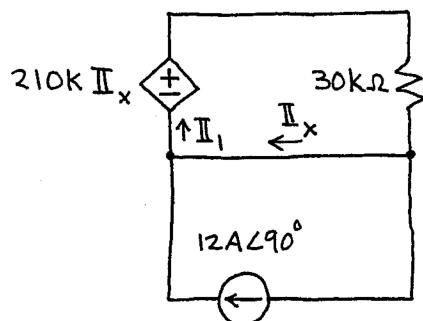

Using a current summation at the left node, we have one egn in two unknowns:

$$(1) \quad 12A \angle 90^\circ + \mathbb{I}_x = \mathbb{I}_1$$

Using a voltage loop around the top half of the circuit, we get a 2nd egn in two unknowns:

$$(2) \quad \mathbb{I}_1 = \frac{210k\mathbb{I}_x}{30k\Omega}$$

We solve egn (1) for \mathbb{I}_x :

$$(1') \quad \mathbb{I}_x = \mathbb{I}_1 - 12A \angle 90^\circ$$

Substituting into (2) gives an egn for \mathbb{I}_1 :

$$(2') \quad \mathbb{I}_1 = \frac{210k}{30k\Omega} (\mathbb{I}_1 - 12A \angle 90^\circ) = 7(\mathbb{I}_1 - 12A \angle 90^\circ)$$

$$(2'') \quad 6\mathbb{I}_1 = 12A \angle 90^\circ$$

$$(2''') \quad \mathbb{I}_1 = 2A \angle 90^\circ$$

$$c) \quad i_1(t) = P^{-1}[\mathbb{I}_1] = P^{-1}[2A \angle 90^\circ]$$

$$i_1(t) = 2 \cos(\omega t + 90^\circ) A = 2 \cos(2kt + 90^\circ) A$$