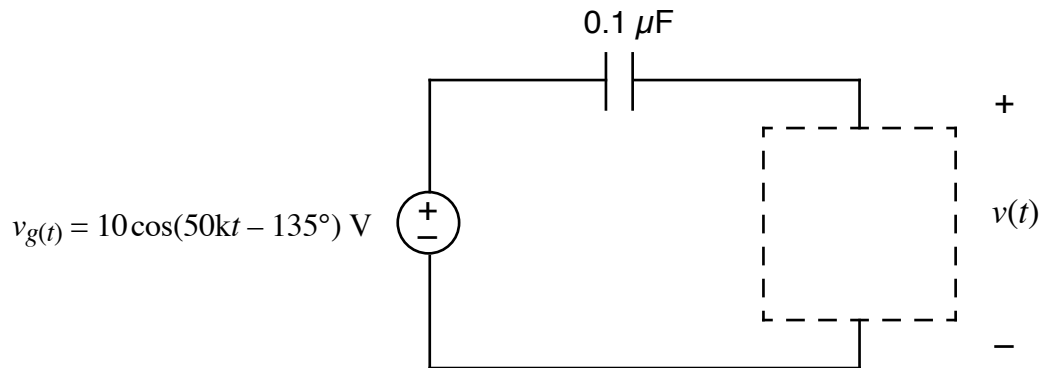


Ex:




- Choose an R, an L, or a C to be placed in the dashed-line box to make $v(t) = V_o \sin(50kt)$ where V_o is a positive real constant (with units of Volts). State the value of the component you choose.
- With your component from (a) in the circuit, calculate the resulting value of V_o .

Sol'n: a) We first transform the circuit to the frequency domain.

$$V_g = 10 \angle -135^\circ \text{ V} \quad V = V_o \angle -90^\circ \text{ since } P[\sin \omega t] = -j \text{ or } 1 \angle -90^\circ$$

$$Z_c = \frac{-j}{\omega C} = \frac{-j}{50\text{K} \cdot 0.1 \mu\text{F}} = \frac{-j \Omega}{5\text{m}} = -j200 \Omega$$

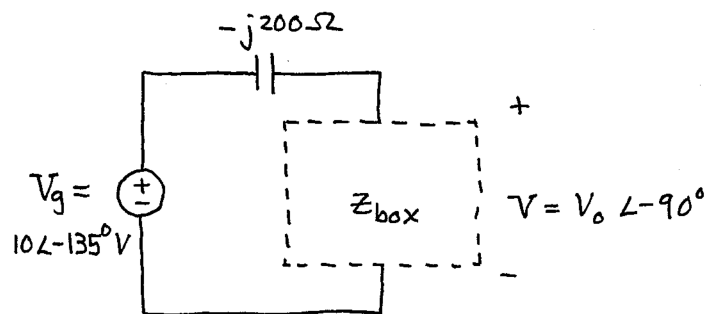Note: $\omega = 50 \text{ k r/s}$ from $v_g(t)$ and $v(t)$.



Now we consider phase relationships.

$$V = V_g \cdot \frac{z_{\text{box}}}{z_{\text{box}} - j200\Omega} \quad \text{from } V\text{-divider}$$

$$\angle V = \angle V_g + \angle z_{\text{box}} - \angle (z_{\text{box}} - j200\Omega)$$

$$\begin{aligned} & \parallel \\ -90^\circ &= -135^\circ + \angle z_{\text{box}} - \angle (z_{\text{box}} - j200\Omega) \end{aligned}$$

$$\text{Thus, } \angle z_{\text{box}} - \angle (z_{\text{box}} - j200\Omega) = 45^\circ.$$

Consider possible contents of z_{box} .

If $z_{\text{box}} = j\omega L$ or $\frac{-j}{\omega C}$, then all z values in the circuit are pure imaginary.

Thus, $\angle z_{\text{box}} - \angle (z_{\text{box}} - j200\Omega)$ would

be some multiple of 90° . It follows that z_{box} must be an R value.


$$\therefore \text{ Let } z_{\text{box}} = R. \quad \angle R = 0^\circ$$

$$\text{Then } \angle z_{\text{box}} - \angle (z_{\text{box}} - j200\Omega) = 45^\circ$$

$$= 0^\circ - \angle (R - j200\Omega)$$

$$\text{or } \angle (R - j200\Omega) = -45^\circ$$

Now we can find R graphically.

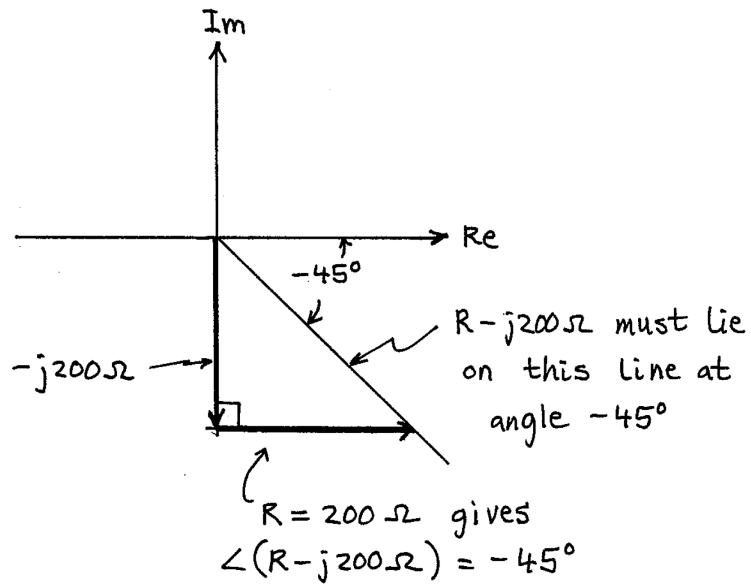

$$Z_{box} = R = 200\Omega$$

b) To find V_o , we use magnitude.

$$\begin{aligned}
 V_o = |V| &= \left| V_g \cdot \frac{Z_{box}}{Z_{box} - j200\Omega} \right| \\
 &= \left| V_g \frac{R}{R - j200\Omega} \right| \\
 &= \left| V_g \frac{200\Omega}{200\Omega - j200\Omega} \right| \\
 &= \frac{|110V| \cdot |200\Omega|}{|200\Omega - j200\Omega|}
 \end{aligned}$$

$$= \frac{10V \cdot 200}{200 |1-j|}$$

$$= \frac{10V}{|1-j|}$$

$$= \frac{10V}{\sqrt{2}}$$

$$V_o = \frac{10}{\sqrt{2}} V$$