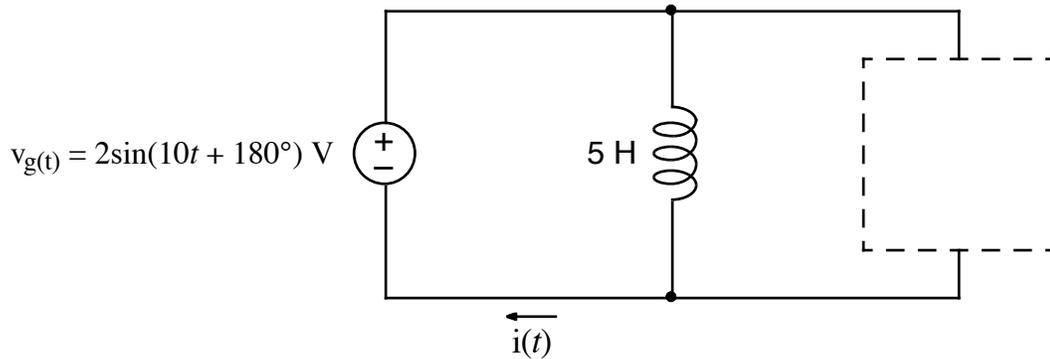


Ex:



- a) Choose an R, an L, or a C to be placed in the dashed-line box to make
- $$i(t) = I_o \cos(10t + 45^\circ) \text{ A}$$
- where  $I_o$  is a real constant. State the value of the component you choose.
- b) With your component in the circuit, calculate the resulting value of  $I_o$ .


Sol'n: a) Transform to frequency domain.

$$V_g = -j2 e^{j180^\circ} \text{ V} \text{ since } P[\sin(\omega t)] = -j$$

$$V_g = +j2 \text{ V} = 2 \angle 90^\circ \text{ V}$$

$$z_L = j\omega L = j \cdot 10 \text{ r/s} \cdot 5 \text{ H} = j50 \Omega$$

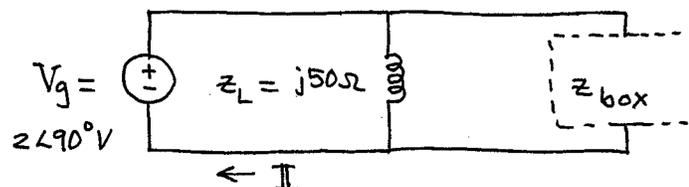Note:  $\omega = 10 \text{ r/s}$  from  $v_g(t)$ .



$$\text{We have } I = \frac{V_g}{z_L \parallel z_{\text{box}}}$$

In terms of angles:

$$\angle \mathbf{I} = 45^\circ \quad \text{from} \quad i(t) = I_0 \cos(10t + 45^\circ) \text{ A}$$

$$\angle \mathbf{I} = 45^\circ = \angle V_g - \angle(z_L \parallel z_{box})$$

$$\text{or} \quad 45^\circ = 90^\circ - \angle(z_L \parallel z_{box})$$

$$\text{Thus,} \quad \angle(z_L \parallel z_{box}) = 45^\circ.$$

For parallel components, it is easier to use conductance =  $\frac{1}{z} \equiv g$

$$g_L = \frac{1}{z_L} \quad g_{box} = \frac{1}{z_{box}}$$

$$\angle(z_L \parallel z_{box}) = -\angle\left(\frac{1}{z_L \parallel z_{box}}\right) = -\angle\left(\frac{1}{z_L} + \frac{1}{z_{box}}\right)$$

or


$$\angle\left(\frac{1}{z_L} + \frac{1}{z_{box}}\right) = -\angle(z_L \parallel z_{box}) = -45^\circ$$

or

$$\angle(g_L + g_{box}) = -45^\circ$$

Now we use a plot:
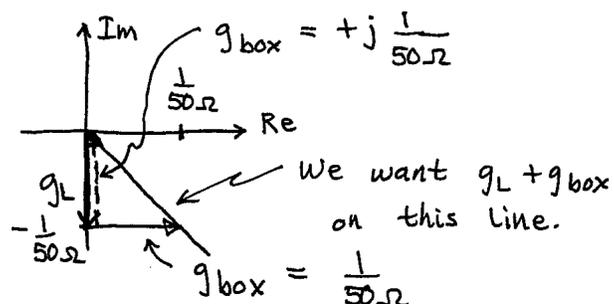
$$g_L = \frac{1}{j50\Omega} = -j \cdot \frac{1}{50\Omega}$$



We have two possible solutions:

$$1) \quad g_{\text{box}} = j \frac{1}{50 \Omega} \Rightarrow z_{\text{box}} = \frac{50 \Omega}{j} = -j50 \Omega$$

$$\text{Need capacitor: } z_c = \frac{-j}{\omega C} = \frac{-j}{10 \cdot C} = -j50 \Omega$$

$$\Rightarrow C = \frac{1}{10 \cdot 50} \text{ F} = 2 \text{ mF}$$

$$\text{or } 2) \quad g_{\text{box}} = \frac{1}{50 \Omega} \Rightarrow z_{\text{box}} = 50 \Omega \text{ resistor}$$

Either sol'n is technically correct, but solution (1) gives  $g_L + g_{\text{box}} = 0 \Rightarrow z = \infty$ .

Thus, no current flows for this sol'n.

b) Now use magnitude.

$$|I| = \left| \frac{V_g}{z_L \parallel z_{\text{box}}} \right| = \frac{|V_g|}{|z_L \parallel z_{\text{box}}|}$$


$$\text{or } I_o = |V_g| \cdot |g_L + g_{\text{box}}|$$

$$I_o = 2 \cdot |g_L + g_{\text{box}}|$$

From diagram used to find  $g_L + g_{\text{box}}$

on  $-45^\circ$  line, use magnitude of vector

for  $g_L + g_{\text{box}}$ .

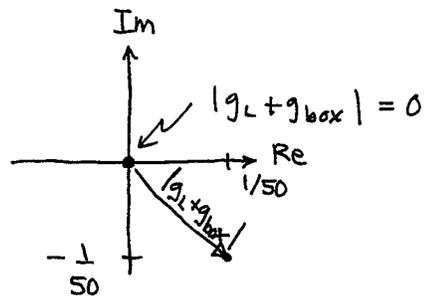

For sol'n (1),  $|g_L + g_{box}| = 0 \Rightarrow I_o = 0 \text{ A}$

For sol'n (2),  $|g_L + g_{box}| = \left| \frac{1}{50\Omega} - j \frac{1}{50\Omega} \right|$

$$= \left| \frac{1}{50\Omega} (1 - j) \right|$$

$$= \frac{1}{50\Omega} \sqrt{1^2 + 1^2}$$

$$= \frac{\sqrt{2}}{50\Omega}$$

$$\Rightarrow I_o = \frac{2 \cdot \sqrt{2} \text{ A}}{50} = \frac{\sqrt{2}}{25} \text{ A}$$