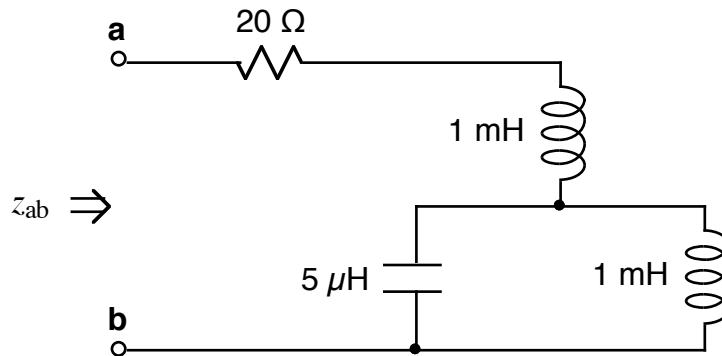


Ex:



Find a frequency,  $\omega$ , that causes  $z_{ab}$  to be real, (i.e., imaginary part equals zero).

$$\text{Sol'n: } z_{ab} = 20 \Omega + z_{L1} + z_C \parallel z_{L2}$$

For  $z_{ab}$  to be real, we must have

$$z_{L1} + z_C \parallel z_{L2} = \text{real}$$

One simple sol'n is to let  $\omega = 0$  so both L's act like wires and C acts like open circuit.

Other potential sol'ns are  $\omega = \infty$ , (so L's act like opens, resulting in  $z_{ab} = \infty$ ), and  $\omega = \text{frequency where } z_C = -z_{L2}$ , (so C and L in parallel have equal but opposite impedances).

The latter case, where  $z_C = -z_L$  gives

$$\text{the interesting result that } z_C \parallel z_L = \frac{L/C}{0} = \infty$$

This means  $z_{ab} = \infty \Omega$ . In this case, (unlike  $\omega \rightarrow \infty$ ),  $z_{ab} \rightarrow \infty$  along real axis as  $z_C \parallel z_L \rightarrow \infty$ .

Another sol'n is that  $z_c \parallel z_L$  has a value is minus  $z_L$  of the top inductor.

In that case,  $z_L + z_c \parallel z_L = 0$  and  $z_{ab} = 0 = \text{wire}$ .

$$z_L = j\omega L$$

$$\begin{aligned} z_c \parallel z_L &= \frac{-j}{\omega C} \parallel j\omega L = \frac{-j \cdot j\omega L}{\frac{-j}{\omega C} + j\omega L} = \frac{L/C}{j(\omega L - \frac{1}{\omega C})} \\ &= -j \frac{L/C}{\omega L - \frac{1}{\omega C}} \end{aligned}$$

$$\text{Thus, we want } j\omega L - \frac{jL/C}{\omega L - \frac{1}{\omega C}} = 0$$

$$\text{or } \omega L = \frac{L/C}{\omega L - \frac{1}{\omega C}}$$

$$\text{or } \omega L \left( \omega L - \frac{1}{\omega C} \right) = L/C$$

$$\text{or } \omega^2 L^2 - \frac{L}{C} = \frac{L}{C}$$

$$\text{or } \omega^2 L^2 = \frac{2L}{C} \quad \text{or } \omega^2 = \frac{2}{LC}$$

$$\text{or } \omega = \sqrt{\frac{2}{LC}} \quad \text{or } \omega = \sqrt{\frac{2}{5\mu\text{F} \cdot 1\text{mH}}}$$

$$\text{or } \omega = \sqrt{\frac{2 \text{ G}}{5}} \text{ r/s} = \sqrt{400\text{M}} \text{ r/s}$$

$$\text{or } \omega = 20\text{k} \text{ r/s}$$