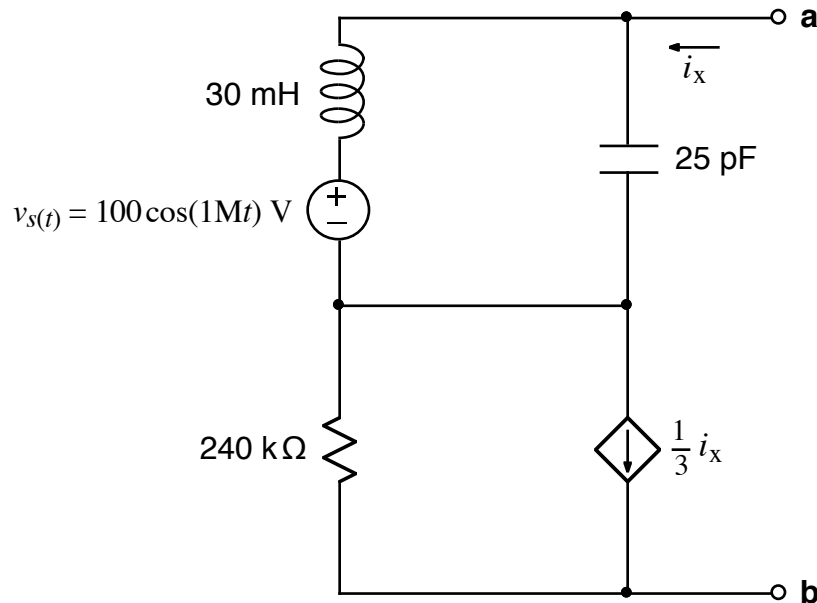


Ex:



- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for  $v_s(t)$ , and show numerical impedance values for R, L, and C. Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for  $V_{Th}$  and the numerical impedance value of  $Z_{Th}$ .


Sol'n: a) First, we find phasors and  $z$  values.

$$V_s = 100 \angle 0^\circ \text{ V} \quad \omega = 1 \text{ M r/s}$$

$$z_L = j\omega L = j 1 \text{ M r/s} \cdot 30 \text{ mH} = j 30 \text{ k}\Omega$$


$$z_C = \frac{-j}{\omega C} = \frac{-j}{1 \text{ M r/s} \cdot 25 \text{ pF}} = \frac{-j \Omega}{25 \mu} = -j 40 \text{ k}\Omega$$

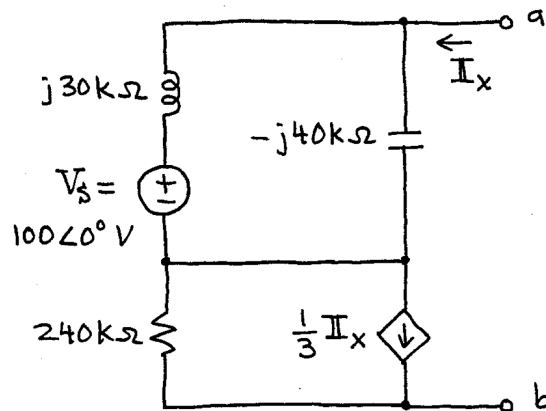Now we can draw the frequency domain model:



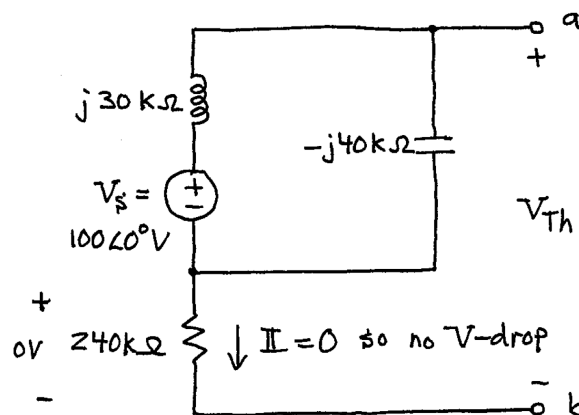b) We first find  $V_{Th} = V_{a,b}$  with no load connected across  $a, b$ .

In this case,  $I_x = 0 A$  since  $a, b = \text{open}$ .



$I_x = 0$  so dependent source disappears.

We have a  $V$ -divider:

$$V_{Th} = V_s \frac{-j40k\Omega}{-j40k\Omega + j30k\Omega} = V_s \frac{-j40k\Omega}{-j10k\Omega}$$


$$V_{Th} = 4V_s = 4(100\angle 0^\circ V)$$

$$V_{Th} = 400\angle 0^\circ V$$

To find  $z_{Th}$ , we replace the dependent source with an equivalent impedance.

We observe that, regardless of what is connected between **a** and **b**,  $I_x$  flows out of the **b** terminal, (and into the **a** terminal).

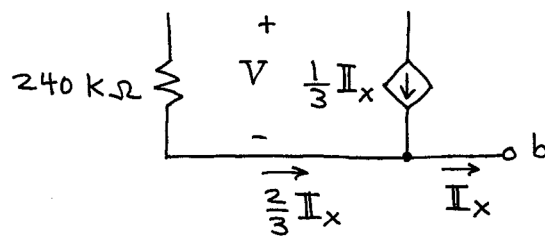Consider a current summation at the bottom node:



We have current  $\frac{2}{3}I_x$  through the  $240k\Omega$ .

The voltage across both the  $240k\Omega$  and the dependent source, by Ohm's law, will be  $V = \frac{2}{3}I_x \cdot 240k\Omega$ .

Thus, the equivalent impedance for the dependent source is found by using Ohm's law:

$$\begin{aligned} z_{eq} &= \frac{V}{\frac{1}{3}I_x} = \frac{\frac{2}{3}I_x \cdot 240k\Omega}{\frac{1}{3}I_x} \\ &= 2(240k\Omega) \end{aligned}$$


$$z_{eq} = 480k\Omega$$

Now we combine the  $240\text{k}\Omega$  and  $480\text{k}\Omega$ .

$$R = 240\text{k}\Omega \parallel 480\text{k}\Omega = 240\text{k}\Omega \cdot \frac{1}{2}$$

$$R = 240\text{k}\Omega \cdot \frac{2}{3} = 160\text{k}\Omega$$

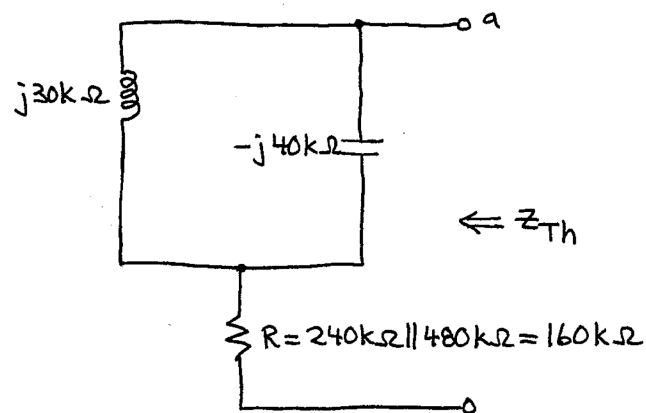Finally, we turn off the  $V_S$  source and look into the circuit from the a, b terminals to find  $z_{Th}$ :



$$z_{Th} = j30\text{k}\Omega \parallel -j40\text{k}\Omega + 160\text{k}\Omega$$

$$= j10\text{k}\Omega \cdot 3 \parallel -4 + 160\text{k}\Omega$$

$$= j10\text{k}\Omega \cdot \frac{-12}{-1} + 160\text{k}\Omega$$

$$= j120\text{k}\Omega + 160\text{k}\Omega$$

$$\text{or } z_{Th} = 160\text{k}\Omega + j120\text{k}\Omega$$