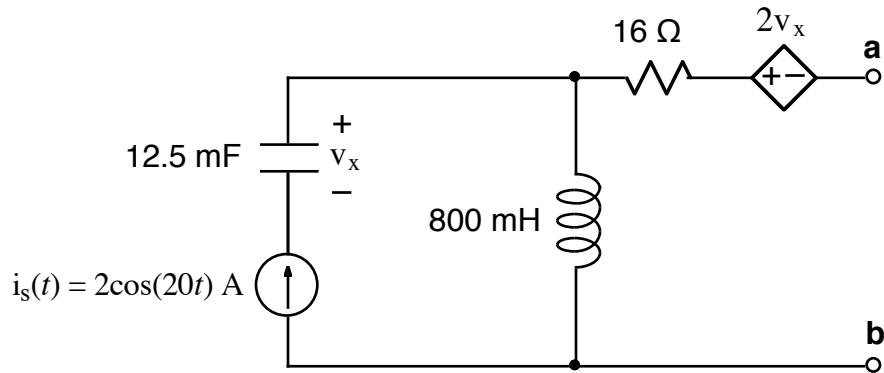


Ex:




- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $i_s(t)$, and show numerical impedance values for R, L, and C. Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for V_{Th} and the numerical impedance value of z_{Th} .

$$\text{Sol'n: a)} \quad \omega = 20 \text{ rad/s from } i_s(t)$$

$$I_s = 2 \angle 0^\circ \text{ A}$$


$$z_C = -j \frac{1}{\omega C} = -j \frac{1}{20 \text{ rad/s} \cdot 12.5 \text{ mF}} = -j \frac{1}{250 \text{ m}} = -j 4 \Omega$$
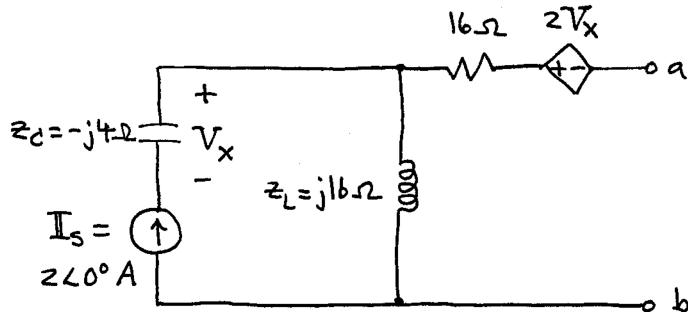
$$z_L = j \omega L = j 20 \text{ rad/s} \cdot 800 \text{ mH} = j 16 \text{ kN/A} = j 16 \Omega$$



b) $V_{Th} = V_{ab}$ open circuit.

Use node voltage V_1 :

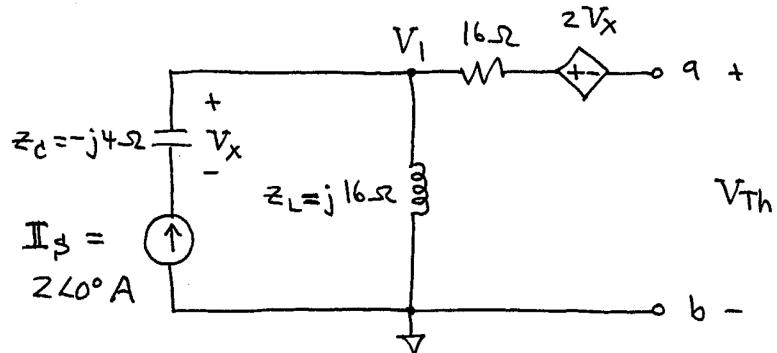

$$V_1 \text{ (from } I_s \cdot z_L) = 2\angle 0^\circ A \cdot j16\Omega = j32V$$


We've 0V across 16Ω since no current flows.

$$\text{Thus, } V_{Th} = V_1 - 2V_x.$$

$$V_x = -I_s z_C = -2\angle 0^\circ A \cdot (-j4\Omega) = j8V$$

$$\text{So } V_{Th} = j32V - 2(j8V) = j16V \text{ or } 16\angle 90^\circ V$$

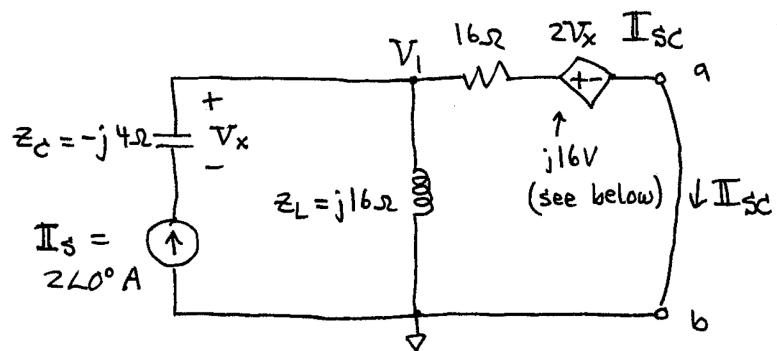To find z_{Th} , use $z_{Th} = \frac{V_{Th}}{I_{SC}}$




Since C is in series with current source, we have $V_x = -I_s z_C = j8V$ as before.

Thus, $2V_x = j16V$. We can now treat the dependent source as an independent source of $j16V$.

Now we use superposition to find I_{sc} :

case I: I_s on, $2V_x$ off

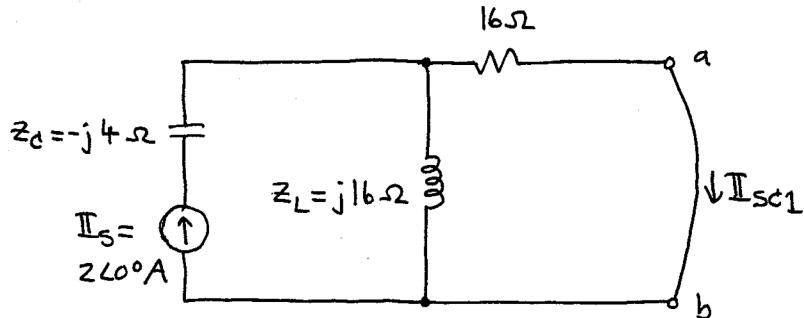


This is a current divider.

$$I_{sc1} = I_s \cdot \frac{z_L}{z_L + 16\Omega} = \frac{j16\Omega I_s}{j16\Omega + 16\Omega} = \frac{j I_s}{1+j}$$

$$= 2\angle 0^\circ A \cdot \frac{j}{1+j} \cdot \frac{1-j}{1-j} = 2\angle 0^\circ A \frac{1+j}{1^2 + 1^2} = 1+j A$$

$$I_{sc1} = 1+j A$$

Case II: I_s off, $2V_x$ on

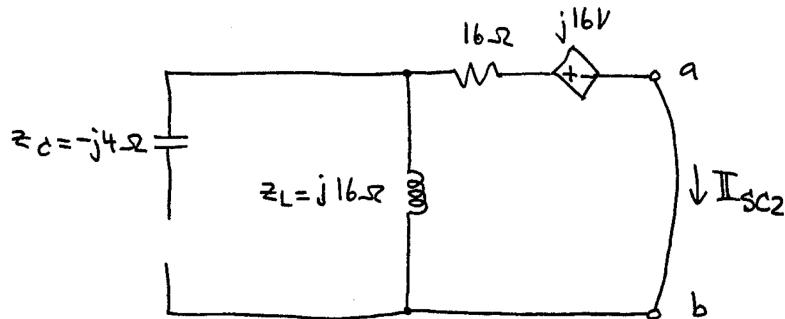

We have a V-loop on the right:

$$I_{sc2} = \frac{-j16V}{16\Omega + z_L} = \frac{-j16V}{16\Omega + j16\Omega} = \frac{-j}{1+j} A$$

$$" = \frac{-j}{1+j} \frac{1-j}{1-j} A = \frac{-1-j}{1^2+1^2} = \frac{-1-j}{2} A$$

Sum the results: $I_{sc} = I_{sc1} + I_{sc2}$

$$= 1+j A + \frac{-1-j}{2} A$$

$$I_{sc} = \frac{1+j}{2} A \text{ or } \frac{1}{\sqrt{2}} \angle 45^\circ A$$

$$z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{j16V}{\frac{1+j}{2}} = \frac{16 \angle 90^\circ V}{\frac{1}{\sqrt{2}} \angle 45^\circ A} = 16\sqrt{2} \angle 45^\circ \Omega$$

$$z_{Th} = 16 + j16 \Omega$$

