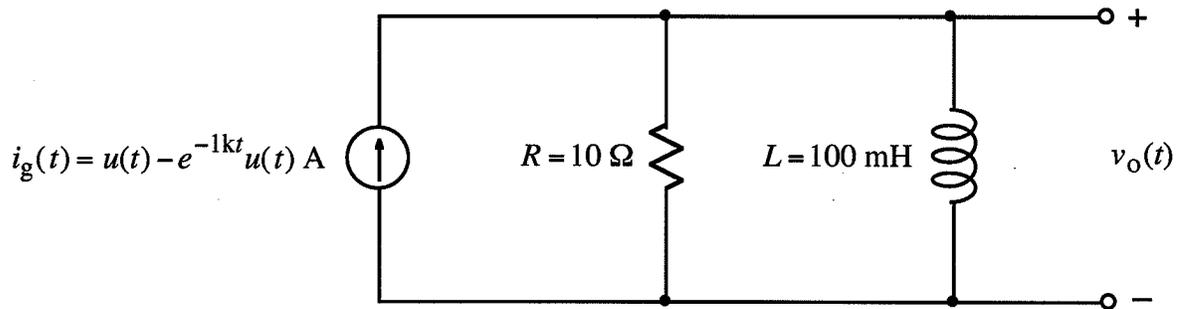


Ex:




- Write the Laplace transform  $I_g(s)$  of  $i_g(t)$ .
- Write the Laplace transform  $V_o(s)$  of  $v_o(t)$ . Be sure to include the effects of the initial current in the L.
- Write a numerical time-domain expression for  $v_o(t)$  where  $t \geq 0$ .

sol'n a)  $\mathcal{L} \{ i_g(t) = u(t) - e^{-1kt} u(t) \} \text{ A}$   
 $= \mathcal{L} \{ u(t) \} - \mathcal{L} \{ e^{-1kt} u(t) \} \text{ A}$   
 $= \frac{1}{s} - \frac{1}{s+1000} \text{ A}$

- b) There is no current at  $t=0^-$  since there is no current from the source for  $t < 0$ .

*s*-domain model:

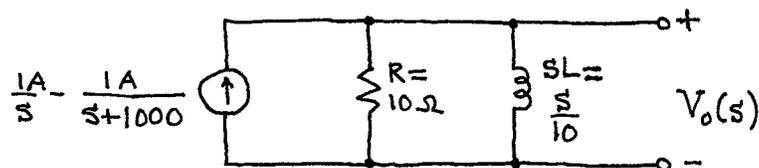

$$-10A_2 + A_2 = -10$$

$$-9A_2 = -10$$

$$A_2 = \frac{10}{9}$$

$$A_1 = -10A_2 = -10 \left( \frac{10}{9} \right) = -\frac{100}{9}$$

$$\text{Thus, } \frac{-10s}{(s+1000)(s+100)} = \frac{-100/9}{s+1000} + \frac{10/9}{s+100}$$

$$V_o(s) = \frac{10}{s+100} - \frac{100/9}{s+1000} + \frac{10/9}{s+100}$$

$$v_o(t) = 10e^{-100t} - \frac{100}{9}e^{-1000t} + \frac{10}{9}e^{-100t} \quad \text{V} \quad t > 0$$

$$\text{or } v_o(t) = \left[ 10e^{-100t} - \frac{100}{9}e^{-1000t} + \frac{10}{9}e^{-100t} \right] u(t) \quad \text{V}$$

$$V_o(s) = I_g(s) \cdot z_{tot}$$

$$= \left( \frac{1A}{s} - \frac{1A}{s+1000} \right) R \parallel sL$$

$$= \left( \frac{1A}{s} - \frac{1A}{s+1000} \right) \frac{sRL}{sL+R}$$

$$V_o(s) = \left( \frac{1A}{s} - \frac{1A}{s+1000} \right) \frac{sR}{s + \frac{R}{L}}$$

$$V_o(s) = \left( \frac{1A}{s} - \frac{1A}{s+1000} \right) \frac{s10}{s+100} \Omega$$

$$V_o(s) = \frac{10}{s+100} V - \frac{10s}{(s+1000)(s+100)} V$$

c) We use partial fractions for the second term.

$$\begin{aligned} \frac{-10s}{(s+1000)(s+100)} &= \frac{A_1}{s+1000} + \frac{A_2}{s+100} \\ &= \frac{A_1(s+100) + A_2(s+1000)}{(s+1000)(s+100)} \end{aligned}$$

Match coefficients of each power of  $s$ .

$$A_1 + A_2 = -10 \quad \text{coeffs of } s$$

$$100A_1 + A_21000 = 0 \quad \text{coeffs of constants}$$

$$\text{or } A_1 = -10A_2$$