



Find poles and zeros of Z<sub>ab</sub>.

ans:  $Z_{ab} = \frac{25(s+5)(s+20)}{(s+30)(s+45)}$  zeros at s = -5, -20  
poles at s = -30, -45

sol'n: We find Z<sub>ab</sub>, (which is a transfer function), by using Laplace transformed circuit elements, (with initial conditions set to zero).

$$Z_{ab} = R_1 \parallel \left( sL + \frac{1}{sC} \parallel R_2 \right)$$

$$\frac{1}{sC} \parallel R_2 = \frac{R_2}{sC} = \frac{R_2}{1 + sR_2 C} = \frac{1/C}{1 + s}$$

$$" = \frac{50}{s+25} \quad 1 = \frac{1}{2(0.02)} = 25$$

$$sL + \frac{1}{sC} \parallel R_2 = \frac{s}{2} + \frac{50}{s+25} = \frac{s(s+25) + 50 \cdot 2}{2(s+25)}$$

$$= \frac{s^2 + 25s + 100}{2(s+25)} = \frac{(s+5)(s+20)}{2(s+25)}$$

$$\begin{aligned} Z_{ab} &= R_1 \parallel \frac{(s+5)(s+20)}{2(s+25)} = \frac{25 \cdot (s+5)(s+20)}{25 + (s+5)(s+20)} = \frac{25(s+5)(s+20)}{25 + 50s + 1250 + s^2 + 25s + 100} \\ &= \frac{25(s+5)(s+20)}{(s+30)(s+45)} \end{aligned}$$

zeros = roots of numerator = -5 and -20  
poles = roots of denominator = -30 and -45.