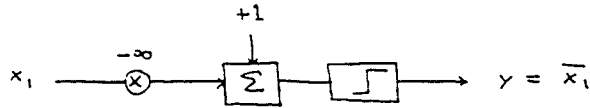


23 Mar 1990  
Neil E. Cottler

Perceptrons -  
McCulloch Pitts - Logic gates

NOT (or inverter) gates




$$x_1 = 0 \quad 0 \cdot -\infty + 1 = 1 > 0 \Rightarrow y = 1 \quad (\text{here } 0 \cdot -\infty = \infty)$$

$$x_1 = 1 \quad 1 \cdot -\infty + 1 = -\infty < 0 \Rightarrow y = 0$$

Truth Table

$x_1$	$y$
0	1
1	0

OR gate

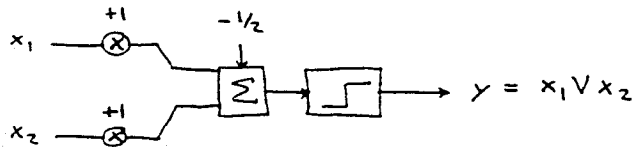


$$x_1 = 1 \text{ or } x_2 = 1 \quad 1 \cdot 1 - 1/2 = 1/2 > 0 \Rightarrow y = 1$$


$$x_1 \text{ and } x_2 = 0 \quad 0 \cdot 1 + 0 \cdot 1 - 1/2 = -1/2 < 0 \Rightarrow y = 0$$

Truth Table

$x_1$	$x_2$	$y$
0	0	0
0	1	1
1	0	1
1	1	1

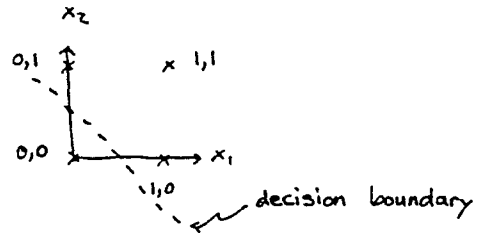

AND gate

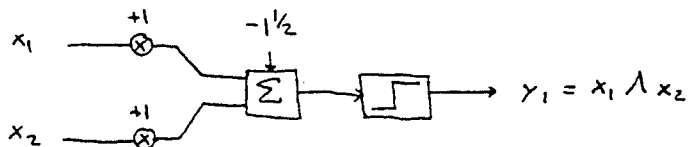

Truth Table

$x_1$	$x_2$	$y$
0	0	0
0	1	0
1	0	0
1	1	1

