
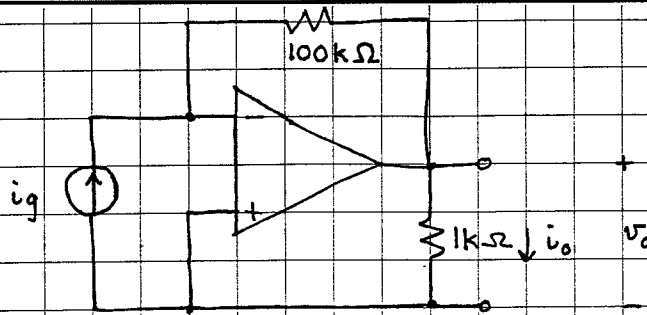


ex:

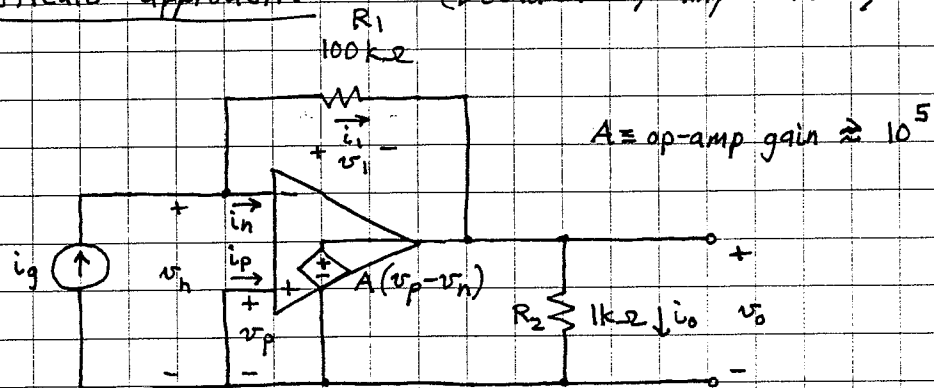

Difficult approach: (Detailed op-amp model)




Assume $i_n = i_p = 0$. Good assumption even if not linear mode, (i.e. negative feedback).

Use Kirchhoff's and Ohm's laws.


Sum of V drops around left loop avoided in this case because of i_g source. (In other situations, we would use this loop.)

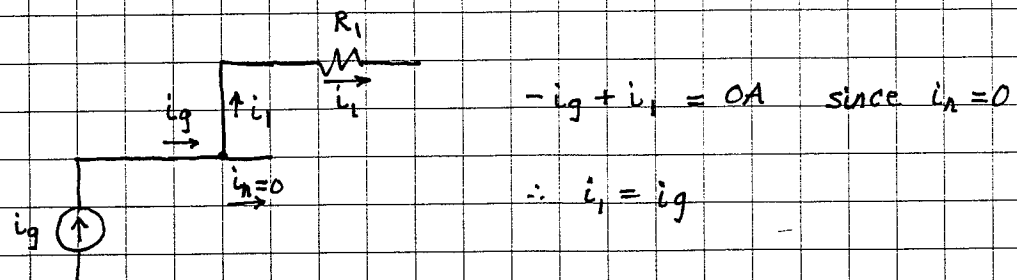Sum of currents out of node at - input of op amp:



Sum of V -drops around loop including feedback R and dependent V source:

ex: (cont)

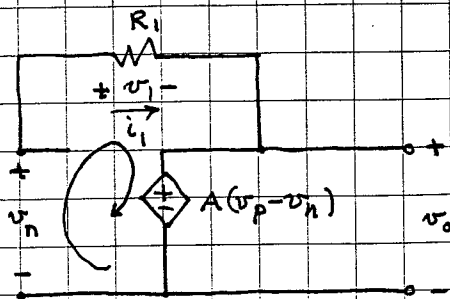

$$v_n - v_1 - A(v_p - v_n) = 0V$$

but $v_1 = i_1 R_1$ by Ohm's Law

$$v_o = A(v_p - v_n) \quad (\text{useful later on})$$

$v_p = 0$ since + input connected to bottom rail by wire

Making these substitutions gives:

$$v_n - i_1 R_1 - A(-v_n) = 0V$$

From before, $i_1 = i_g$. Thus, we may solve for v_n :

$$v_n - i_g R_1 + A v_n = 0V$$

$$\text{or } v_n (1+A) = i_g R_1 \quad \text{or } v_n = \frac{i_g R_1}{1+A} \quad \text{Note: } v_o = -i_g R_1 \frac{A}{1+A} \approx -i_g R_1$$

We observe that $i_g R_1 = v_1$ will be on the order of a few volts: typically. When divided by $1+A$, we have $v_n \approx 0V$.

Thus, $v_n \approx v_p$. This is always true in linear mode.

An easier way to solve the problem is to leave out the dependent voltage source and, instead, determine what value of v_o will cause $v_n = v_p$.

Now for the easier approach:

ex: (cont)

Easier approach: (Simplified Op-Amp model)

Assume $i_n = i_p = 0A$ as always

Assume $v_n = v_p$ (Linear mode)


Apply Kirchhoff's and Ohm's laws and follow specific steps:

1) Determine v_p : Here $v_p = 0V$, since is v across wire.

2) Set $v_n = v_p$: $v_n = v_p = 0V$ here.

3) Calculate current, ^{call it i_s ,} i_s flowing toward node by - input of op-amp.

Here, $i_s = -i_g$

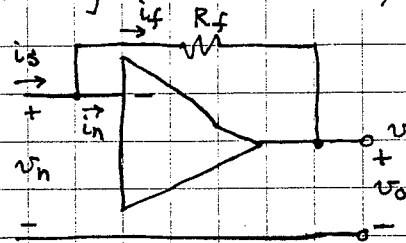

4) Use v -drop across feedback resistor, R_f , and Ohm's law to calculate i_s :

Here, $i_s = \frac{v_n - v_o}{R_f}$ (V drop across R_f is $v_n - v_o$ from v drops around loop sum to zero.)

5) Since $i_n = 0$, $i_s = i_g$.

6) Solve for v_o in terms of input signal:

$$\text{Here, } i_s = i_g \Rightarrow \frac{0V - v_o}{R_f = R_1} = i_g$$

$$\therefore v_o = -i_g R_1$$

This is very close to answer $v_o = -i_g R_1 \frac{A}{Hz}$ from difficult approach.

ex:(cont)

7) v_o is unaffected by "load" resistor R_2 .

Note: This curious result occurs because we assume an ideal dependent source in the op-amp. A more detailed model would include a resistor, R_o , in series with the dependent V source in the op-amp. Typically, $R_o \approx 10\Omega$. If the load resistor is much larger than R_o , we may safely ignore R_o .

$$\text{Here, } i_o = \frac{v_o}{R_2}$$

Now we can answer the problem at hand:

$$v_o = -i_g R_1 \quad \text{and} \quad i_o = \frac{v_o}{R_2} \quad \Rightarrow \quad i_o = -i_g \frac{R_1}{R_2}$$

$$\therefore \frac{i_o}{i_g} = -\frac{R_1}{R_2} = -\frac{100\text{k}\Omega}{1\text{k}\Omega} = -100$$