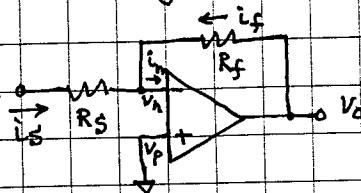


ex:

Which op-amp config, (inverting or noninverting), has highest input resistance. Use that config to design amp with V-gain of 1000.

Inverting: V_s



$$1) V_h = V_p = 0V$$

$$\text{input resistance } R_{in} = \frac{V_s}{i_s}$$

equiv circuit



$$\text{clearly } \frac{V_s}{i_s} = R_s \quad \text{since } i_s = \frac{V_s - 0V}{R_s} = \frac{V_s}{R_s}$$

$$\text{gain} = \frac{V_o}{V_s}$$


$$i_n = 0 \text{ so } i_f = -i_s$$

Feedback current flows in series resistor R_s .

$$\begin{aligned} V_o &= i_f R_f \quad \text{since } V_h = 0 \quad (V_o = V_h + i_f R_f) \\ &= -i_s R_f \quad \text{since } i_n = 0 \\ &= -\frac{V_s}{R_s} R_f \quad \text{from above} \end{aligned}$$

$$\text{gain} = \frac{V_o}{V_s} = -\frac{R_f}{R_s}$$

Non-inverting:

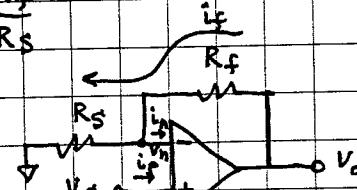

$$\text{input resistance} = \frac{V_s}{i_s} = \frac{V_s}{i_f} = \frac{V_s}{0} = \infty$$

This has the higher input resistance.

$$\text{gain} = \frac{V_o}{V_s} \quad \text{use ideal op-amp rules to find gain.}$$

$$1) V_h = V_p \text{ and } V_p = V_s \Rightarrow V_h = V_s$$

ex: (cont) 2) $i_n = i_p = 0A \Rightarrow i_f$ flows thru R_f and R_s

$$i_f = \frac{v_n - 0V}{R_s} = \frac{v_p - 0V}{R_s} = \frac{v_s - 0}{R_s} = \frac{v_s}{R_s}$$

$$v_o = v_n + i_f R_f = v_n + \frac{v_s}{R_s} R_f = v_p + \frac{v_s}{R_s} R_f = v_s + \frac{v_s}{R_s} R_f$$

$$\therefore v_o = v_s \left(1 + \frac{R_f}{R_s} \right)$$

$$\text{gain} = \frac{v_o}{v_s} = 1 + \frac{R_f}{R_s}$$

We want gain = 1000. Use $\frac{R_f}{R_s} = 999$.

Engineering considerations:

1) R's we use are 10% so we just use $\frac{R_f}{R_s} = 1000$.

2) Current i_f comes from v_o terminal of op-amp. Op-amp such as LF353 that we use in lab is rated for max output current of 10 mA.

This means we must choose R_s and R_f such that

$$i_f \leq 10 \text{ mA. } i_s = \frac{v_n}{R_s} = \frac{v_s}{R_s} \text{ and } i_f = \frac{v_o - v_n}{R_f} = \frac{v_o - v_s}{R_f}$$

Given our gain is 1000 and v_o cannot exceed op-amp pwr supply voltages, we conclude that $|v_o| \leq 12V$, (if pwr supply V's are $V_{CC} = 12V$ $-V_{CC} = -12V$).

$$\text{Then } |v_s| \leq \frac{12V}{1000} = 12mV.$$

$$\text{So we need } \frac{12mV}{R_s} \leq 10 \text{ mA} \text{ or } R_s \geq \frac{12mV}{10 \text{ mA}} = 1.2 \Omega$$

Just to be safe we can use $R_s + R_f \geq 12k\Omega$ so that

if $v_o = 12V$ and $v_n \neq v_p$, (because v_s is too large and we no longer have linearity), we still have $i_f \leq 10 \text{ mA}$. \therefore Use $R_s = 13\Omega$ $R_f = 13k\Omega$.

Note: $R_f < 10M$ also recommended so feedback not too weak. Double these for safety margin.