
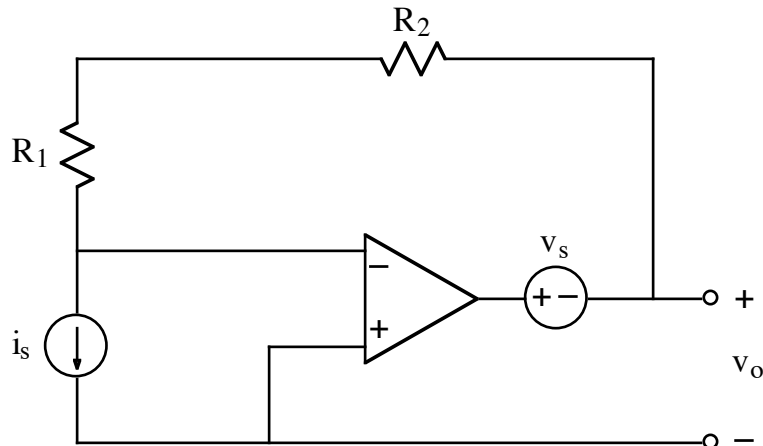


Ex:

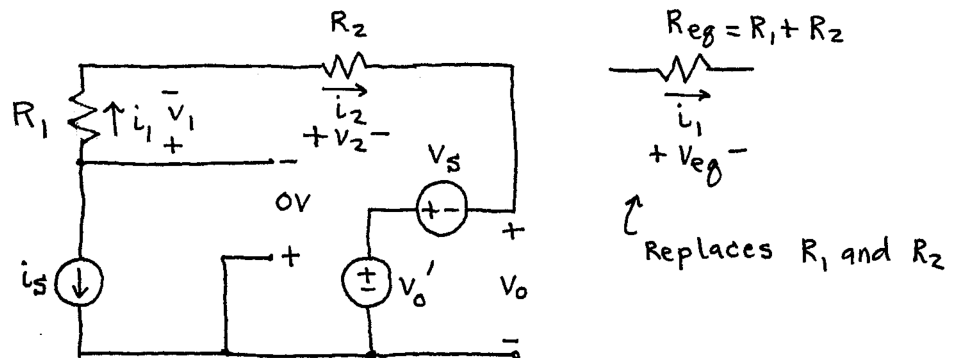

The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for v_o in terms of not more than v_s , i_s , R_1 , and R_2 .

sol'n: We assume a 0V drop across the + and - inputs of the op-amp, and we replace the op-amp output with a src called v_o' .



We may combine R_1 and R_2 into one resistor: $R_{eq} \equiv R_1 + R_2$.

R_{eq} carries current i_1 and has v -drop $V_{eq} = i_1 R_{eq}$.

We now look for v-loops, including those passing thru the $0V$ drop across the op-amp inputs.

The only v-loop not containing an i-src is on the right side.

$$-0V - v_{eg} + v_s - v_o' = 0V$$

If we ignore dangling wires, we have no nodes where three or more wires are connected.

Thus, we have no i-sum eq's for nodes.

We look for components in series that carry the same current.

$$i_1 = -i_s$$

Finally, we use Ohm's law for R_{eg} :

$$v_{eg} = i_1 R_{eg}$$

Since $i_1 = -i_s$, we have

$$v_{eg} = -i_s R_{eg}.$$

Using our earlier v-loop eq'n, we can solve for v_o' :

$$v_o' = -v_{eg} + v_s = i_s R_{eg} + v_s$$

We use a v-loop to find V_o from V_o' :

$$+V_o' - V_s - V_o = 0V$$

$$\text{or } V_o = V_o' - V_s$$


$$\text{or } V_o = i_s R_{eq} + V_s - V_s$$

$$\text{or } V_o = i_s R_{eq}$$

Consistency check:

Let $i_s = 0A$. Then no current flows in R_1 and R_2 . Thus, there is no v-drop across R_1 and R_2 .

We have a simple v-loop thru V_o :

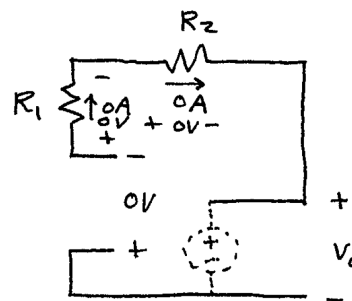

$$-0V - 0V - 0V - V_o = 0V$$

Thus $V_o = 0V$.

Plugging $i_s = 0A$ into $V_o = i_s R_{eq}$ gives $V_o = 0$ ✓