
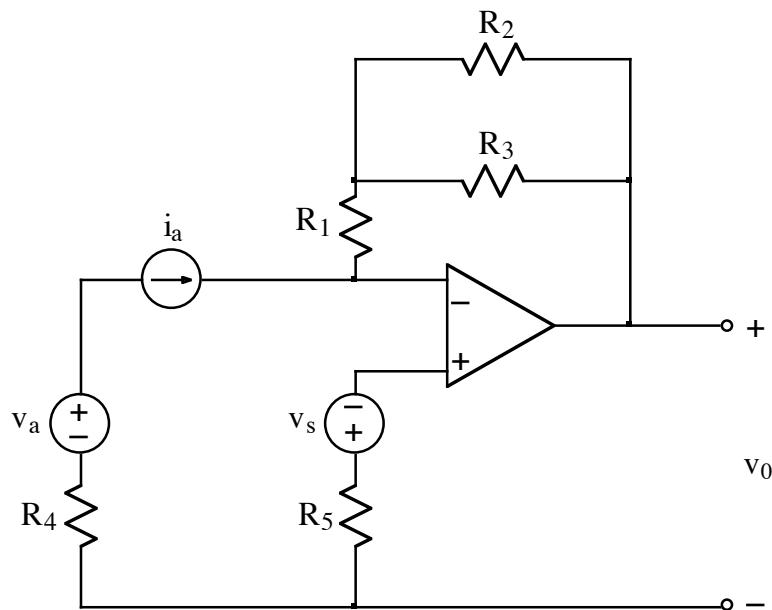


Ex:

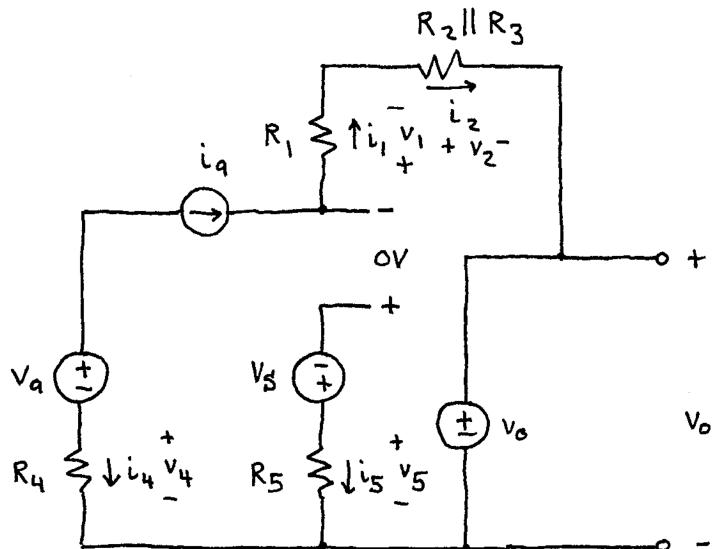

The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for v_0 in terms of not more than v_a , v_s , i_a , R_1 , R_2 , R_3 , R_4 and R_5 .

sol'n: Replace op-amp with src called v_o and assume v-drop across + and - terminals is 0V. We also combine R_2 and R_3 .



Write v-loops passing thru OV across + and - terminals:

$$+v_4 + v_9 + ? \quad \text{Don't use left-side v-loop because of current src.}$$

$$+v_5 - v_5 - OV - v_1 - v_2 - v_0 = OV$$

Write current sums at nodes.

The only true node is on the bottom.

$$-i_4 - i_5 - i_2 = 0A$$

Look for components in series carrying the same current:

$$i_4 = -i_9$$

$$i_1 = i_9$$

$$i_2 = i_1 = i_9$$

$$i_5 = 0A \text{ (since it is in series with an open circuit)}$$

We see that i_9 flows all the way around the outer loop.

We need only substitute for v's in v-loop using i_9 and Ohm's law for each resistor:

$$V_1 = i_1 R_1 = i_9 R_1$$

$$v_2 = i_2 \cdot R_2 \parallel R_3 = i_q \cdot R_2 \parallel R_3$$

$$v_5 = i_5 \cdot R_5 = 0 \cdot R_5 = 0V$$

Our v -loop becomes:

$$0V - v_S - 0V - i_q \cdot R_1 - i_q \cdot R_2 \parallel R_3 - v_o = 0V$$

Solving v_o gives the expression we seek:

$$v_o = -v_S - i_q (R_1 + R_2 \parallel R_3)$$