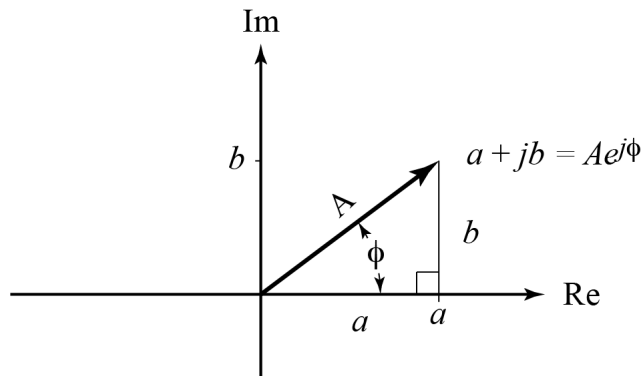


TOOL:

	<u>Sinusoid</u>	<u>Phasor</u>
	$P[A\cos(\omega t + \phi)]$	$\xrightarrow{P} Ae^{j\phi}$
	$P[A\sin(\omega t + \phi)]$	$\xrightarrow{P} -jAe^{j\phi}$



<u>Rect Form</u>	<u>Polar Form</u>
$a + jb$	$Ae^{j\phi}$
$a = A\cos\phi$	$A = \sqrt{a^2 + b^2}$
$b = A\sin\phi$	$\phi = \tan^{-1}\left(\frac{b}{a}\right)$
$A\cos(\omega t + \phi)$	$\xrightarrow{P} Ae^{j\phi}$
$\frac{d}{dt} \downarrow$	$\downarrow \cdot j\omega$
$\omega A\cos(\omega t + \phi + 90^\circ)$	$\xrightarrow{P} j\omega Ae^{j\phi}$

TOOL:

	<u>Impedance</u>	
$v = iR$	$\xrightarrow{P} \mathbf{V} = \mathbf{I}R$	$z_R = R$
$v = L \frac{di_L}{dt}$	$\xrightarrow{P} \mathbf{V} = j\omega \mathbf{L} \mathbf{I}$	$z_L = j\omega L$
$i = C \frac{dv_C}{dt}$	$\xrightarrow{P} \mathbf{I} = j\omega \mathbf{C} \mathbf{V}$	$z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$