



$$i_g = 15 \cos(10kt) \text{ A}$$

Find ave pwr dissipated in 20Ω R.

sol'n: $I_g = 15 \angle 0^\circ \text{ A}$ $j\omega L = j \cdot 10k \cdot 1m = j10 \Omega$
 $-j/\omega C = -j/10k \cdot 2.5\mu = -j/25m = -j40$

Use mesh currents:

$$i_A = I_g - I_2 \quad \text{constraint eq'n}$$

$$I_2(-j40) - 10(I_g - I_2) + I_2 j10\Omega + I_2 20\Omega = 0V$$

$$-I_g(-j40)$$

or $I_2(-j40\Omega + 10 + j10\Omega + 20\Omega) = I_g(-j40\Omega + 10)$

$$I_2 = I_g \frac{(10 - j40\Omega)}{30\Omega - j30\Omega} = \frac{I_g}{3} \frac{1 - j4\Omega}{1 - j\Omega}$$

$$= \frac{I_g}{3} \frac{1 - j4\Omega}{1^2 + 1^2} \cdot \frac{1 + j\Omega}{1 + j\Omega} = \frac{I_g}{3 \cdot 2} [(1+4) + j(1-4)]$$

$$= \frac{I_g}{6} (5 - j3) = \frac{15}{6} (5 - j3) \text{ A} = \frac{5}{2} (5 - j3) \text{ A}$$

$$= \frac{25}{2} - j\frac{15}{2} \text{ A}$$

$$= 14.6 \angle -31^\circ \text{ A}$$

$$V_{20\Omega} = I_2 \cdot 20\Omega = 292 \angle -31^\circ \text{ A}$$

$$\theta_v - \theta_i = -31^\circ - -31^\circ = 0^\circ \quad (\text{Always } 0^\circ \text{ for an R})$$

$$P_{20\Omega} = \frac{i_m v_m}{2} \cos(\theta_v - \theta_i) \quad i_m = |I_2| = 14.6$$

$$v_m = |V_{20\Omega}| = 292$$

$$\therefore P_{20\Omega} = \frac{14.6 \cdot 292}{2} (\cos 0^\circ = 1) = 2130 \text{ W}$$