



a) Calculate V_s (rms) given $I_L = 30 + j10$ A (rms)

$$\begin{aligned} \text{sol'n: } V_s \text{ (rms)} &= I_L \text{ (rms)} (0.2 + j1.6) + 2400 \angle 0^\circ \text{ V (rms)} \\ &= I \cdot Z + V_{\text{load}} \\ &= (30 + j10)(0.2 + j1.6) \text{ V} + 2400 \text{ V (rms)} \\ &= 6 - 16 + j(2 + 48) + 2400 \text{ V (rms)} \\ &= 2390 + j50 \text{ V (rms)} \end{aligned}$$

$$\text{or } V_s \text{ (rms)} = 2391 \angle 1.2^\circ \text{ V (rms)}$$

b) Calculate ave (or real) and reactive power for line z .

sol'n: Only the resistance dissipates ^{real} power.

$$\therefore P = |I_L \text{ (rms)}|^2 \cdot 0.2 \Omega = |30 + j10|^2 \cdot 0.2 \text{ W}$$

$$P = \sqrt{30^2 + 10^2}^2 \cdot 0.2 \text{ W} = 1000 \cdot 0.2 \text{ W} = 200 \text{ W}$$

$$Q = |I_L \text{ (rms)}|^2 \cdot 1.6 \Omega = 1600 \text{ VAR}$$

↑ Volt-Amps Reactive

c) Calculate ave and reactive power for V_s .

$$\begin{aligned} \text{sol'n: } \theta_v - \theta_i &= \angle V_s \text{ (rms)} - \angle I_L = 1.2^\circ - \tan^{-1} \frac{10}{30} \\ &= 1.2^\circ - 18.4^\circ = -17.2^\circ \\ &\quad \frac{2391}{\sqrt{1000}} \end{aligned}$$

$$P = |V_s \text{ (rms)}| |I_L \text{ (rms)}| \cos(-17.2^\circ) = 72.2 \text{ kW}$$

$$Q = |V_s \text{ (rms)}| |I_L \text{ (rms)}| \sin(-17.2^\circ) = -22.4 \text{ kW}$$

d) Calculate efficiency, $\eta = \frac{P_{\text{load}}}{P_{\text{source}}} \cdot 100\%$
given $P_{\text{load}} = 72 \text{ kW}$

Sol'n: $\eta = \frac{72 \text{ kW}}{72.2 \text{ kW}} \cdot 100\% = 99.72\%$

Note: $P_{\text{load}} = |I_L|_{\text{(rms)}} |2400 \angle 0^\circ \text{ V (rms)}| \cos(\theta_p - \theta_i)$
 $= |I_L \text{ (rms)}| \cos(-\angle I_L) \cdot 2400 \text{ V}$
 $= |I_L \text{ (rms)}| \cos(\angle I_L) \cdot 2400 \text{ V}$
 $= \text{Re} \{ I_L \text{ (rms)} \} \cdot 2400 \text{ V}$
 $= 30 \cdot 2400 \text{ W}$
 $= 72 \text{ kW}$