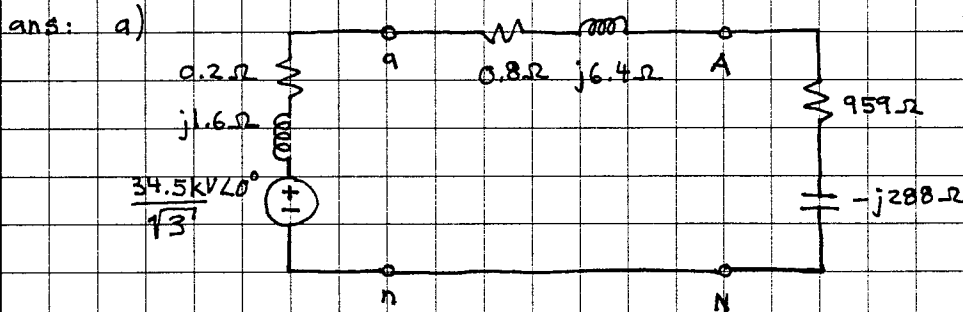



- a) Construct single-phase equiv circuit
- b) Calculate magnitude of line current
- c) Calculate " " " voltage at terminals of load
- d) " " " " " " " " source
- e) " " " phase current at load
- f) " " " " " in source



- b)  $|I_{aA}| = 19.9 \text{ A}$
- c)  $|V_{AB}| = 34.6 \text{ kV}$
- d)  $|V_{ab}| = 34.5 \text{ kV}$
- e)  $|I_{AB}| = 11.5 \text{ A}$
- f)  $|I_{ba}| = 11.5 \text{ A}$

sol'n: a) We must transform the  $\Delta$  source and  $\Delta$  load into a Y source and Y load, respectively.

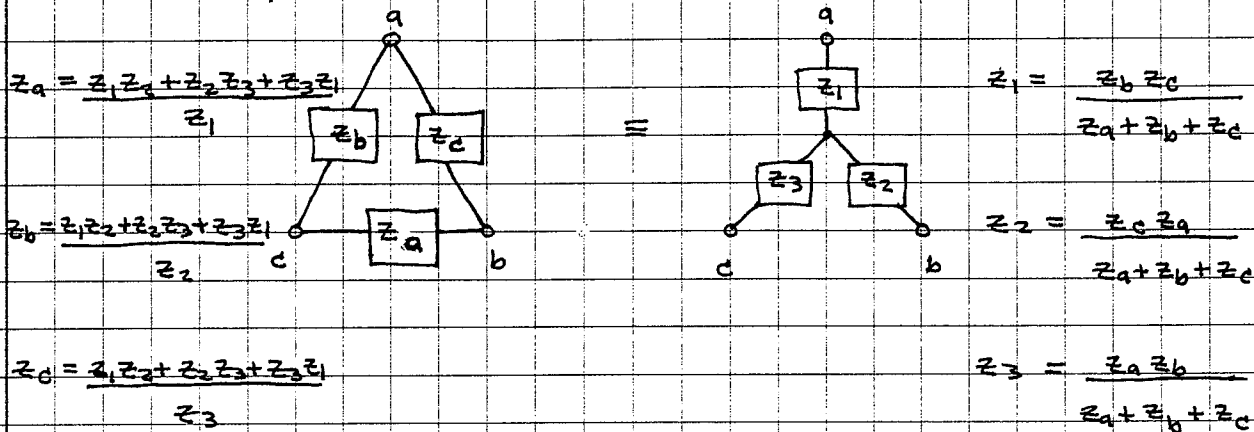For the  $\Delta$  load we use eq's 9.51 - 9.53 p 434 of Text:



If  $Z_a = Z_b = Z_c$ , then  $Z_1 = Z_2 = Z_3 = \frac{Z_a^2}{3Z_a} = \frac{Z_a}{3}$ .

$\therefore$  our  $\Delta$  load transforms to Y load (per phase) of

$$Z_\phi = \frac{2877 - j864}{3} = 959 - j288 \Omega$$

The source (or generator) internal impedances transform the same way.


$\therefore$  our  $\Delta$  source internal  $Z$ 's transform to Y source

(per phase)  $Z$ 's of  $Z_g = \frac{0.6 + j4.8}{3} = 0.2 + j1.6 \Omega$ .

One might suspect that we divide the source  $V$ 's by 3 to get the Y source  $V$ 's. This is not the case because each source is shifted by  $\pm 120^\circ$  from the other two sources.

Instead, we observe that, with no load, the voltages at the  $\Delta$  terminals are line voltages, (i.e. voltage differences across a pair of lines), such as  $V_{ab}$ .

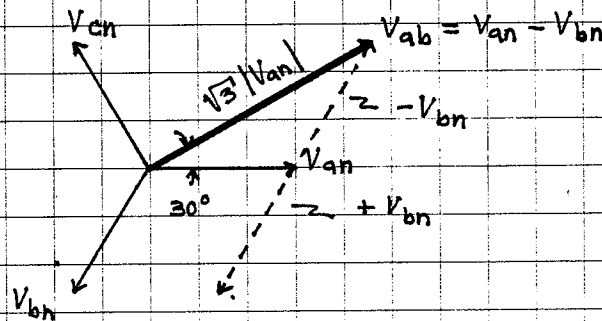If we have a Y source, then we find  $V_{ab} \equiv V_{an} - V_{bn}$  (for no load) from a phasor diagram:



Note: I'm assuming positive phase sequence since the problem statement in Text allows me to label a, b, c whichever way I desire.

From the diagram we see that  $|V_{ab}| = \sqrt{3} |V_{an}|$ .


It follows that if we go the other direction, (from  $V_{ab}$  to  $V_{an}$ ), we have:

$$\text{Y source: } |V_{an}| = \frac{|V_{ab}|}{\sqrt{3}} \quad \text{i.e.} \quad \frac{\Delta \text{ source } V}{\sqrt{3}}$$

Note: We also have a  $-30^\circ$  phase shift when we transform from  $V_{ab}$  to  $V_{an}$  (i.e. from  $\Delta$  source to Y source). We may, however, rotate our entire diagram any way we wish since the problem did not actually state which signal is at  $40^\circ$ .

$\therefore$  We assume  $\angle V_{an} = 0^\circ$ .

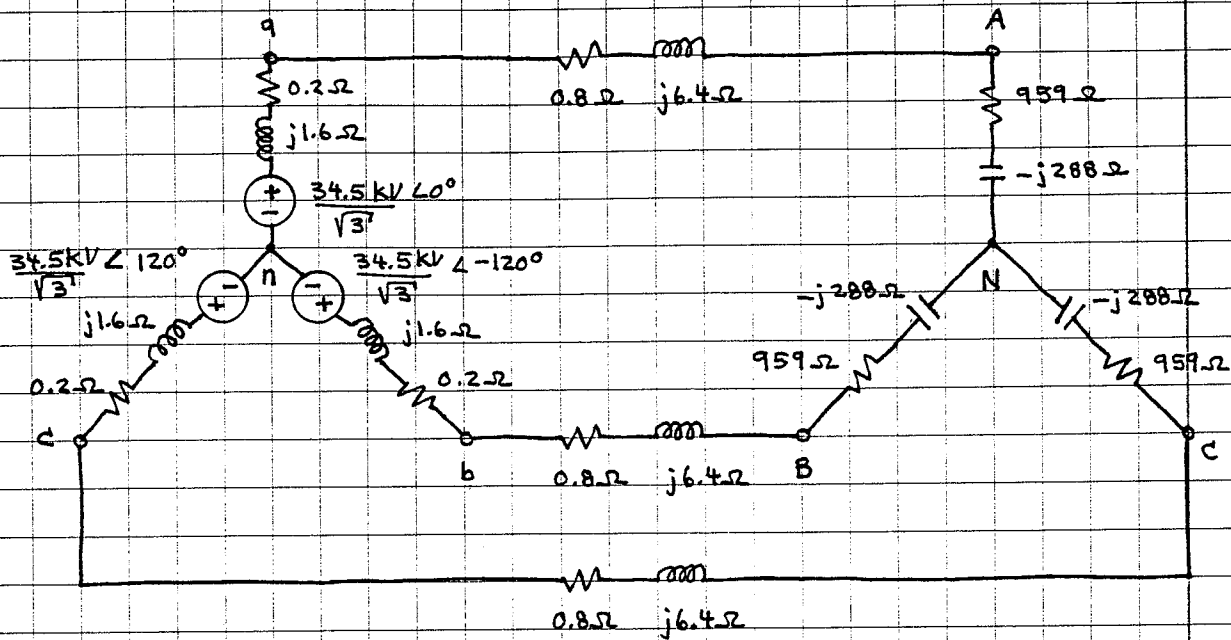
Since we don't transform them, our distribution line  $z$ 's remain the same. Our complete circuit has become:



Note: Because the terminal characteristics of our source and load are exactly the same as before, we have exactly the same line voltages and currents as before.

Thus, we may use a single phase equivalent to the above circuit as a model for line voltages and currents in the original  $\Delta$ - $\Delta$  configuration.

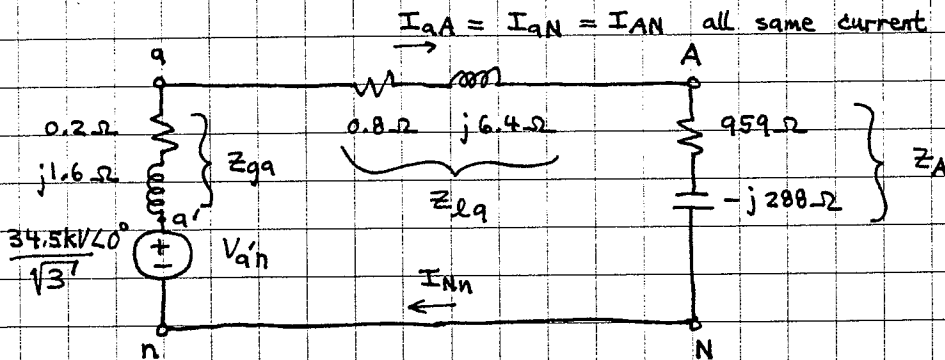For the single-phase equivalent, we just use one leg of the above circuit:



Note: This model gives correct  $I_{aA}$  line current, but not correct  $I_{nN}$ . Use it for everything but  $I_{nN}$ .

b) Magnitude of line current  $\equiv |I_{aA}| = \frac{|V_{\text{source}}|}{|Z_{\text{tot}}|}$

$$= \frac{34.5 \text{ kV} \angle 0^\circ / \sqrt{3}}{|Z_g + Z_{Lg} + Z_A|} = \frac{34.5 \text{ kV} / \sqrt{3}}{|0.2 + j1.6 + 0.8 + j6.4 + 959 - j288 \Omega|}$$

$$= \frac{34.5 \text{ kV} / \sqrt{3}}{|960 - j280 \Omega|} = \frac{34.5 \text{ kV} / \sqrt{3}}{|1 \text{ k}\Omega \angle -16.3^\circ|} = \frac{34.5 \text{ kV} / \sqrt{3}}{1 \text{ k}\Omega}$$

$$= \frac{34.5 \text{ A}}{\sqrt{3}} = 19.9 \text{ A}$$

$|I_{aA}| = 19.9 \text{ A}$

c) Magnitude of line voltage  $\equiv |V_{AB}| = \sqrt{3} |V_{AN}|$   
at terminals of load

(Same logic as  $|V_{ab}| = \sqrt{3} |V_{an}|$  in part (a))

$$|V_{AN}| = |I_{aA}| |Z_A| = 19.9 \text{ A} \cdot |959 - j288| = 19.9 \text{ A} \cdot 1 \text{ k}\Omega = 19.9 \text{ kV}$$

$$\therefore |V_{AB}| = \sqrt{3} |V_{AN}| = \sqrt{3} \cdot 19.9 \text{ kV} = 34.5 \text{ kV}$$

d) Magnitude of line voltage  $\equiv |V_{ab}| = \sqrt{3} |V_{an}|$   
at terminals of source

$$|V_{an}| = |I_{aA}| |Z_A + Z_{Lg}| \text{ or } |V_{an}| = |V_{an} - I_{aA} Z_{gA}|$$

Use 2<sup>nd</sup> form for answer guaranteed to be less than  $V_{a'n}$ .

$$|V_{an}| = \left| \frac{34.5 \text{ kV}}{\sqrt{3}} - \frac{34.5 \text{ kV}}{\sqrt{3}} \frac{Z_{gA}}{Z_{gA} + Z_{Lg} + Z_A} \right|$$

$$= \left| \frac{34.5 \text{ kV}}{\sqrt{3}} \left( 1 - \frac{Z_{gA}}{Z_{gA} + Z_{Lg} + Z_A} \right) \right| = \left| \frac{34.5 \text{ kV}}{\sqrt{3}} \frac{Z_{Lg} + Z_A}{Z_{gA} + Z_{Lg} + Z_A} \right|$$

$$= \frac{34.5 \text{ kV}}{\sqrt{3}} \frac{0.8 + j6.4 + 959 - j288}{0.2 + j1.6 + 0.8 + j6.4 + 959 - j288} = \frac{34.5 \text{ kV}}{\sqrt{3}} \frac{959.8 - j281.6}{960 - j280}$$

$$|V_{an}| = \frac{34.5 \text{ kV}}{\sqrt{3}} \left| \frac{1 \angle -16.35^\circ}{1 \angle -16.26^\circ} \right| = \frac{34.5 \text{ kV}}{\sqrt{3}} \frac{1}{1}$$

$$|V_{an}| = \frac{34.5 \text{ kV}}{\sqrt{3}}$$

$$\therefore |V_{ab}| = \sqrt{3} |V_{an}| = 34.5 \text{ kV}$$

Comment:  $|z_{ga}|$  and  $|z_{ea}| \ll |z_A|$  so only small part of total % drop is across  $z_{ga}$  and  $z_{ea}$ . In other words, the voltage across the load  $\approx$  generator voltage.

e) The phase current refers to the original  $\Delta$  load.

Phase current  $\equiv$  current through one leg of  $\Delta$  load  
 $\equiv I_{AB}$

For original  $\Delta$ - $\Delta$  circuit we have  $|I_{AB}| = \frac{|V_{AB}|}{|2877 - j864 \Omega|}$

and we can use  $|V_{AB}|$  from (b) (i.e. from single-phase model):

$$\begin{aligned} |I_{AB}| &= \frac{|V_{AB}|}{|2877 - j864|} = \frac{|V_{AB}|}{3|z_A|} = \frac{\sqrt{3}|V_{an}|}{3|z_A|} \\ &= \frac{\sqrt{3}|I_{aA}||z_A|}{3|z_A|} = \frac{|I_{aA}|}{\sqrt{3}} = \frac{19.9 \text{ A}}{\sqrt{3}} = 11.5 \text{ A} \end{aligned}$$

$$|I_{AB}| = 11.5 \text{ A}$$

f) Phase current in source refers to original  $\Delta$  circuit.

We want  $|I_{ab}|$ .

We have  $I_{aA} = I_{ca} - I_{ab}$  (sum of currents out of node = 0)

$$I_{ca} = I_{ab} \cdot (\angle 120^\circ) \Rightarrow |I_{aA}| = |I_{ab}| \cdot |\angle 120^\circ - 1|$$

$$\therefore |I_{ab}| = |I_{aA}| / \sqrt{3} = 19.9 \text{ A} / \sqrt{3} = 11.5 \text{ A} (= I_{AB} \text{ for } \Delta\text{-}\Delta)$$

