

The switch has been closed for a long time before opening at time $t=0$.


Note: Whenever a circuit configuration has existed "for a long time" it means forever — from $t=-\infty$ to $t=0$. Thus, all currents and voltages have achieved final values. In other words,
 $\frac{di}{dt} = 0$ for all currents, $\frac{dv}{dt} = 0$ for all voltages.

a) Find $i_1(t=0^-)$ and $i_2(t=0^-)$.

sol'n: At $t=0^-$ the circuit has had the same configuration "for a long time," and $\frac{di_1}{dt} = 0$ $\frac{di_2}{dt} = 0$.

For the L we have $v_L = L \frac{di}{dt} = L \cdot 0 = 0V$.

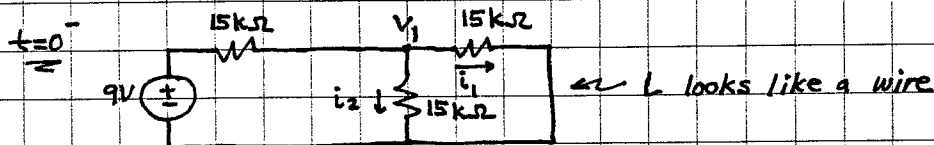Thus, the 30mH L looks like a wire (as L's always do for their final values), and our circuit model is:




We get V_1 from V-divider: $V_1 = 9V \cdot \frac{15k\Omega // 15k\Omega}{15k\Omega + 15k\Omega // 15k\Omega}$

$\therefore V_1 = 3V$

$i_1(t=0^-) = i_2(t=0^-) = V_1 / 15k\Omega = \frac{3V}{15k\Omega} = 0.2mA$

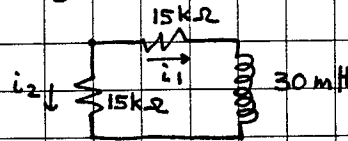b) Find $i_1(t=0^+)$ and $i_2(t=0^+)$.

sol'n: With the switch open, the 9V and $15k\Omega$ before the switch no longer affect i_1 and i_2 . Our model (for i_1 and i_2) becomes:



Since the current through the L cannot change instantly, we must have $i_1(t=0^+) = i_1(t=0^-)$.


But now we also have the two $15k\Omega$ R's in series. Thus, $i_2 = -i_1 = -i_1(t=0^-)$.

$$\therefore i_1(t=0^+) = 0.2\text{mA} \quad i_2(t=0^+) = -0.2\text{mA}$$

Note: The current in an R can change instantly, as happens here (with i_2 changing sign).

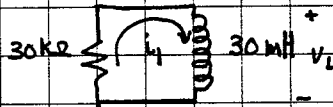c) Find $i_1(t)$ for $t \geq 0$

sol'n: Our circuit model (with $15k\Omega$ R's summed) is:



$$V_L = L \frac{di_1}{dt} \quad \text{and} \quad V_L = -i_1 \cdot 30k\Omega \quad \text{by Ohm's law}$$

$$\therefore -i_1 \cdot \underset{\text{R}}{30k\Omega} = L \frac{di_1}{dt} \quad \text{or} \quad i_1 \cdot R + L \frac{di_1}{dt} = 0 \text{ V}$$

Note: we used sum of V's around loop = 0V

$$\text{From text p. 279, } i_1(t) = i_1(0^+) e^{-tR/L} = 0.2\text{mA} e^{-t \cdot 30k\Omega / 30\text{mH}}$$

$$\therefore i_1(t) = 0.2\text{mA} \cdot e^{-t \cdot 10^6/s}$$

d) Find $i_2(t)$ for $t \geq 0^+$

sol'n: From part (b) we have $i_2(t) = -i_1(t)$ for $t \geq 0^+$

$$\therefore i_2(t \geq 0^+) = -0.2 \text{ mA} \cdot e^{-t \cdot 10^6 / 5}$$

e) Explain why $i_2(0^-) \neq i_2(0^+)$.

answer: As noted in the solution to (b), the current in an R can change instantly. It does so here to keep $i_1(t)$ the same when the switch opens.

Note: The R current can change instantly because an R stores no energy. It takes time to change the energy stored in an L, and energy = $\frac{1}{2} Li^2$.